

Frequency Synthesizers (2/2)

ZHAO BO


Institute of VLSI Design

Zhejiang University

Email: zhaobo@zju.edu.cn

Web: person.zju.edu.cn/zhaobo

TSPC

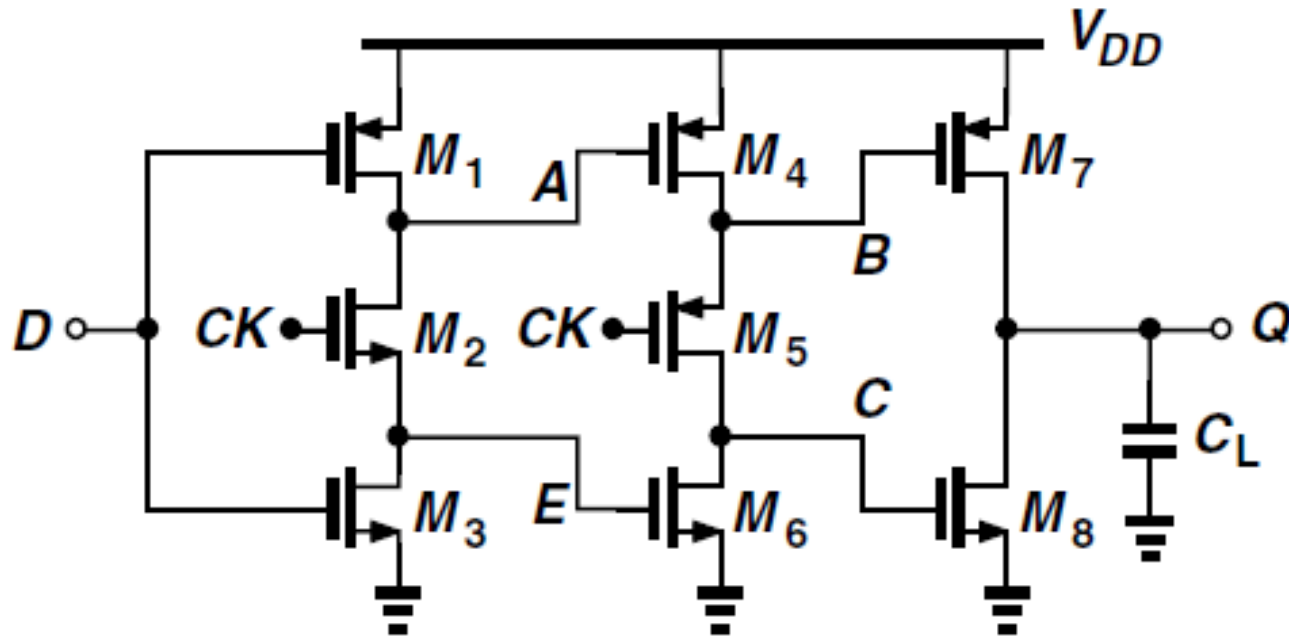


- ❑ In comparison to CML, TSPC is a kind of dynamic logic
- ❑ TSPC achieves relatively high speeds with low power dissipation (no static power)
- ❑ TSPC divider fails at very low clock frequencies due to the leakage of the transistors

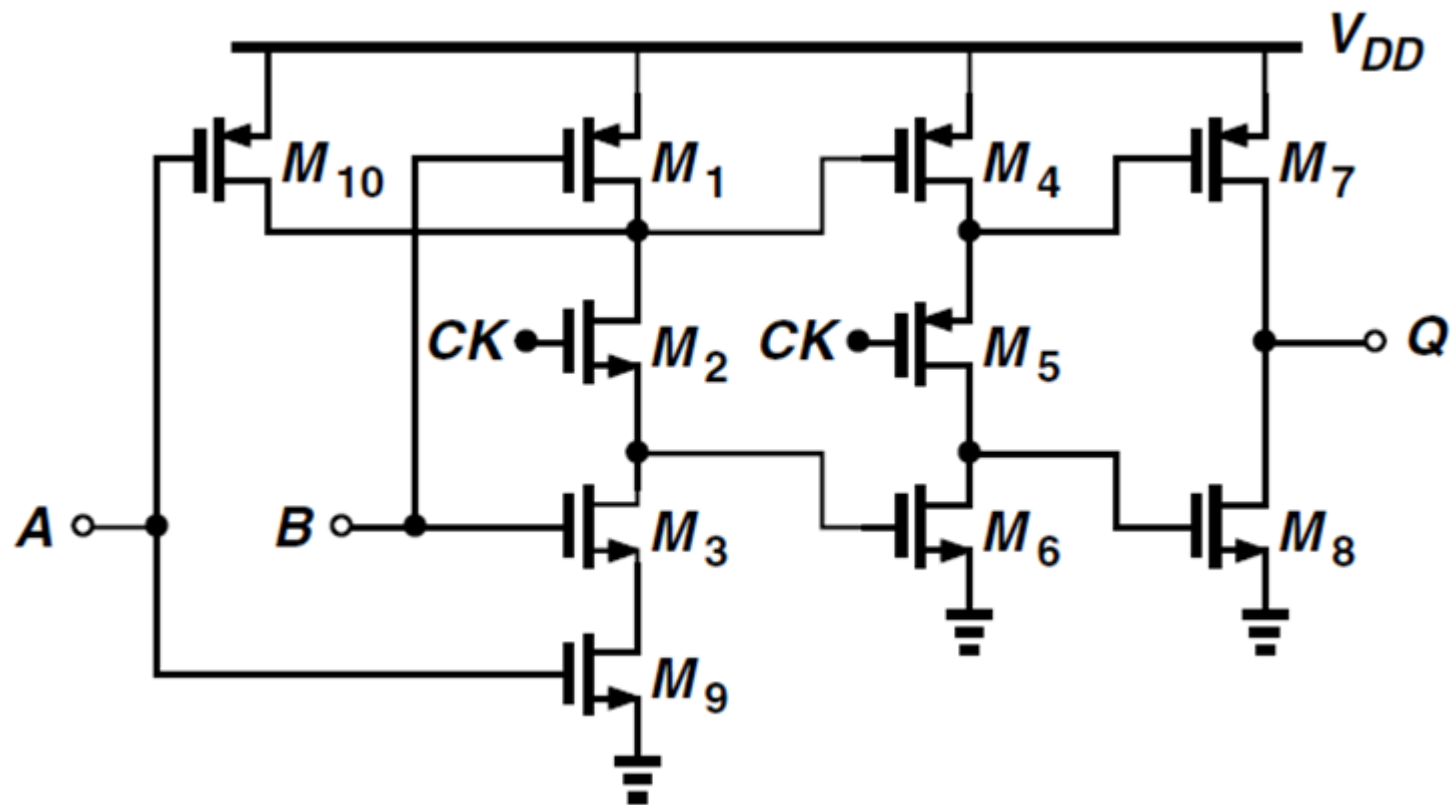[B. Razavi, RF Microelectronics]


TSPC Logic

□ The TSPC FF can readily incorporate logic at its input. For example, a NAND gate can be merged with the master latch



[B. Razavi, RF Microelectronics]


TSPC Ratioed Logic

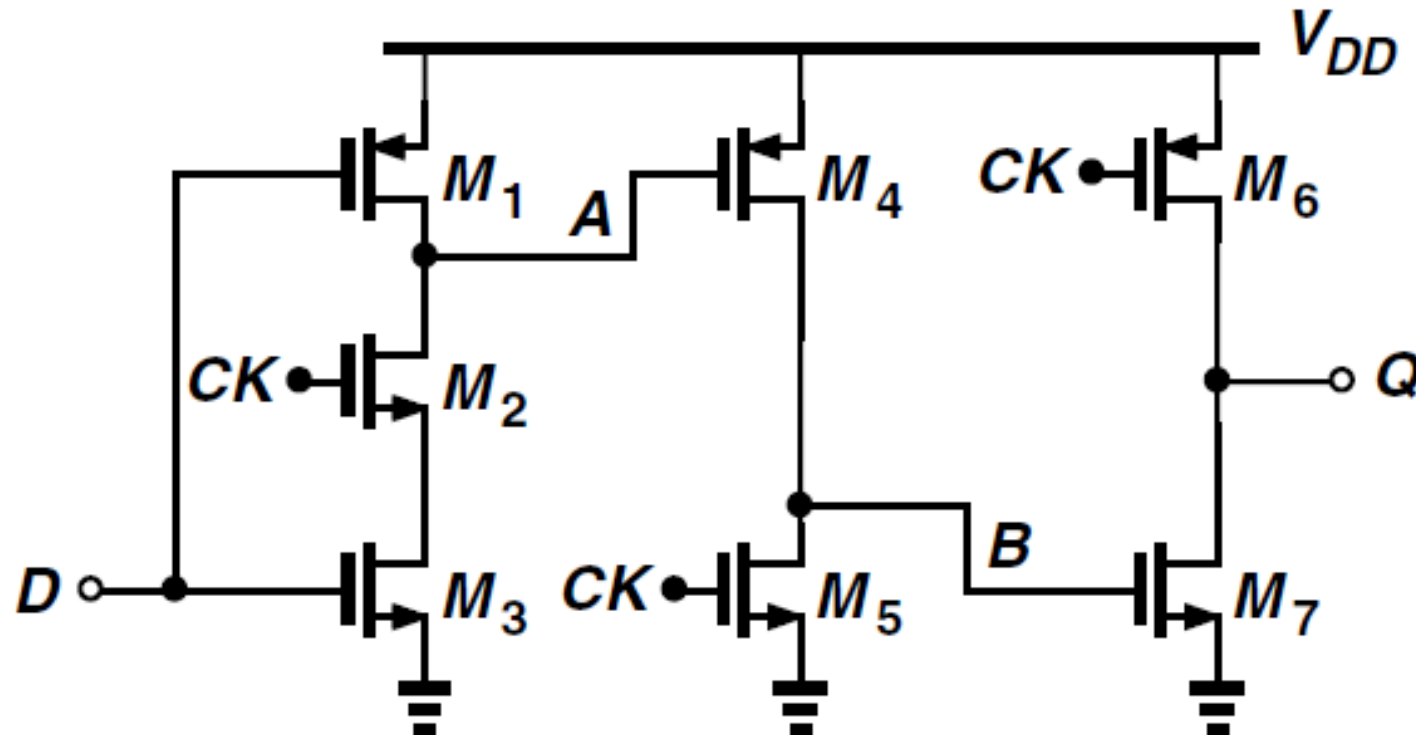

□ The slave latch is designed as “ratioed” logic, i.e., both NMOS devices are strong enough to pull down B and Q even if M_4 or M_6 is on.

[B. Razavi, RF Microelectronics]


Miller Divider

 

- If the circuit operates properly, $f_{out} = f_{in}/2$, yielding two components, $3f_{in}/2$ and $f_{in}/2$, at node X. The former is attenuated by the LPF, and the latter circulates around the loop
- Correct operation requires that the loop gain for $3f_{in}/2$ be sufficiently small and that for the latter exceed unity


[B. Razavi, RF Microelectronics]

Miller Divider

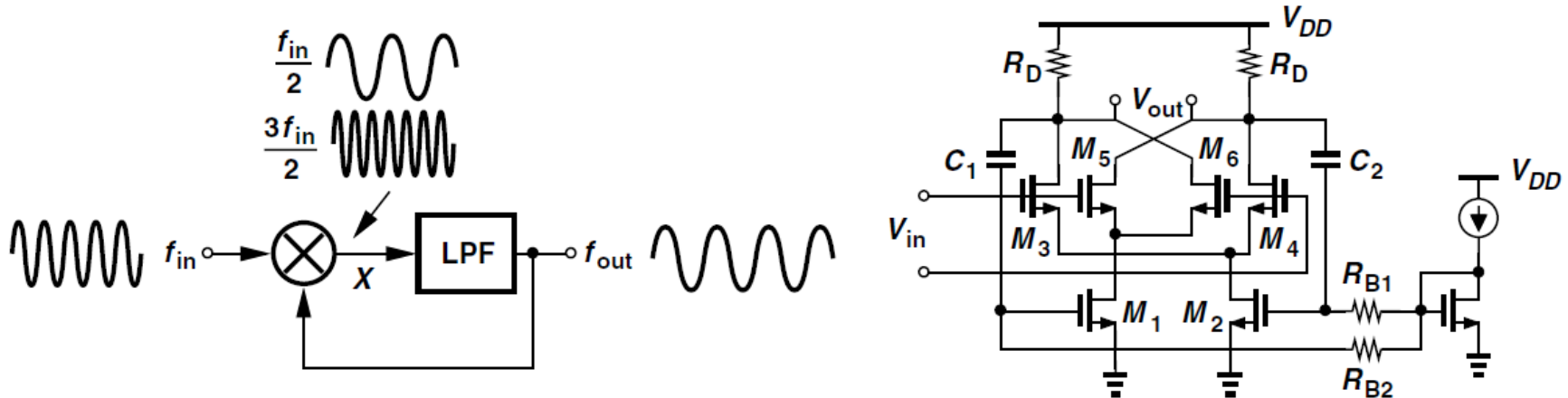

- ❑ With a shorter delay, Miller divider can provide a higher speed than CML logic
- ❑ However, that the divider loop requires some cycles to reach steady state, i.e., it does not divide correctly instantaneously


Third Harmonic

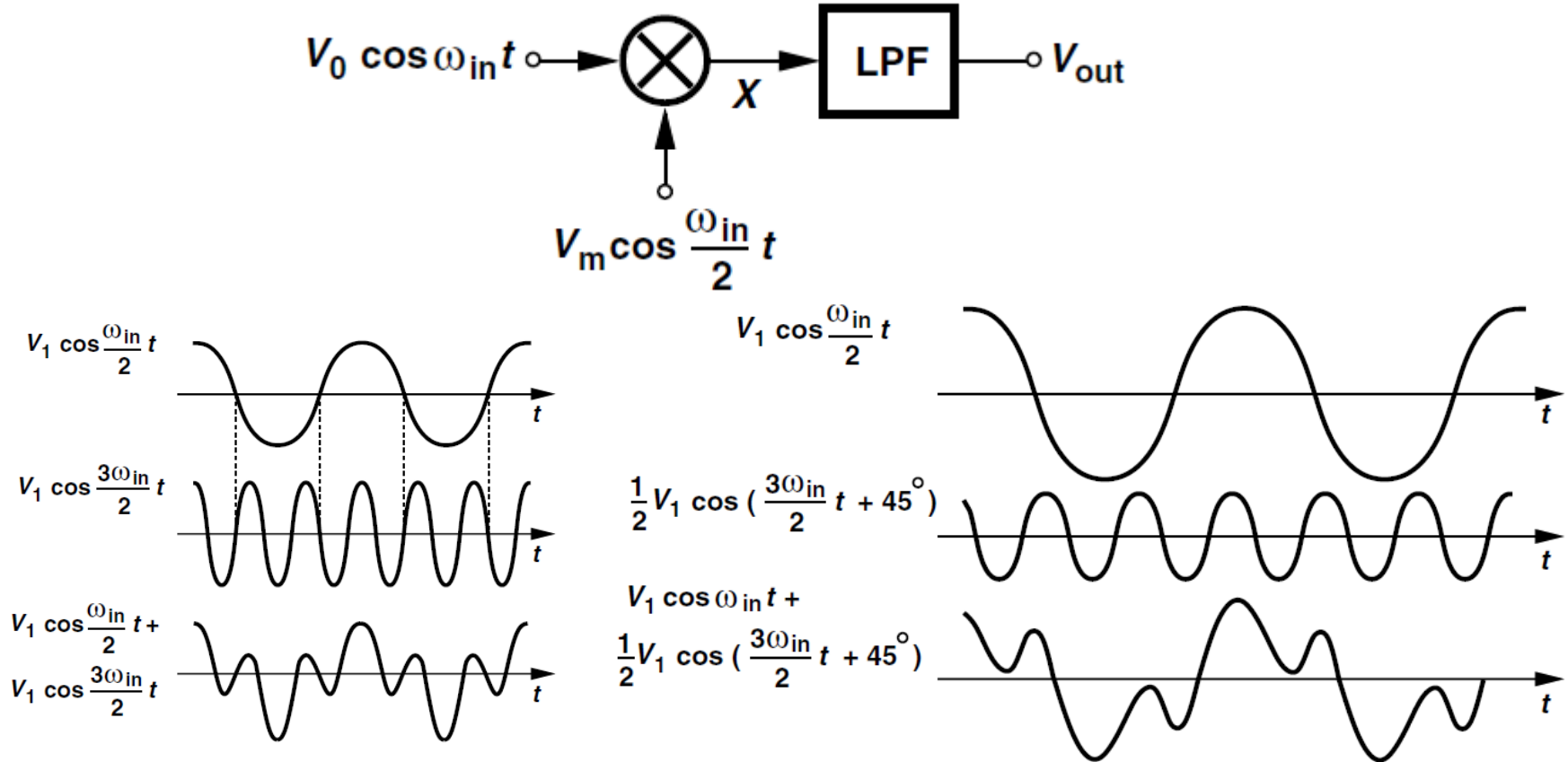

□ Miller divider operates properly if the third harmonic is attenuated and shifted to avoid the additional zero crossings

[B. Razavi, RF Microelectronics]

Inductive Load

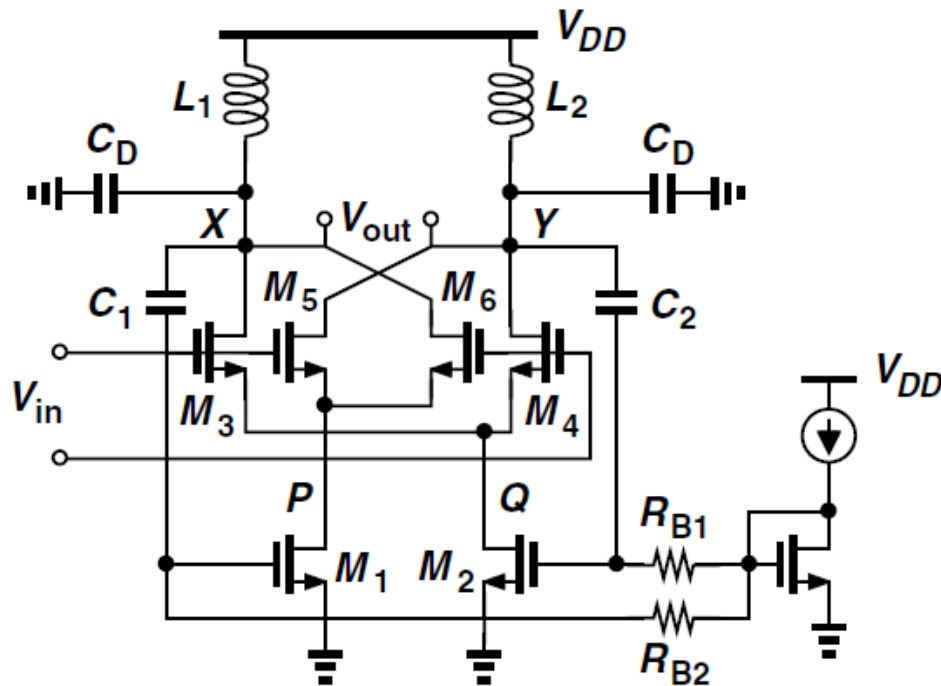

□ Gain-headroom and gain-speed trade-offs are greatly relaxed


□ Inductors take more layout area

□ Inductors L_1 and L_2 must resonate with the total capacitance at X and Y at the output frequency

□ The tanks significantly suppress the third harmonic of the desired output

[B. Razavi, RF Microelectronics]


Inductive Load

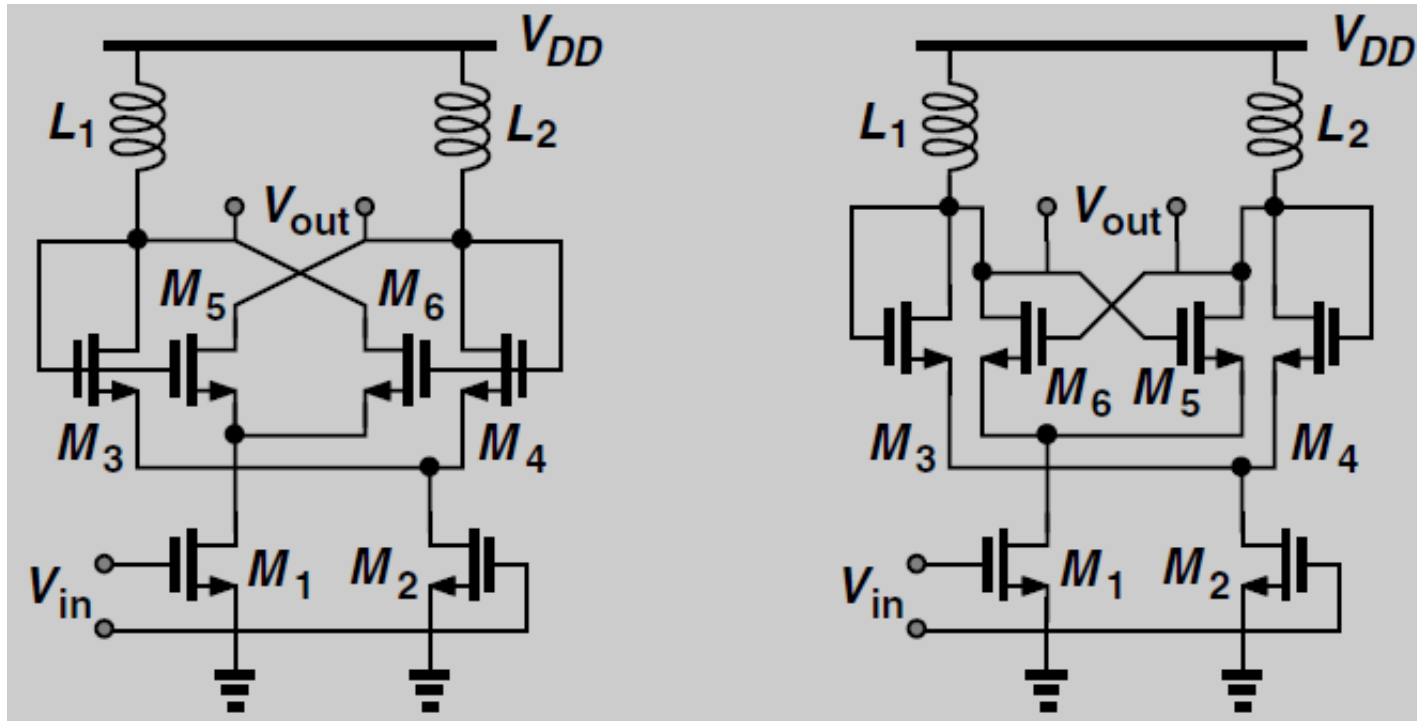

- Inductively-loaded with feedback to the switching quad, operating as a divider by 2
- An oscillator is formed by M_5 - M_6 and L_1 - L_2 is heavily loaded by M_3 - M_4

[B. Razavi, RF Microelectronics]

Passive Mixer

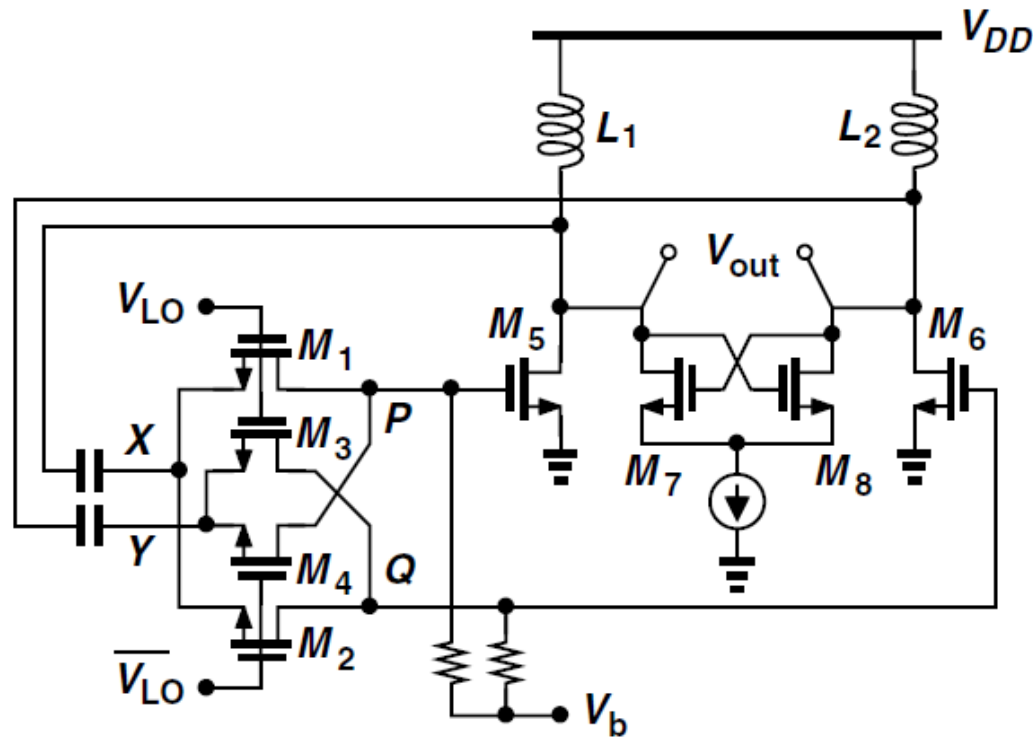


- ❑ M_1 - M_4 constitute a passive mixer and M_5 - M_6 an amplifier
- ❑ The cross-coupled pair M_7 - M_8 can be added to increase the gain by virtue of its negative resistance.

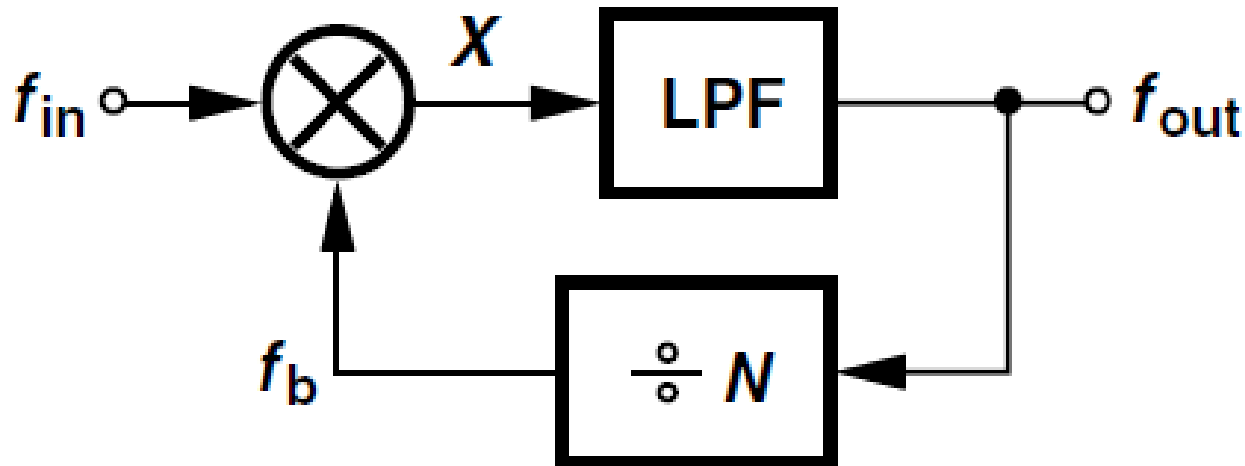[B. Razavi, RF Microelectronics]

Feedback Divider

□ A divider within the feedback loop can be used to produce moduli other than 2




□ If the sum is suppressed by the LPF, then $f_{out} = f_{in} - f_{out}/N$

$$f_{out} = \frac{N}{N+1} f_{in} \quad f_b = \frac{1}{N+1} f_{in}$$

[B. Razavi, RF Microelectronics]


Feedback Divider

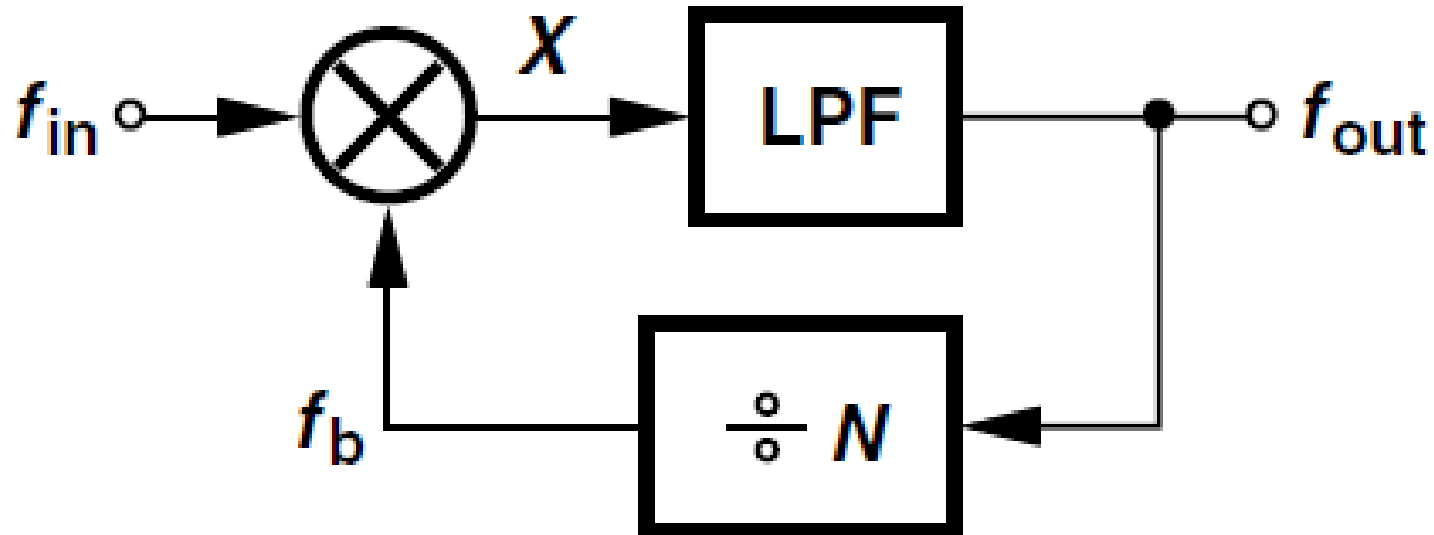

- ❑ The sum component at X comes closer to the difference component as N increases, such as $4f_{in}/3$ and $2f_{in}/3$, dictating a sharper LPF roll-off.
- ❑ The Miller divider suffers from port-to-port feedthroughs of the mixer


[B. Razavi, RF Microelectronics]

Spurs

 

- ❑ The feedthrough from the main input to node X produces a spur at f_{in}
- ❑ The feedthrough from Y to X creates a component at $f_{in}/3$


SSB Mixing

 

- ❑ The sum component is suppressed by single-sideband (SSB) mixing rather than filtering, thereby avoiding the problem of additional zero crossings
- ❑ however, this approach requires a broadband 90 degree phase shift, a very difficult design.



[B. Razavi, RF Microelectronics]

SSB Mixing

 

- ❑ Employing a $\div 2$ circuit and generating $f_{in}/3$ at the output generates quadrature outputs
- ❑ The principal drawback is that it requires quadrature LO phases as well


Injection-Locked Dividers

 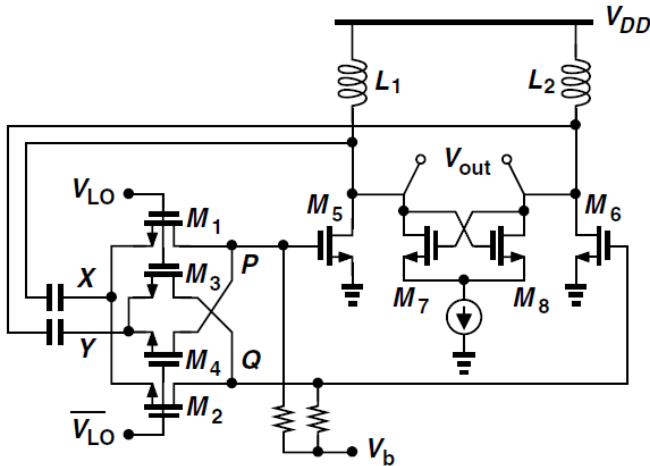

- Assume the cross-coupled pair is strong enough to produce oscillation, transistors M_5 and M_6 can now be viewed as devices that couple the mixer output to the oscillator
- If f_{in} varies across a certain “lock range,” the oscillator remains injection locked to the frequency component at node X
- If f_{in} falls outside the lock range, the oscillator is injection-pulled, thus producing a corrupted output

[B. Razavi, RF Microelectronics]

Injection-Locked Dividers

 

□ The mixer yields two components at node X, namely, $f_{in}-f_{out}/N$ and $f_{in}+f_{out}/N$.

□ If the oscillator locks to $f_{in}-f_{out}/N$, then

$$f_{out} = \frac{N}{N+1}f_{in}$$


□ If the oscillator locks to $f_{in}+f_{out}/N$, then

$$f_{out} = \frac{N}{N-1}f_{in}$$

□ The oscillator lock range must therefore be narrow enough to lock to only one of the two components


[B. Razavi, RF Microelectronics]

Injection-Locked Dividers

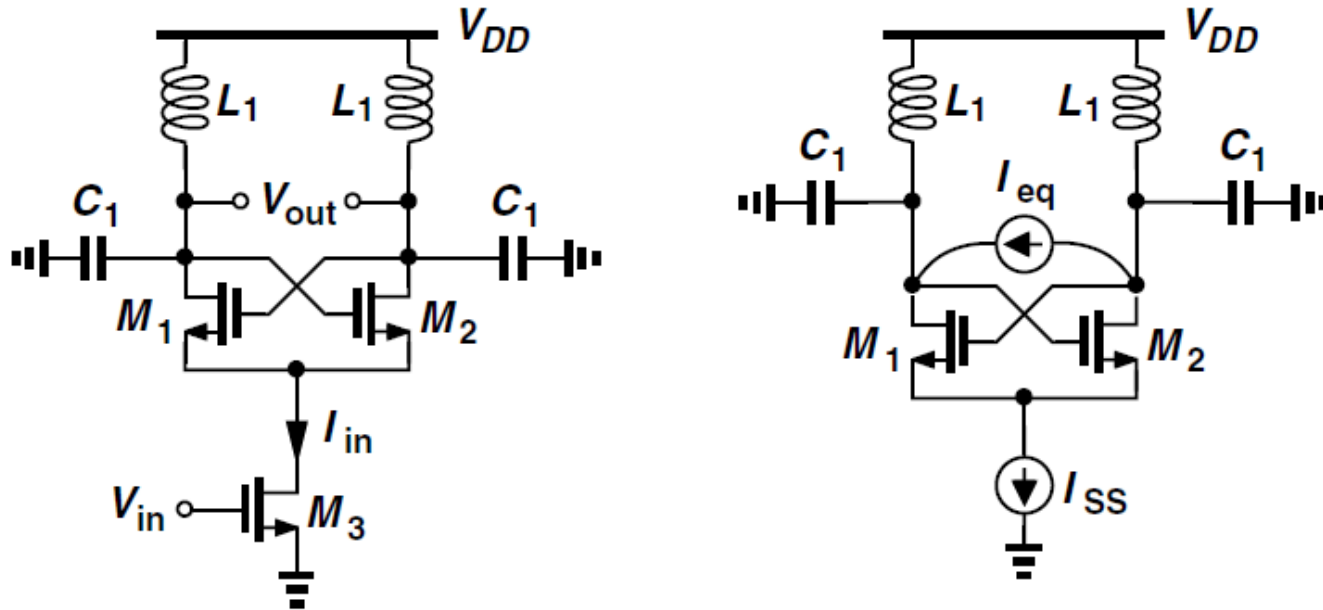

□ $I_{in} = g_m V_{in}$ is commutated by M_1 and M_2 and hence translated to $f_{out} \pm f_{in}$ as it emerges at the drains of these transistors.


Divider Noise

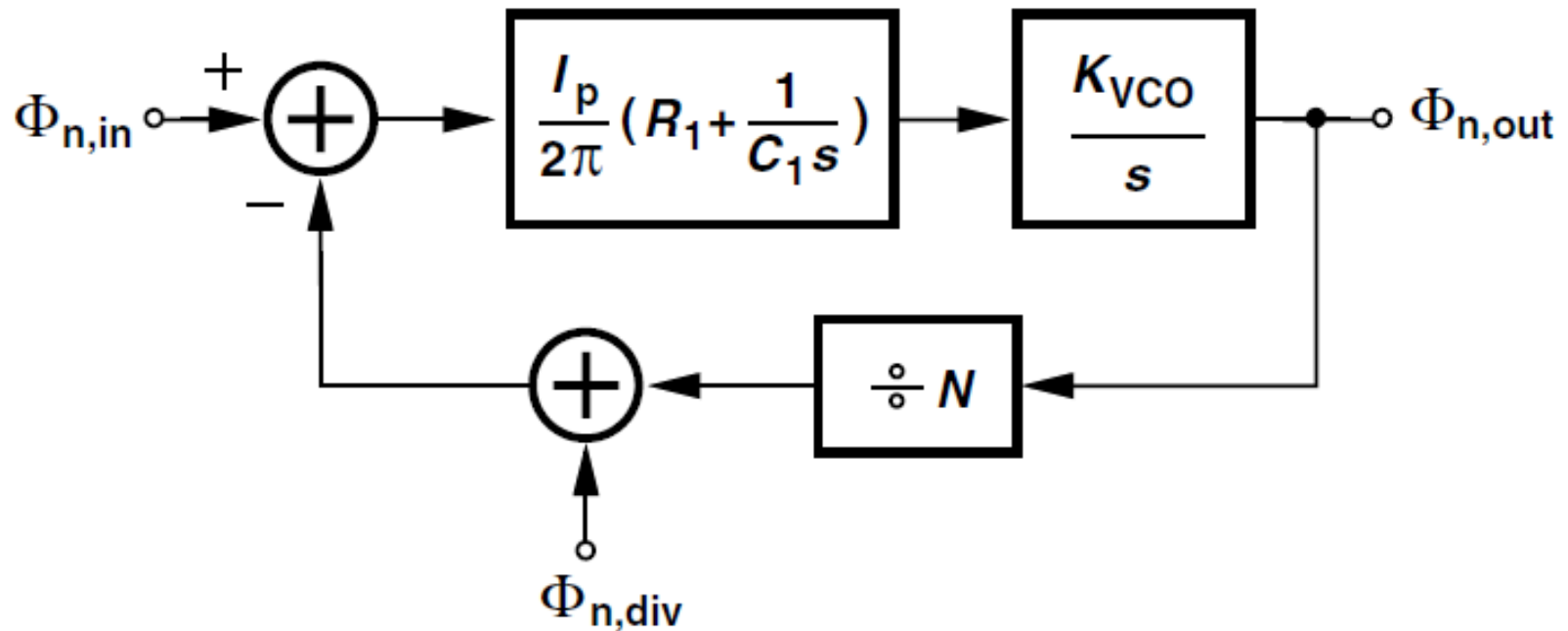

- The output phase noise of the divider, $\phi_{n,div}$, directly adds to the input phase noise, $\phi_{n,in}$, experiencing the same low-pass response as it propagates to ϕ_{out}

[B. Razavi, RF Microelectronics]



Divider Noise

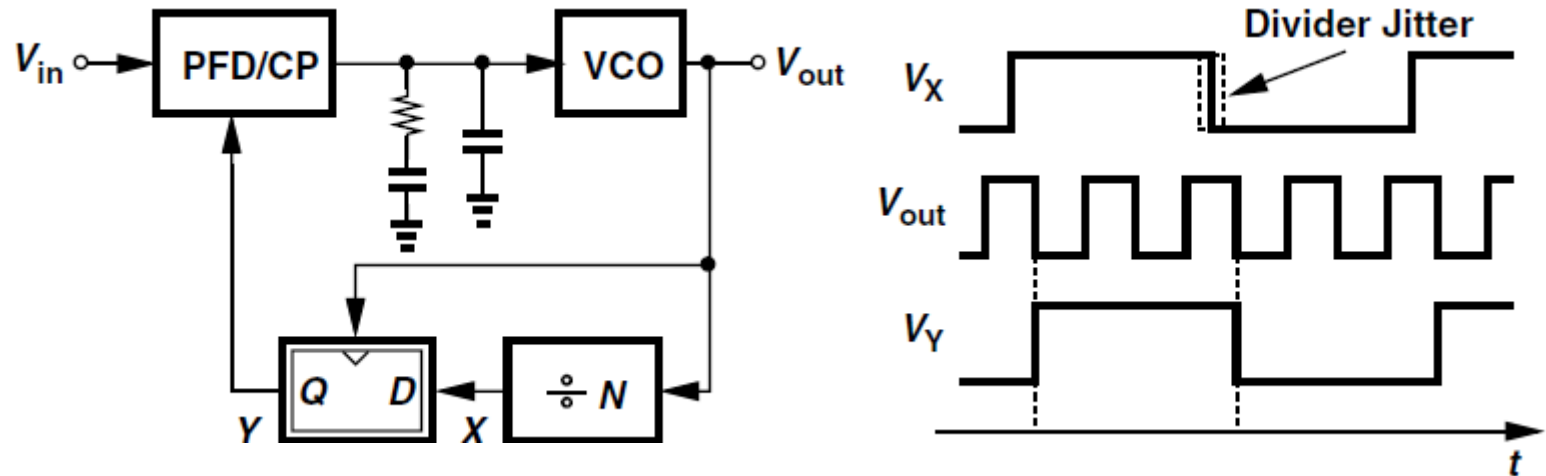

- ❑ A retiming flipflop can be used to suppress the divider noise
- ❑ The divider output is sampled by the VCO waveform, thus presenting the edges to the PFD only at the VCO transitions
- ❑ In essence, the retiming operation bypasses the phase noise accumulated in the divider chain

[B. Razavi, RF Microelectronics]


Metastability

 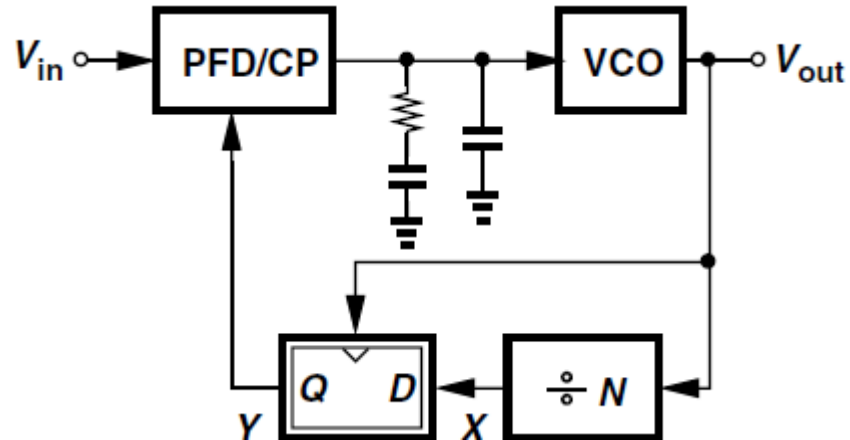

- ❑ If the VCO output edge occurs close to the transition at node X, the FF becomes “metastable,” i.e., it takes a long time to produce a well-defined logical level
- ❑ This effect results in a distorted transition at node Y, confusing the PFD.


[B. Razavi, RF Microelectronics]

Fractional Multiplication

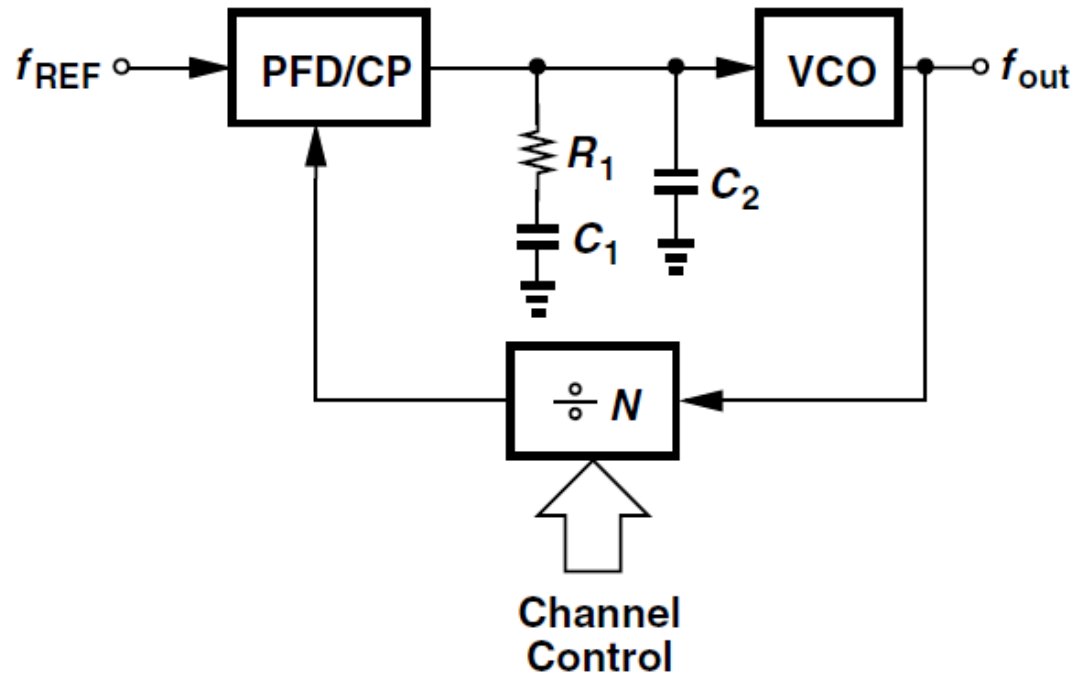

□ How to realize a fractional multiplication of f_{REF} ?


Fractional-N PLL

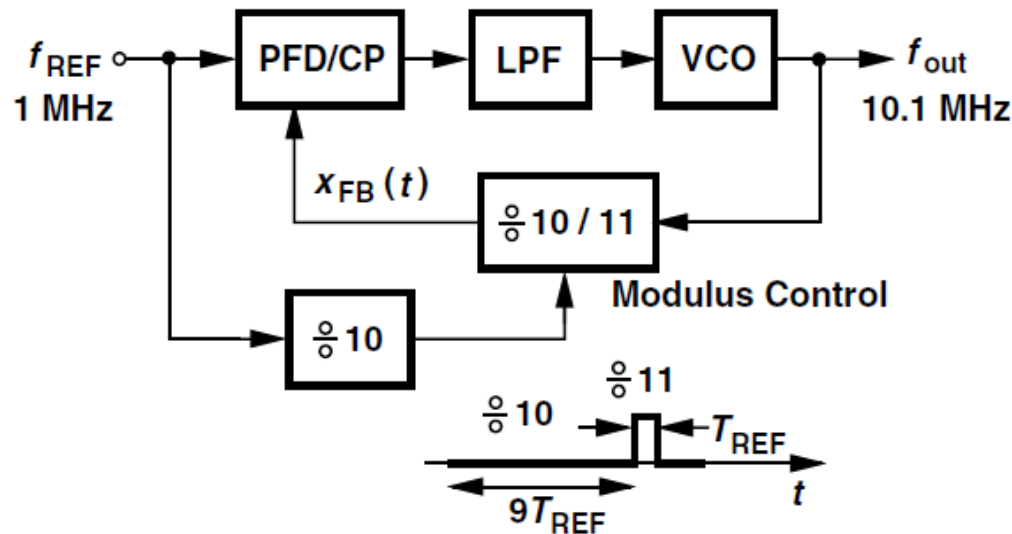

- ❑ Assume the prescaler divides by 10 for 90% of the time (nine reference cycles) and by 11 for 10% of the time,
- ❑ For every 10 reference cycles, the output produces $9 \times 10 + 11 = 101$ pulses, yielding an average divide ratio of 10.1
- ❑ If this operation is repeated, the PLL output contains many sidebands at integer multiples of 0.1 MHz (10 reference cycles)


[B. Razavi, RF Microelectronics]

Randomization

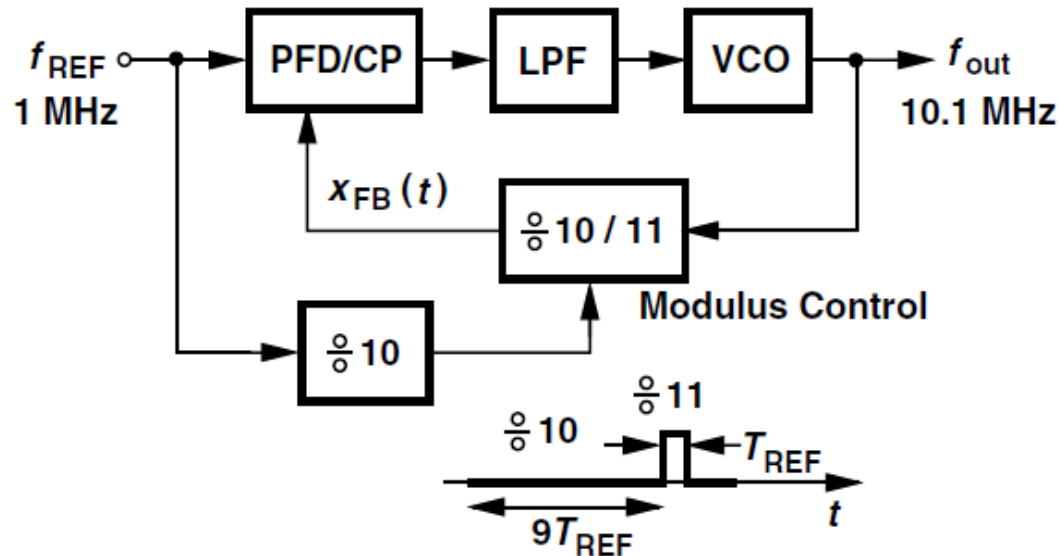

- ❑ If the divider modulus is randomly set to 10 or 11 but such that its average value is still 10.1
- ❑ Randomization of the modulus breaks the periodicity in the loop behavior, converting the spurs to noise

Quantization Noise

 


- ❑ Suppose the divider has two moduli, N and $N+1$, and must provide an average modulus of $N+\alpha$.
- ❑ We can write the instantaneous modulus as $N+b(t)$, where $b(t)$ randomly assumes a value of 0 or 1 and an average value of α .

$$f_{FB}(t) = \frac{f_{out}}{N + b(t)} \quad b(t) = \alpha + q(t)$$

- ❑ $q(t)$ the “quantization noise” because it denotes the error incurred by $b(t)$ in approximating the value of α


Modulus Randomization

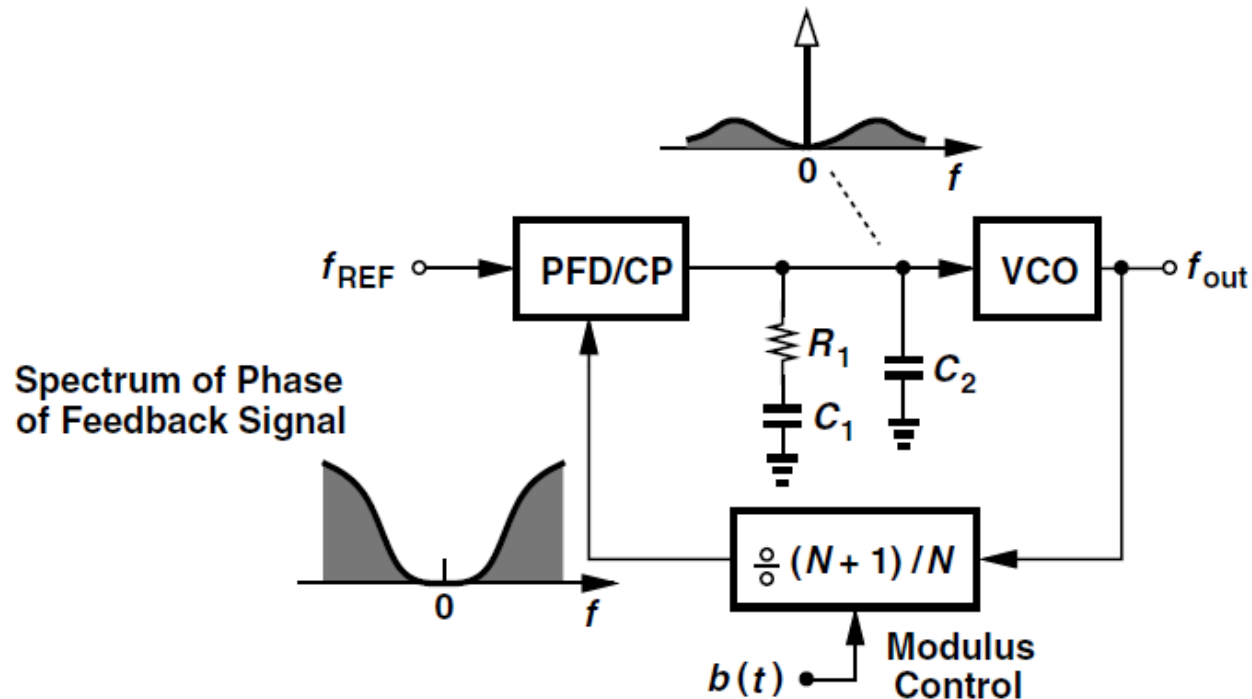

- ❑ Randomization can be performed such that the resulting phase noise exhibits a high-pass spectrum
- ❑ The generation of the sequence $b(t)$ so as to create a high-pass phase spectrum is called “noise shaping”

[B. Razavi, RF Microelectronics]

Transfer Function

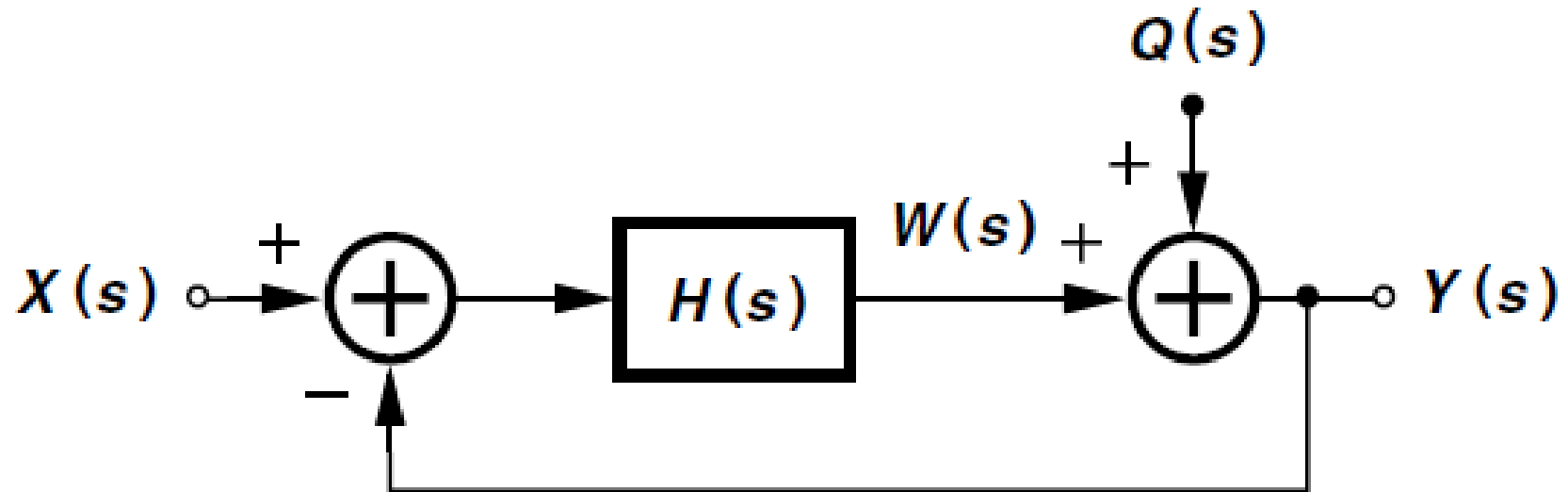


□ if $H(s)$ is an ideal integrator

$$\frac{Y(s)}{Q(s)} = \frac{1}{1 + H(s)} \quad \frac{Y(s)}{Q(s)} = \frac{s}{s + 1}$$

□ A negative feedback loop containing an integrator acts as a high-pass system on the noise injected “near” the output

Time Domain

 

- Recall from the definition of the z-transform that $z = \exp(j2\pi f T_{CK})$, where T_{CK} denotes the sampling or clock period
- At a given clock, $g(t)$ shows a high-pass versus the input $a(t)$


$$\frac{Y}{Q}(z) = 1 - z^{-1}$$

$$= e^{-j\pi f T_{CK}} (e^{j\pi f T_{CK}} - e^{-j\pi f T_{CK}})$$

$$= 2je^{-j\pi f T_{CK}} \sin(\pi f T_{CK})$$

$$S_y(f) = S_q(f) |2 \sin(\pi f T_{CK})|^2$$


$$= 2S_q(f) |1 - \cos(2\pi f T_{CK})|$$

 

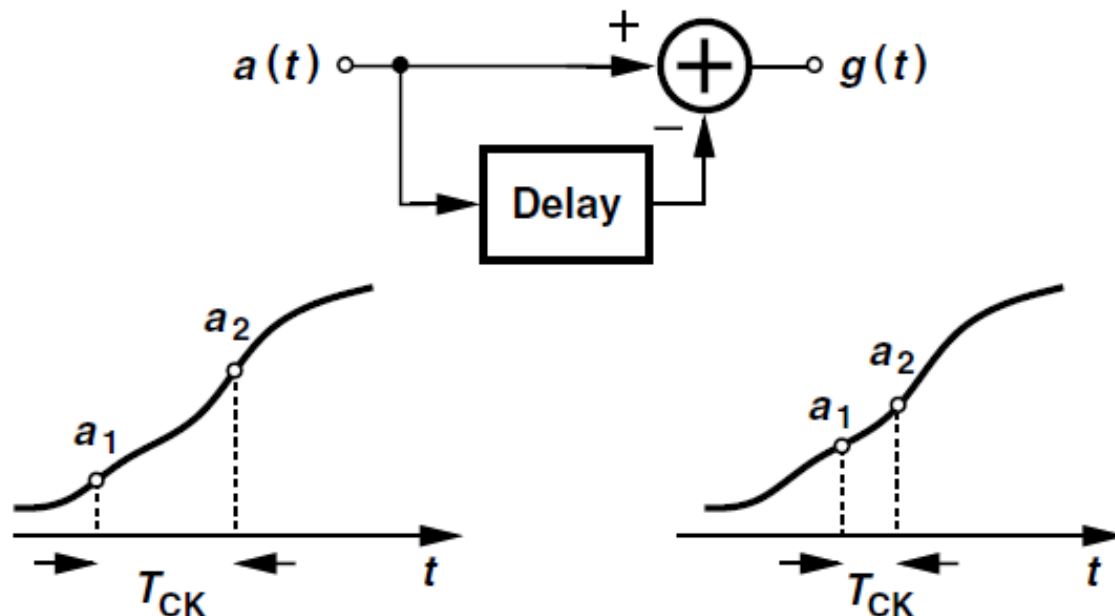[B. Razavi, RF Microelectronics]

Integrator


- Discrete-time integration can be realized by delaying the signal and adding the result to itself



- If the clock frequency increases, $a(t)$ finds less time to change, and a_1 and a_2 exhibit a small difference, so the high-frequency noise of clock can be rejected by a greater amount. [B. Razavi, RF Microelectronics]

$\Sigma\Delta$ Modulator

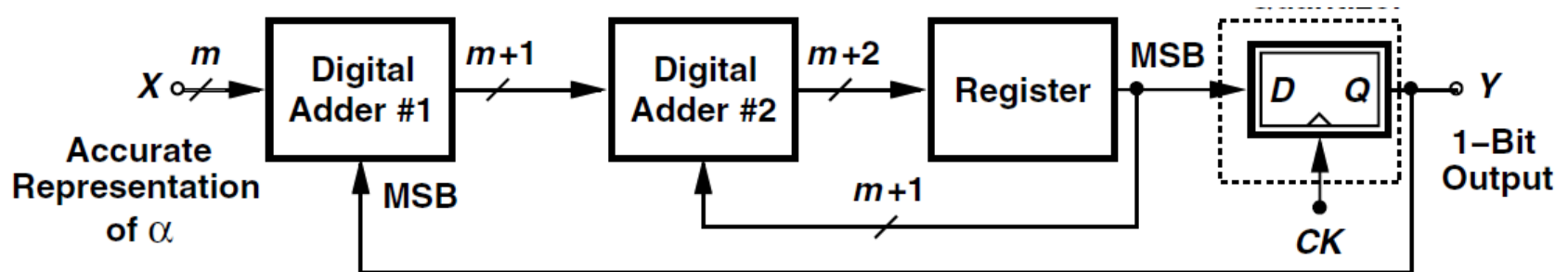□ $\Sigma\Delta$ modulator is constructed to produce a binary output with an average value of α and a shaped noise spectrum




□ The high-resolution output of the integrator drives a flipflop (i.e., a one-bit quantizer), thereby generating a single-bit binary stream at the output.

□ The quantization from $m+2$ bits to 1 bit introduces quantization noise, but the feedback loop shapes this noise in proportion to $1-z^{-1}$

[B. Razavi, RF Microelectronics]



$\Sigma\Delta$ PLL

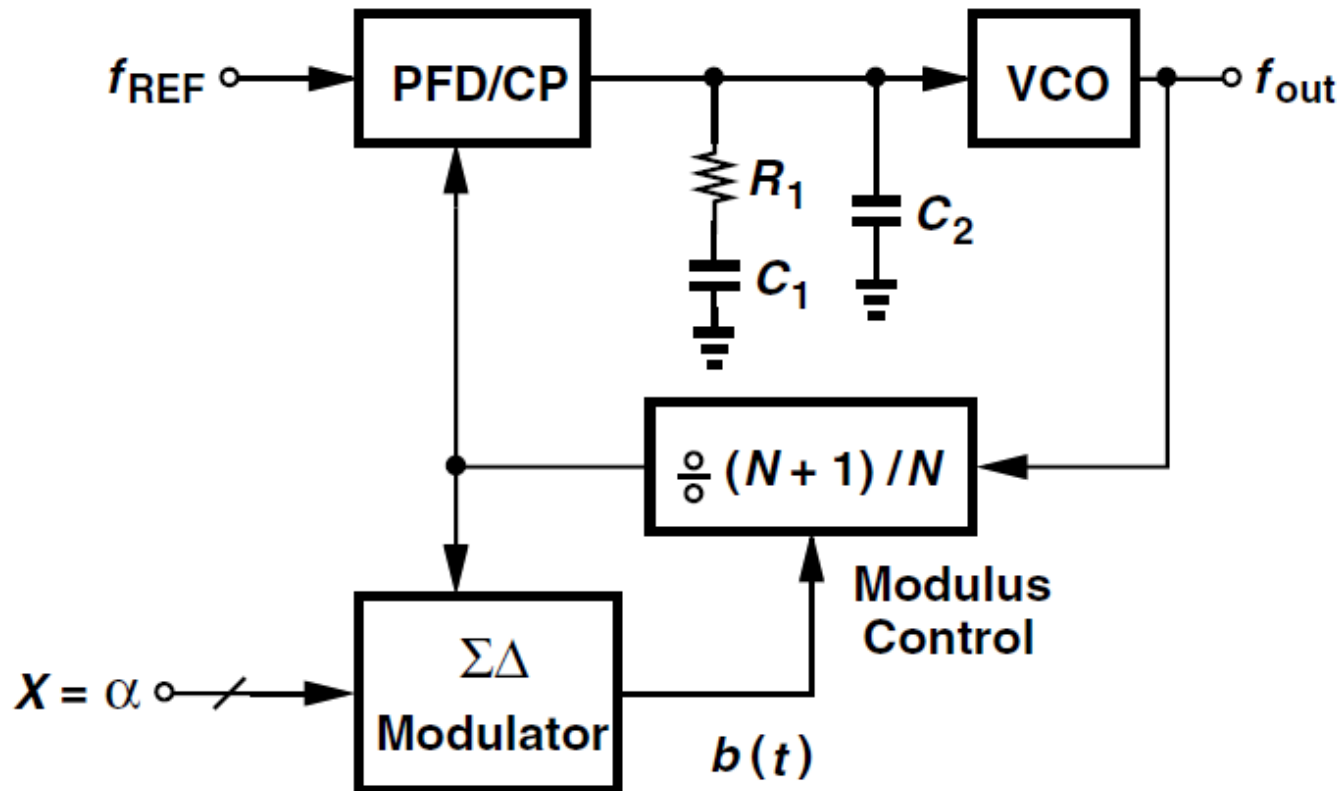

- Clocked by the feedback signal, the modulator toggles the divide ratio between N and $N+1$ so that the average is equal to $N+\alpha$.

[B. Razavi, RF Microelectronics]

Noise Shaping Order

  



$$\begin{aligned} S_y(f) &= S_q(f) |2 \sin(\pi f T_{CK})|^2 \\ &= 2S_q(f) |1 - \cos(2\pi f T_{CK})| \end{aligned}$$

If $f \ll (\pi T_{CK})^{-1}$

$$S_y(f) = S_q(f) |2\pi f T_{CK}|^2$$

- An integrator results in a 2nd-order roll-off in a PLL
- We therefore seek a system that exhibits a sharper roll-off, e.g., an output spectrum in proportion to f^n with $n > 2$

2nd-Order $\Sigma\Delta$ Modulator

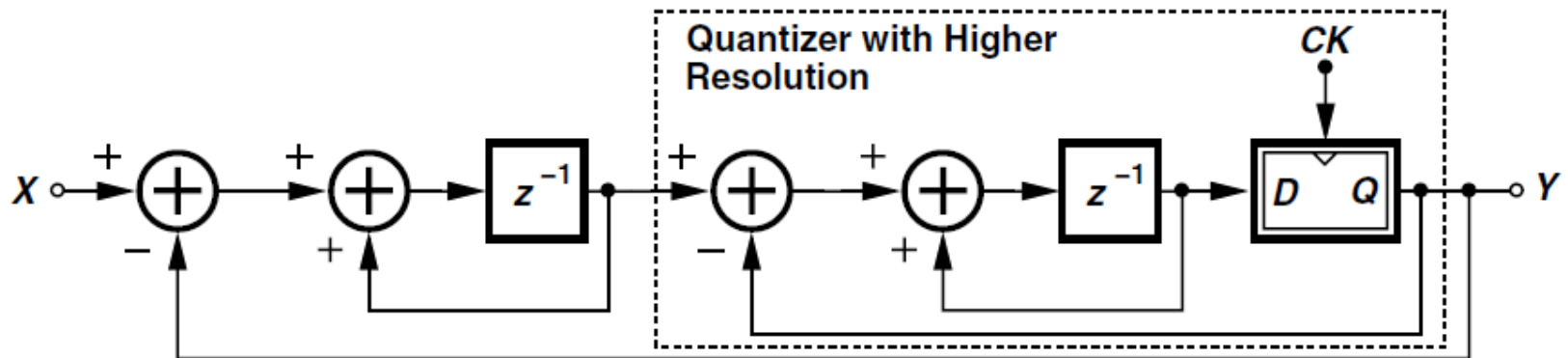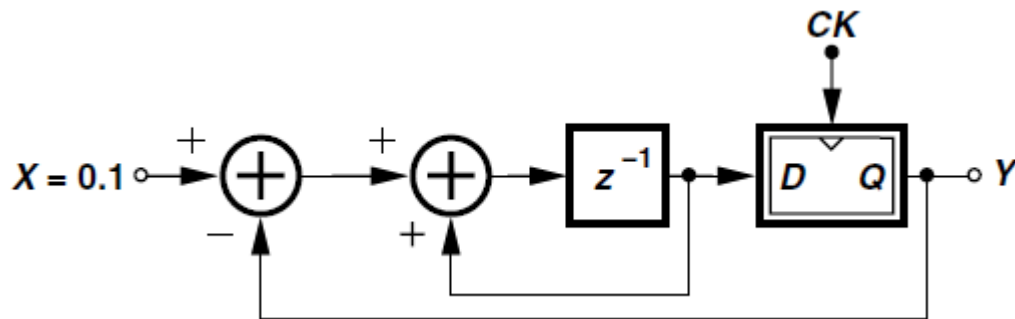

□ A $\Sigma\Delta$ modulator can suppress the quantization noise at low frequencies, we therefore replace the 1-bit quantizer with another $\Sigma\Delta$ modulator

[B. Razavi, RF Microelectronics]


 


Figure 10.10 is a plot of the output noise spectral density $S_y(f)$ versus frequency f . The y-axis is labeled $S_y(f)$ and has tick marks at 0.5, 4, and 16. The x-axis is labeled f and has tick marks at 0, $\frac{1}{6T_{CK}}$, and $\frac{1}{2T_{CK}}$. Two curves are shown: a solid curve labeled "Second-Order Noise Shaping" and a dashed curve labeled "First-Order Noise Shaping". Both curves start at (0,0). At $f = \frac{1}{6T_{CK}}$, both curves reach a value of 0.5. At $f = \frac{1}{2T_{CK}}$, the second-order curve reaches 16 and the first-order curve reaches 4. Dashed lines connect these points to the axes. An arrow points from the label "First-Order Noise Shaping" to its corresponding dashed curve.

- [B. Razavi, RF Microelectronics]**



Cascaded Modulator

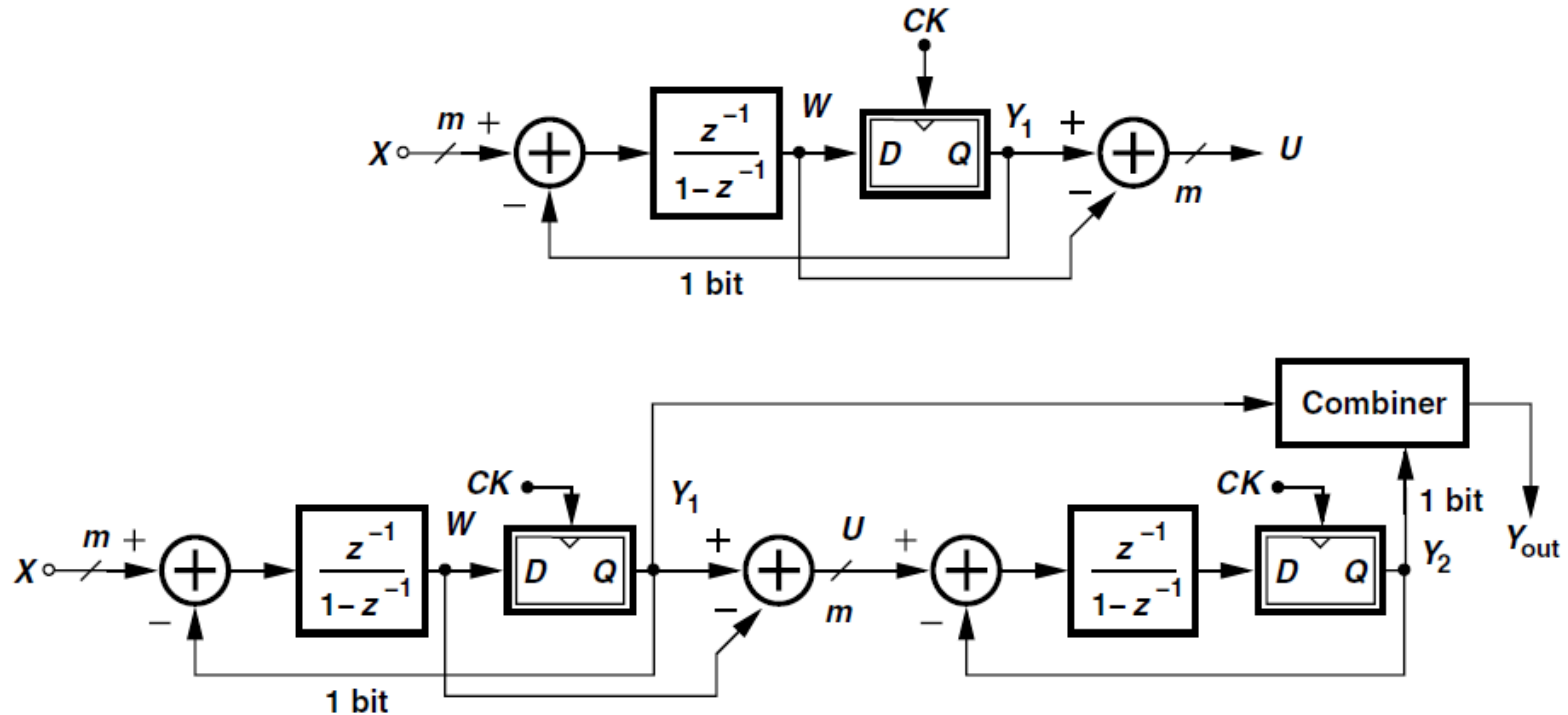

- $U = Y_1 - W = Q$ is the quantization error introduced by the first quantizer. Y_2 is a relatively accurate replica of U
- Y_2 is combined with Y_1 , yielding Y_{out} as a more accurate representation of X , achieving a 2nd-order modulator


[B. Razavi, RF Microelectronics]

Quantization Noise of PLL

  

□ There is peaking of the phase noise spectrum at a certain frequency.

Reconstruct Quantization Noise

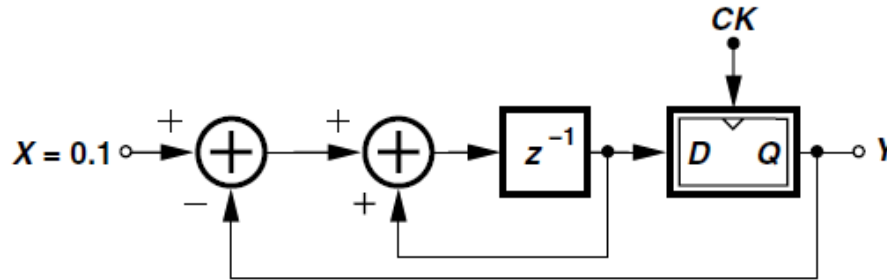


□ A first-order, one-bit modulator produces

$$Y(z) = z^{-1}X(z) + (1 - z^{-1})Q(z)$$

□ We delay $X(z)$ by one clock cycle and subtract the result from $Y(z)$ to reconstruct the quantization error:

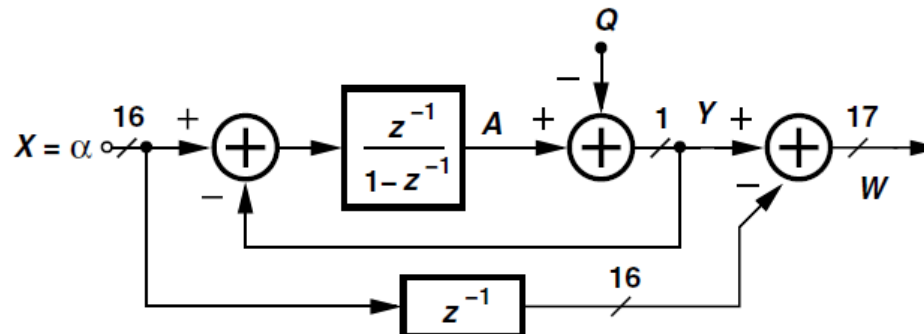
$$W(z) = Y(z) - z^{-1}X(z) = (1 - z^{-1})Q(z)$$



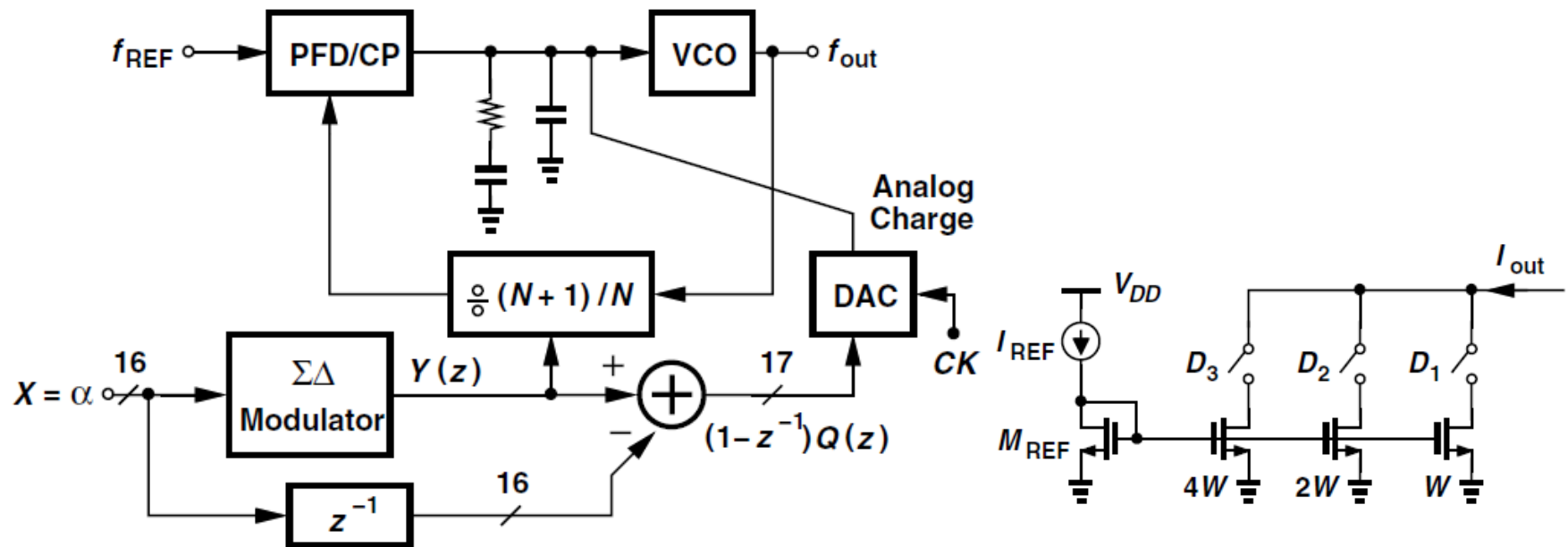[B. Razavi, RF Microelectronics]



DAC Forward Cancellation

- The output of $\Sigma\Delta$ modulator travels through the divider, the PFD, and the charge pump is met by the output of a DAC, facing perfect cancellation



[B. Razavi, RF Microelectronics]



Double-Edge-Triggered Flipflop

 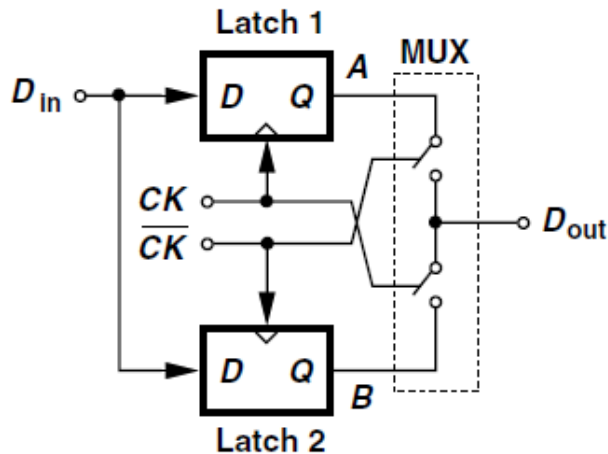

- When CK is high, the top latch is in the sense mode and the bottom latch in the hold mode, and vice versa
- For a given clock rate, the input data can be twice as fast as that applied to a single-edge-triggered counterpart

[B. Razavi, RF Microelectronics]


Fractional Divider

  

- ❑ With the double-edge-triggered flipflops, the $\div 3$ divider can realize a divide-by-1.5 circuit
- ❑ The fractional divider can replace the $\Sigma\Delta$ modulator in some case to avoid the quantization noise

[B. Razavi, RF Microelectronics]

Reference Doubling

 


- ❑ The noise shaping function indicates a direct dependence on the clock frequency

$$S_y(f) = S_q(f) |2\pi f T_{CK}|^2$$


- ❑ If T_{CK} is halved, the noise power falls by 6 dB

 - ❑ However, a crystal oscillator can only provide a reference frequency less than 100 MHz



[B. Razavi, RF Microelectronics]


Multiphase Frequency Division

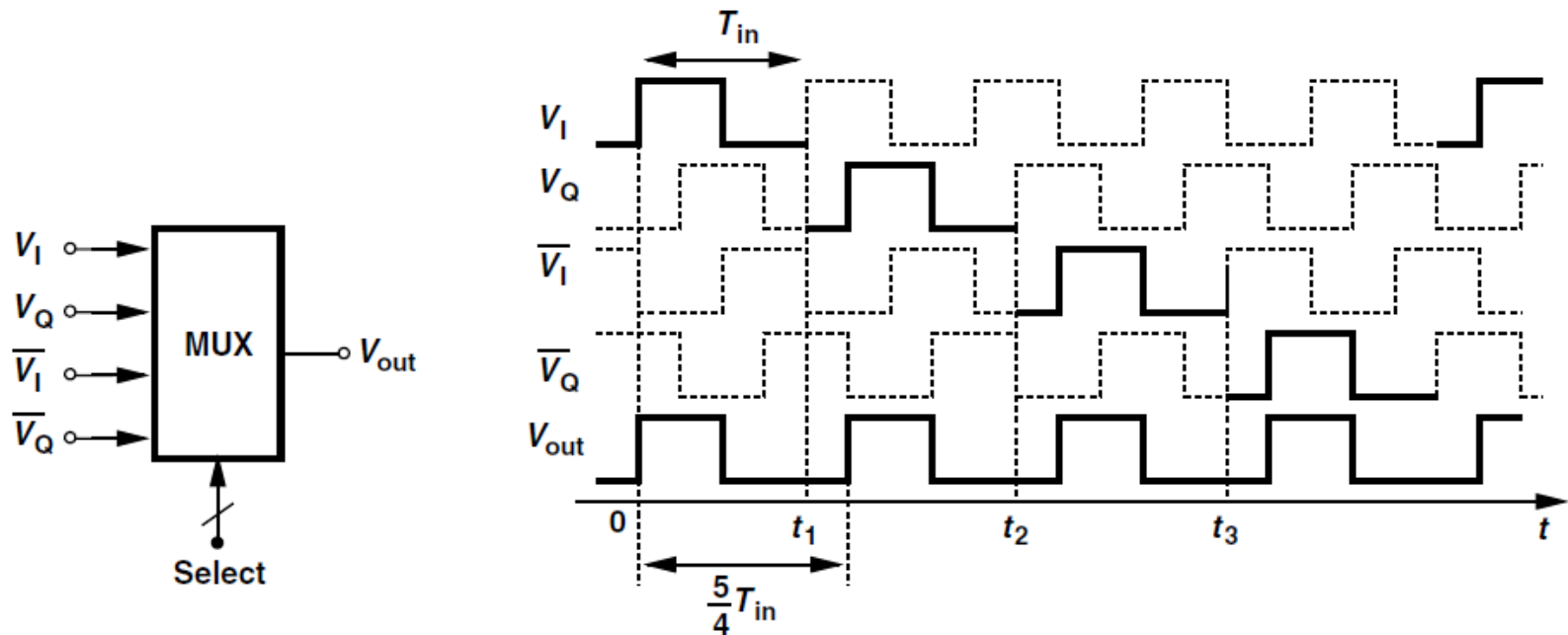

- The VCO is designed to generate multiple phases at the output
- The I and Q are picked out to realize a divide-by-1.25 operation

[B. Razavi, RF Microelectronics]

Multiphase Frequency Division

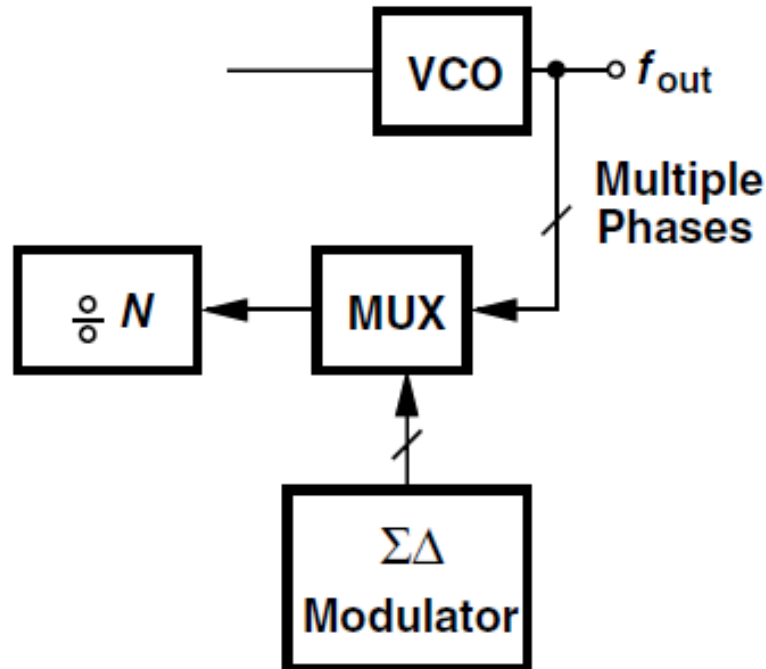

□ A $\Sigma\Delta$ modulator is adopted to randomize selection of the VCO phases

- This randomization can also incorporate noise shaping
- The multiplexing of the VCO phases can be placed after the feedback divider to make the MUX easier to design

[B. Razavi, RF Microelectronics]