



RF circuits and systems

Project Report

实验名称 Receiver Link Design

姓 名 LuZexi

学 号 3220102478

实验日期 January 10, 2025


指导老师 Zhao Bo

Contents

Contents	1
1 Requirements	1
2 Simulation Process	1
2.1 Schematic Diagram	1
2.2 Circuit Parameters	1
2.3 Simulation Settings	3
3 Simulation Results	5
4 Theoretical Calculation	6
5 Summery	7

1 Requirements

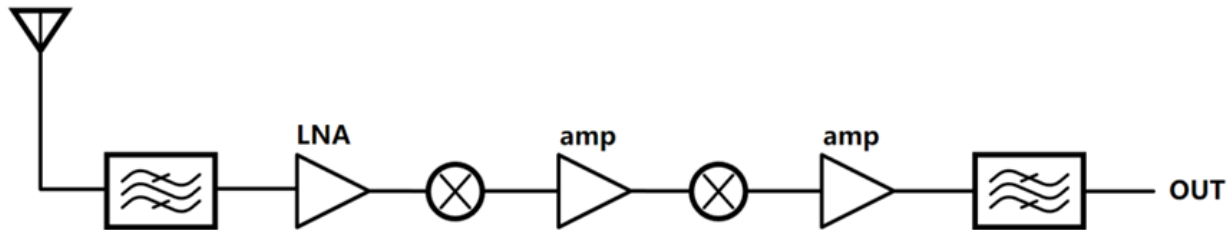Using ADS software to build a receiver link in the frequency of **2478 MHz** band, and the power of input signal is -60 dBm. The system block diagram is as follows. Finish the calculation and simulation of the **Power, Gain, Output Power** and **Sensitivity**.




The parameters of Antenna, RF Filter, LNA, Amp, Mixer are as follows.

Antenna	Input Impedance : 50ohm		
RF Filter	Bandwidth: 2MHz, Insert Loss: 1.5dB, N:5		
	Power (mW)	Noise Figure (dB)	Gain (dB)
LNA	1.8	2	16
Mixer	0	19	-4
Amp	1	9	20
	Center Frequency (MHz)	Bandwidth (MHz)	Insert Loss (dB)
Low Frequency Filter	2	1	2

2 Simulation Process

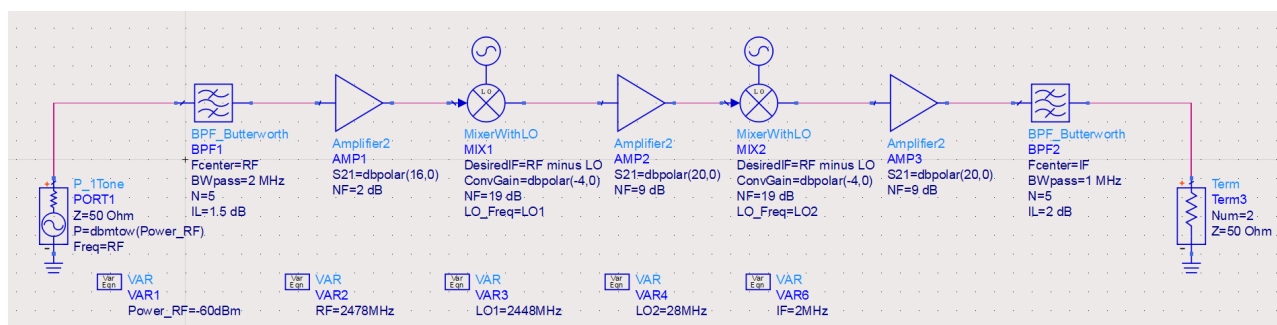2.1 Schematic Diagram

According to the requirements, we can have the schematic shown below.



2.2 Circuit Parameters

Second, we need to determine the parameters of each circuit according to the requirements.

Library name: ads_simulation
 Cell name: P_1Tone
 View name: symbol
 Instance name: PORT1

Select Parameter

- Num=1
- Z=50 Ohm
- P=dbmtow(Power_RF)
- Freq=RF
- PhaseNoise=
- P_USB=
- P_LSB=
- Mod=
- Noise=yes
- Pac=polar(dbmtow(0,0))
- FundIndex=
- Vdc=

Num (Integer, e.g. 1) None

Equation Editor...
 Tune/Opt/Stat/DOE Setup...

☐ Display parameter on schematic

Add Cut Paste Component Options... Reset

Num:Port number

OK Apply Cancel Help

Library name: ads_behavioral
 Cell name: Amplifier2
 View name: symbol
 Instance name: AMP1

Select Parameter

- S21=dbpolar(16,0)
- S11=polar(0,0)
- S22=polar(0,180)
- S12=0
- NF=2 dB
- NFmin=
- Sopt=
- Rn=
- Z1=
- Z2=
- GainCompType=LIST
- GainCompFreq=

Parameter Entry Mode
 Standard

S21
 dbpolar(16,0) None

Equation Editor...
 Tune/Opt/Stat/DOE Setup...

☒ Display parameter on schematic

Add Cut Paste Component Options... Reset

S21:Forward Transmission Coefficient, use x*tj*y, polar(x,y), dbpolar(x,y) for complex value

OK Apply Cancel Help

Library name: ads_behavioral
 Cell name: BPF_Butterworth
 View name: symbol
 Instance name: BPF1

Select Parameter

- Fcenter=RF
- BWpass=2 MHz
- Apass=3.0103 dB
- BWstop=10 MHz
- Astop=20 dB
- StopType=open
- MaxRej=
- N=5
- IL=1.5 dB
- Qu=1E308
- Z1=50 Ohm
- Z2=50 Ohm

Parameter Entry Mode
 Standard

Fcenter
 RF None

Equation Editor...
 Tune/Opt/Stat/DOE Setup...

☒ Display parameter on schematic

Add Cut Paste Component Options... Reset

Fcenter:Passband Center Frequency

OK Apply Cancel Help

Library name: ads_behavioral
 Cell name: BPF_Butterworth
 View name: symbol
 Instance name: BPF2

Select Parameter

- Fcenter=IF
- BWpass=1 MHz
- Apass=3.0103 dB
- BWstop=5 MHz
- Astop=20 dB
- StopType=open
- MaxRej=
- N=5
- IL=2 dB
- Qu=1E308
- Z1=50 Ohm
- Z2=50 Ohm

Parameter Entry Mode
 Standard

Fcenter
 IF None

Equation Editor...
 Tune/Opt/Stat/DOE Setup...

☒ Display parameter on schematic

Add Cut Paste Component Options... Reset

Fcenter:Passband Center Frequency

OK Apply Cancel Help

Library name: ads_simulation
 Cell name: MixerWithLO
 View name: symbol
 Instance name: MIX1

Select Parameter

- ZRef=50 Ohm
- DesiredIF=RF minus LO
- ConvGain=dbpolar(-4,0)
- SP11=polar(0,0)
- SP22=polar(0,180)
- NF=19 dB
- ReferToInput=OUTPUT
- SOI=1000
- TOI=1000
- LO_Freq=LO1

Parameter Entry Mode
 Standard

ZRef
 50 Ohm

Equation Editor...
 Tune/Opt/Stat/DOE Setup...

☐ Display parameter on schematic

Add Cut Paste Component Options... Reset

ZRef:Reference resistance for all Ports

OK Apply Cancel Help

Library name: ads_simulation
 Cell name: MixerWithLO
 View name: symbol
 Instance name: MIX2

Select Parameter

- ZRef=50 Ohm
- DesiredIF=RF minus LO
- ConvGain=dbpolar(-4,0)
- SP11=polar(0,0)
- SP22=polar(0,180)
- NF=19 dB
- ReferToInput=OUTPUT
- SOI=1000
- TOI=1000
- LO_Freq=LO2

Parameter Entry Mode
 Standard

ZRef
 50 Ohm


Equation Editor...
 Tune/Opt/Stat/DOE Setup...

☐ Display parameter on schematic

Add Cut Paste Component Options... Reset

ZRef:Reference resistance for all Ports

OK Apply Cancel Help

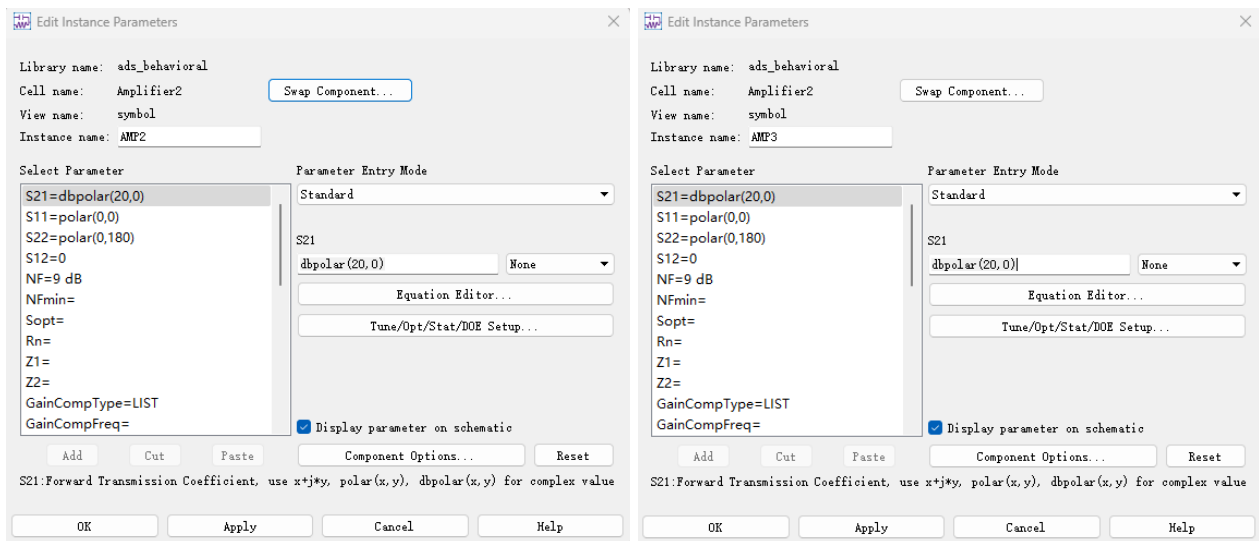

We have to note that

- PORT1 refers to the antenna;
- AMP1 refers to the low noise amplifier;
- BPF1 refers to the RF filter and BPF2 refers to the low pass filter;
- MIX1 refers to the first mixer and MIX2 refers to the second mixer;
- AMP2 refers to the first power amplifier and AMP3 refers to the second power amplifier.

Since the receiver is two-stage heterodyne architecture, where the first down-converting frequency is provided by a PLL working at 2448 MHz, so we can calculate that the LO2 frequency is

$$f_{LO2} = f_{RF} - f_{LO1} - f_{IF} = 2478 - 2448 - 2 = 28 \text{ MHz}$$

2.3 Simulation Settings

Finally we select Budget as the simulation tool. Output of Budget include

- Cmp_NF_dB (NF of each stage)
- Cmp_S21_dB (Gain of each stage)
- NF_Refln_Nolmage_dB (system noise figure)
- OutPwr_dBm (output power)
- OutPGain_dB (system Gain)
- InFreq (frequency)

The parameters are shown below.

Budget Simulation:1

ads_simulation:Budget Instance Name
Budget

Setup Measurements Display

Simulation

Nonlinear Analysis

☒ Enable nonlinear analysis

Harmonic order 3

Max. component input power (dBm) 50_dBm

Noise Simulation

Frequency span 1 MHz

Frequency step 100 kHz

Frequency points 11

Resolution bandwidth 1 Hz

Results

Components in ☐ Rows ☒ Columns

Angle unit ☒ degrees ☐ radians

Frequency unit Hz

☒ Auto format display with overwrite

☐ Output results as comma separated values (CSV) to file

☐ Run command after analysis

System command

OK Apply Cancel Help

Budget Simulation:1

ads_simulation:Budget Instance Name
Budget

Setup Measurements Display

Recall selected measurements from file

Available Measurements

Cmp_Ctrb_SysNF_dB
Cmp_Ctrb_SysTOI_dB
Cmp_LS_GainChange_dB
Cmp_OutN0_dBm
Cmp_OutP1dB_dBm
Cmp_OutSOI_dBm
Cmp_OutTOI_dBm
Cmp_S11_dB
Cmp_S11_mag

>>Add>>
<<Delete<<

Selected Measurements

Cmp_NF_dB
Cmp_S21_dB
NF_Refln_NoImage_dB
OutPwr_dBm
OutPGain_dB
InFreq


Raise Lower

Description

Cmp_Ctrb_SysNF_NoImage_dB:
System noise figure improvement if component
contributes no noise; excludes system image noise

Save selected measurements to file

OK Apply Cancel Help

 **BUDGET**

Budget
Budget


NonlinearAnalysis=yes
NonlinearHarmonicOrder=3
CmpMaxPin=50_dBm
NoiseFreqSpan=1 MHz
NoiseFreqStep=100 kHz
NoiseResolutionBW=1 Hz
TableComponentFormat=Columns
MeasurementFrequencyUnit=Hz
MeasurementAngleUnit=degrees
AutoFormatDisplay=yes
OutputCSVFile=no
RunCommand=no
SystemCommand=
Measurement[1]="Cmp_NF_dB"
Measurement[2]="Cmp_S21_dB"
Measurement[3]="NF_Refln_NoImage_dB"
Measurement[4]="OutPwr_dBm"
Measurement[5]="OutPGain_dB"
Measurement[6]="InFreq"

3 Simulation Results

Simulation results are shown below

Meas_Name	BPF1	AMP1	MIX1	AMP2	MIX2
Cmp_NF_dB	1.500	2.000	19.000	9.000	19.000
Cmp_S21_dB	-1.500	16.000	-4.000	20.000	-4.000
NF_Refin_NoImage_dB	1.500	3.500	7.008	7.513	7.567
OutPwr_dBm	-61.500	-45.500	-49.500	-29.500	-33.500
OutPGain_dB	-1.500	14.500	10.500	30.500	26.500
InFreq	2.478E9	2.478E9	2.478E9	3.000E7	3.000E7

AMP3	BPF2
9.000	2.000
20.000	-2.000
7.578	7.578
-13.500	-15.500
46.500	44.500
2.000E6	2.000E6

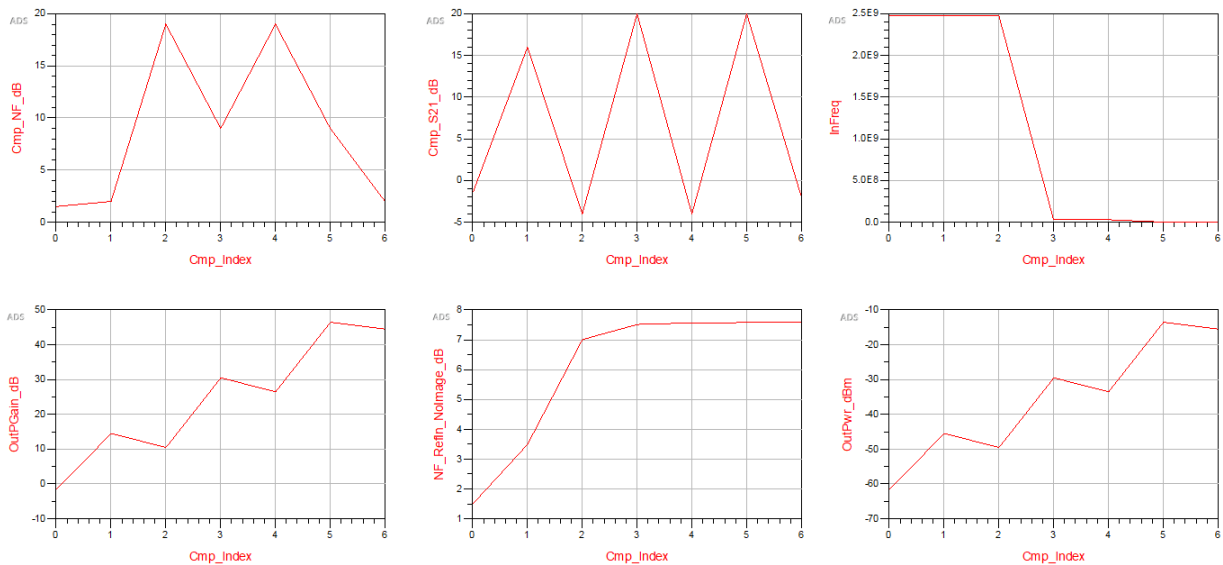

We can get some system information according to the simulation results. The final output IF signal

RESULTS	Output Power	OUTPUT Freq	Total Gain	Total Noise
VALUE	-15.5dBm	2MHz	44.5dB	7.578dB

Table 1: System Output

frequency is 2 MHz, which meets expectations, indicating a successful simulation.

Based on the result curves, we can also verify some conclusions from the classroom:

- (1). The NF curve increases, indicating that circuit components inevitably introduce noise. No matter how superior the components are, noise cannot be completely eliminated.
- (2). Power amplifiers and LNAs are active components, so the signal power increases as it passes through them. However, the mixer here is passive, which results in a decrease in signal power.
- (3). The RF receiver converts high-frequency signals into low-frequency signals, leading to a decrease in signal frequency.

4 Theoretical Calculation

Question.1. Calculate the **Noise Figure** of the receiver system, then compare the calculation results with the simulation results.

Soln. We can use the equation

$$NF_{tot} = NF_1 + \frac{NF_2 - 1}{G_1} + \dots + \frac{NF_m - 1}{G_1 \dots G_{m-1}}$$

Substitute all the data we can obtain

$$NF_{tot} = 10 \lg(10^{0.15} + \frac{10^{0.2} - 1}{10^{-0.15}} + \frac{10^{1.9} - 1}{10^{1.45}} + \frac{10^{0.9} - 1}{10^{1.05}} + \frac{10^{1.9} - 1}{10^{3.25}} + \frac{10^{0.9} - 1}{10^{2.85}} + \frac{10^{0.2} - 1}{10^{4.85}}) = 7.578dB$$

RESULTS	RF Filter	LNA	MIX1	AMP1	MIX2	AMP2	LPF
NF dB	1.5	3.5	7.01	7.514	7.567	7.578	7.578

Table 2: NF calculation results of all circuits

Compare the simulation results with calculation results, we can see that they are almost the same, so the simulation is correct.

Question.2. Calculate the **Output Power** of the receiver system, then compare the calculation results with the simulation results.

Soln. We can use the equation

$$G = G_1 \times G_2 \times \dots G_m = \sum G|dB = -1.5 + 16 - 4 \times 2 + 20 \times 2 - 2 = 44.5dB$$

So we can obtain

$$P_{out} = G \times P_{in}, \quad 10 \lg \frac{P_{out}}{1mW} = 10 \lg G + 10 \lg \frac{P_{in}}{1mW} = 44.5 + (-60) = -15.5dBm$$

Compare the simulation results with calculation results, we can see that they are almost the same, so the simulation is correct.

Question.3. Assume the **minimum input SNR** of demodulator is **12 dB** and the input Bandwidth is **2 MHz**. At temperature of 290k, noise power of 1 Hz bandwidth is **-174 dBm**, judge the **Sensitivity** of the system.

Soln.

$$Sen = -174dBm + NF|dB + SNR_{min} + 10\lg B = -174 + 7.578 + 12 + 10\lg(2 \times 10^6) = -91.412dB$$

5 Summery

The simulation and theoretical analysis of the receiver link design were successfully completed using ADS software. The simulation involved constructing a two-stage heterodyne receiver operating at a frequency of 2478 MHz with an input signal power of -60 dBm. The system components, including the antenna, RF filter, low noise amplifier (LNA), mixers, and power amplifiers, were carefully selected and their parameters determined based on design requirements. The theoretical calculations for noise figure, gain, output power, and sensitivity closely matched the simulation results, validating the accuracy of the simulation model. Overall, the simulation successfully demonstrated the design's performance, verifying both theoretical principles and practical results. This project has deepened my understanding of RF circuit design and the importance of careful component selection and simulation accuracy in achieving reliable results.