

# Frequency Synthesizers (1/2)

**ZHAO BO**

**Institute of VLSI Design**


**Zhejiang University**

**Email: [zhaobo@zju.edu.cn](mailto:zhaobo@zju.edu.cn)**

**Web: [person.zju.edu.cn/zhaobo](http://person.zju.edu.cn/zhaobo)**

# Channel Selection

---

 


- ❑ For example, Bluetooth has 80 1-MHz channels in the range of 2.400 GHz to 2.480 GHz.
- ❑ For each channel, the corresponding frequency is allocated to the user, requiring that the LO frequency be set by a frequency synthesizer.

[B. Razavi, RF Microelectronics]

# LO Frequency Error

---

 


- ❑ Narrow, tightly-spaced channels in wireless standards tolerate little error in transmit and receive carrier frequencies
- ❑ A slight shift leads to significant spillage of a high-power interferer into a desired channel.

[B. Razavi, RF Microelectronics]

# Conceptual Picture


---

 

□ The output frequency is generated as a multiple of a precise reference,  $f_{\text{REF}}$ , and this multiple is changed by the channel selection command so as to cover the carrier frequencies required by the standard

[B. Razavi, *RF Microelectronics*]


# Reciprocal Mixing

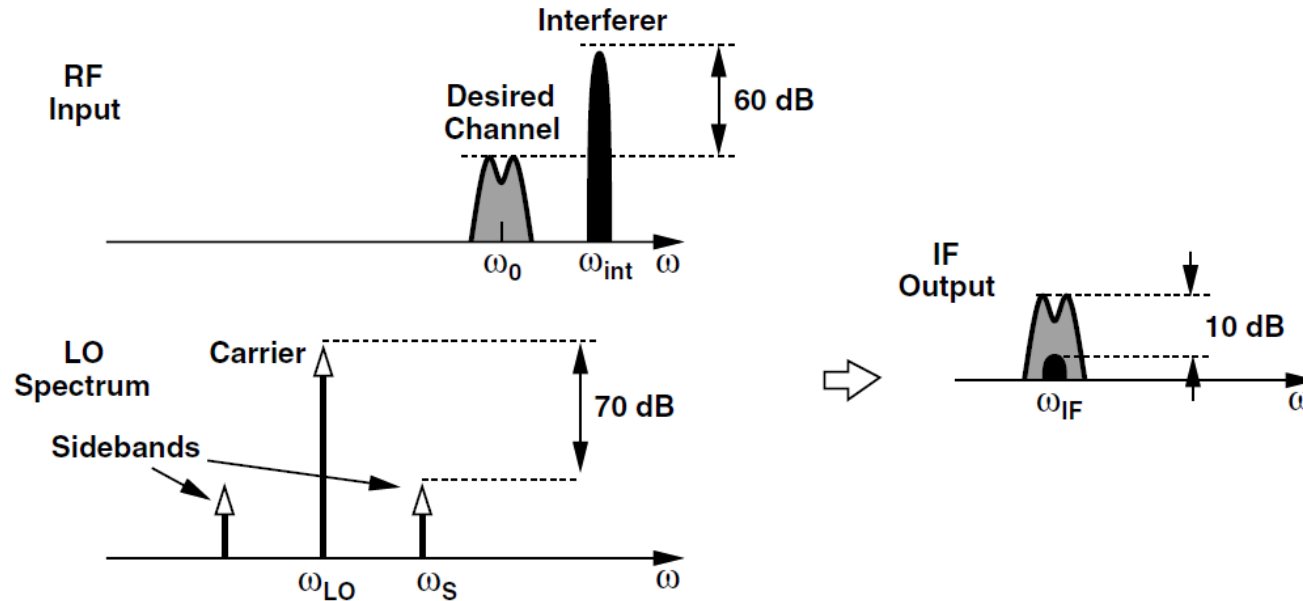

- ❑ If the control voltage of a VCO is periodically disturbed, then the output spectrum contains sidebands symmetrically disposed around the carrier (spurs)
- ❑ Upon downconversion mixing, the desired channel is convolved with the carrier and the interferer with the sideband

[B. Razavi, RF Microelectronics]

# Frequency Settling

 


- When the digital channel selection command changes value, the synthesizer takes a finite time to settle to a new output frequency, which is called the “lock time”
- This settling time directly determines the channel switching time of a transmitter or receiver

[B. Razavi, RF Microelectronics]

# Integer-N Frequency Synthesizer


---

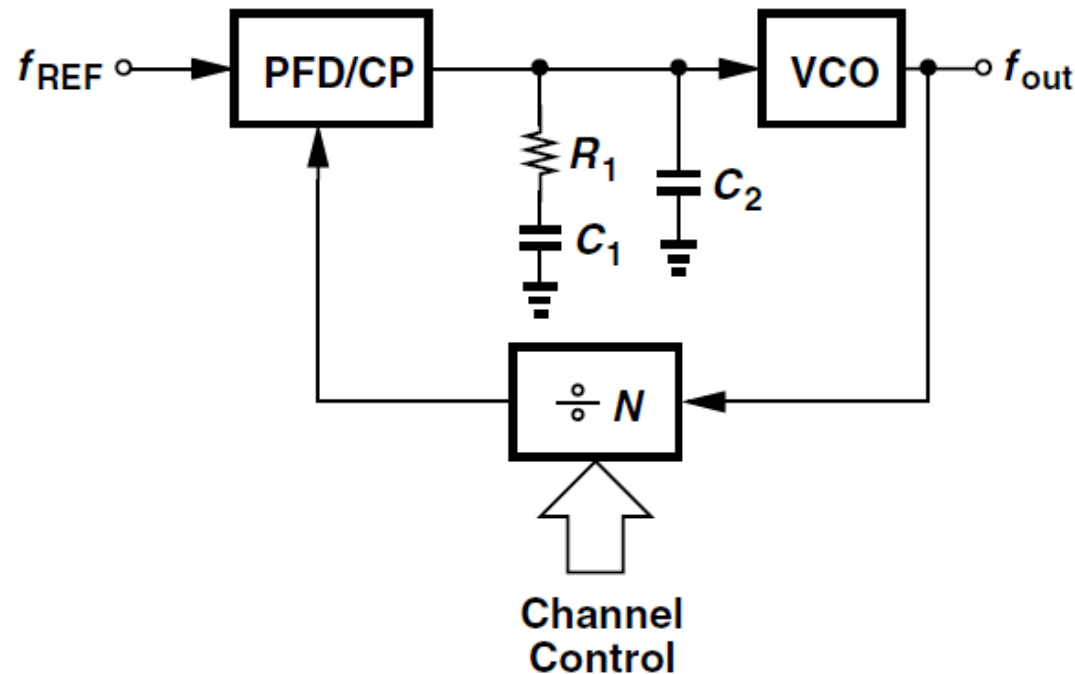

- ❑ Integer-N synthesizers produce an output frequency that is an integer multiple of the reference frequency
- ❑ If  $N$  increases by 1, then  $f_{out}$  increases by  $f_{REF}$ ; i.e., the minimum channel spacing is equal to the reference frequency

[B. Razavi, RF Microelectronics]

# Integer-N Frequency Synthesizer

 


- ❑ The principal drawback of the integer-N architecture is that the channel spacing is equal to the reference frequency
- ❑ A rule of thumb for the settling of PLLs is 100 times the reference period
- ❑ The lock time ( $\approx 100$  input cycles) and the loop bandwidth are tightly related to the channel spacing

[B. Razavi, RF Microelectronics]



# Charge Injection/Clock Feedthrough

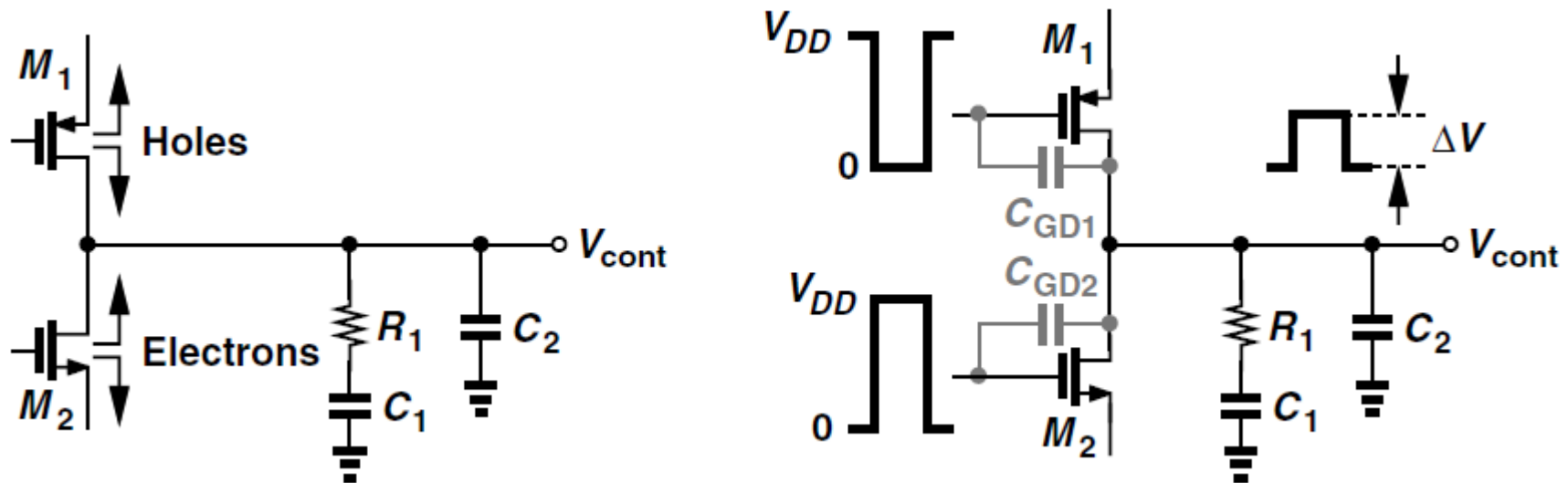


□ As the switches turn on, they absorb this charge and as they turn off, they dispel this charge, in both cases through their source and drain terminals

□ The clock feedthrough relates to the gate-drain overlap capacitance of the switches

[B. Razavi, RF Microelectronics]

# Spurs

 


- ❑ The issues such as charge sharing, channel length modulation, and Up and Down current mismatch lead to spurs
- ❑ There is trade-off between the loop bandwidth and the level of reference spurs

[B. Razavi, RF Microelectronics]
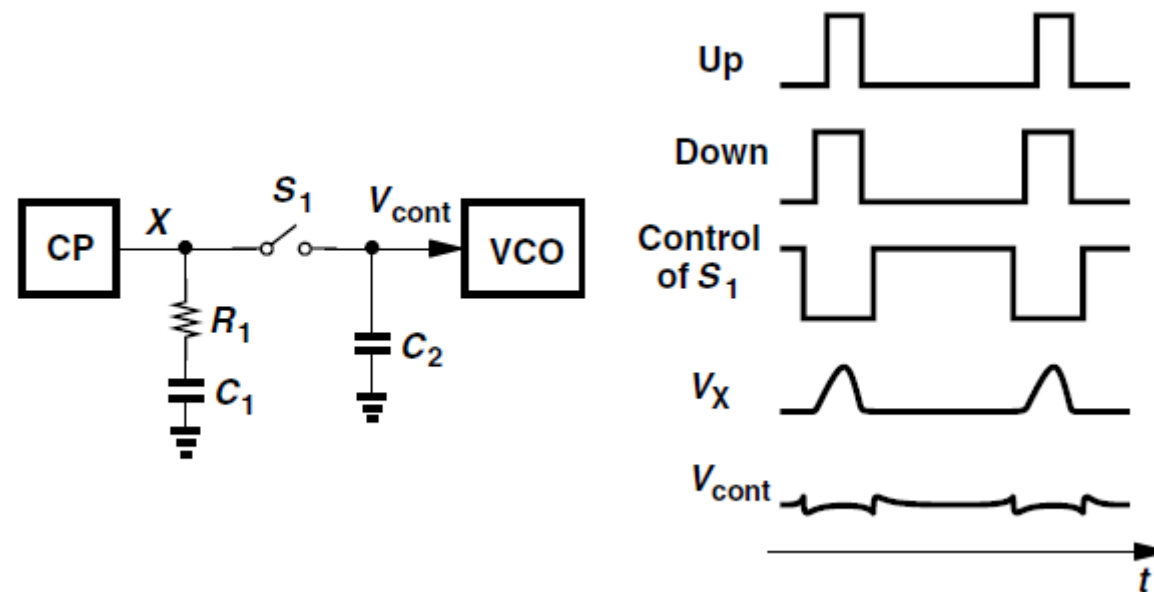
# Spur Reduction


- A key point in devising spur reduction techniques is that the disturbance of the control voltage occurs primarily at the phase comparison instant
- We therefore surmise that the output sidebands (spurs) can be lowered if  $V_{\text{cont}}$  is isolated from the disturbance for that duration



[B. Razavi, RF Microelectronics]
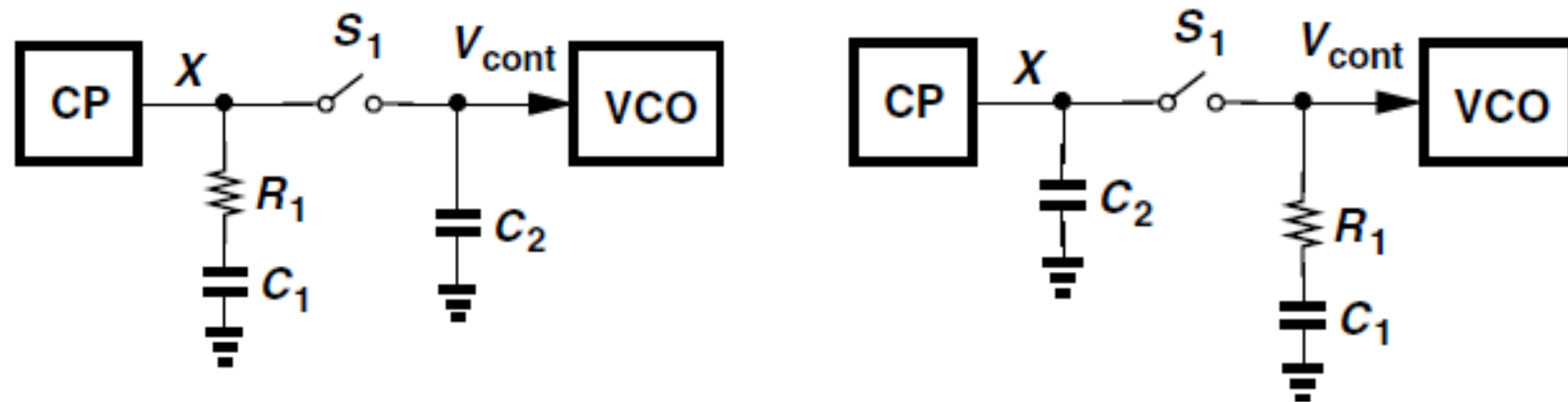
# Spur Reduction


- ❑ Unfortunately, the isolation of  $V_{\text{cont}}$  from the disturbance also eliminates the role of  $R_1$ , leading to an unstable PLL
- ❑ By switching  $R_1$ - $C_1$  with  $C_2$ , the role of  $R_1$  is maintained




[B. Razavi, RF Microelectronics]
 
# PLL Based Modulation

- ❑ FSK and PSK modulation can be realized by means of a VCO that senses the binary data
- ❑ In open-loop modulation, the VCO center frequency drifts with time and temperature with no bound



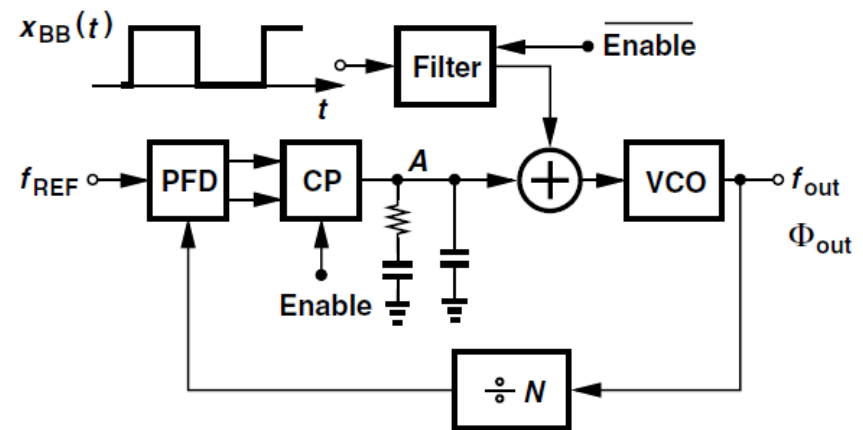
- ❑ One remedy is to phase-lock the VCO periodically to a reference so as to reset its center frequency



[B. Razavi, RF Microelectronics]
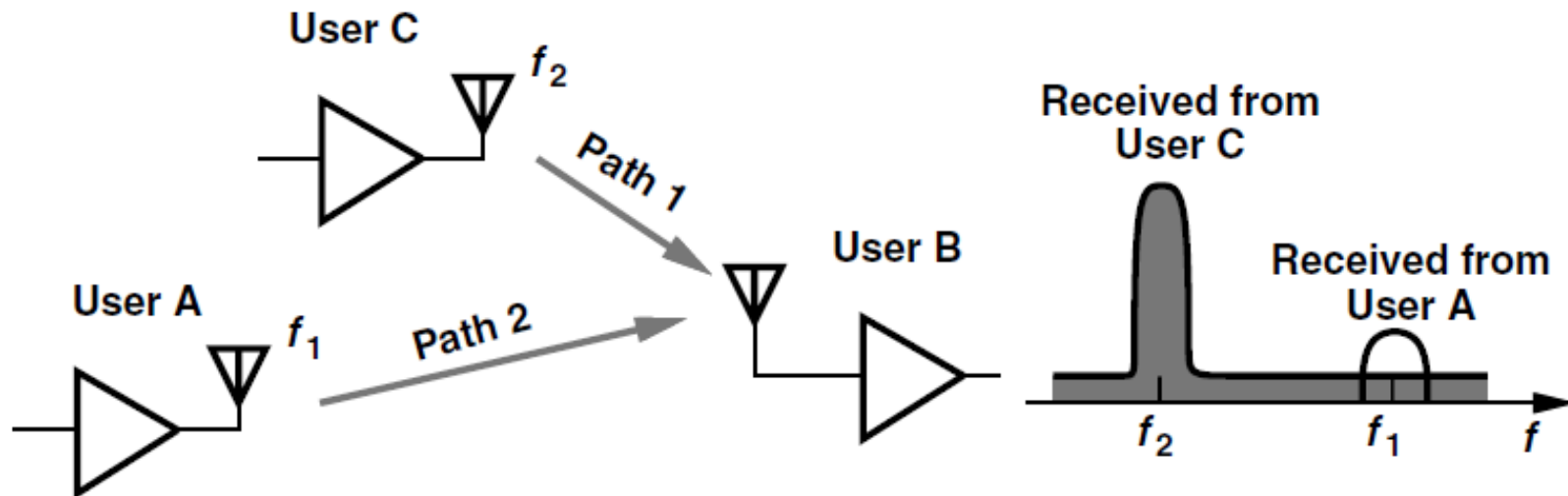
# Noise Issue


- ❑ User B receives a weak signal around  $f_1$  from user A while user C, located in the close proximity of user B, transmits a high power around  $f_2$  and significant broadband noise
- ❑ The noise transmitted by user C corrupts the desired signal around  $f_1$



[B. Razavi, RF Microelectronics]
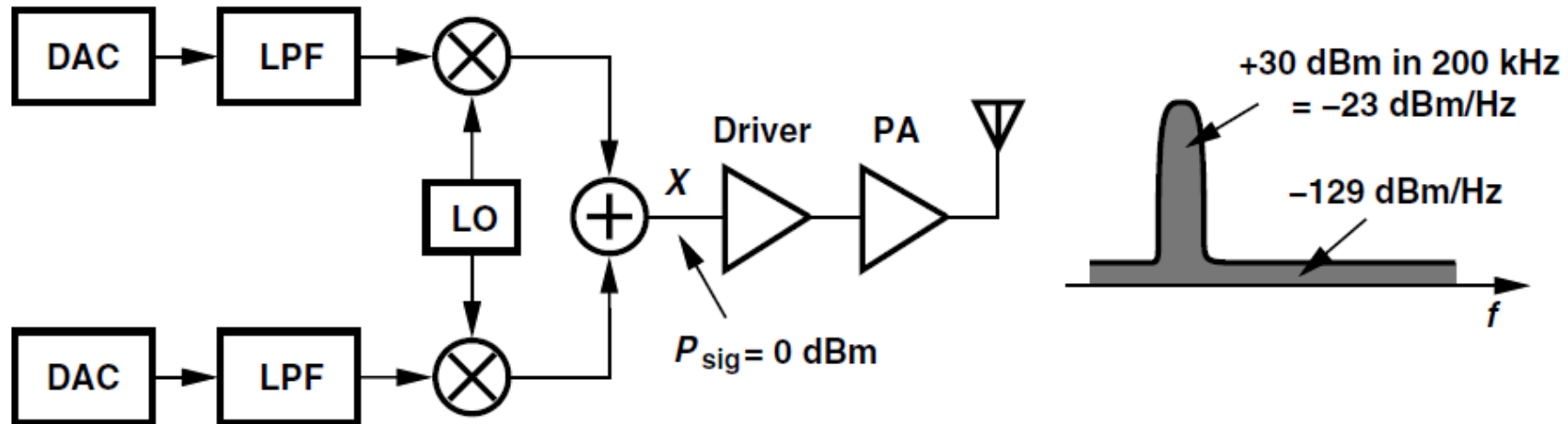
# Direct-Conversion TX


- ❑ Each stage in the signal path contributes noise, producing high output noise in the RX band even if the baseband LPF suppresses the out-of-channel DAC output noise
- ❑ The far-out phase noise of the LO also manifests itself as broadband noise at the PA output



- ❑ The maximum noise that a GSM transmitter is allowed to emit in the GSM receive band, namely, -129 dBm/Hz

[B. Razavi, RF Microelectronics]

# PLL Modulation

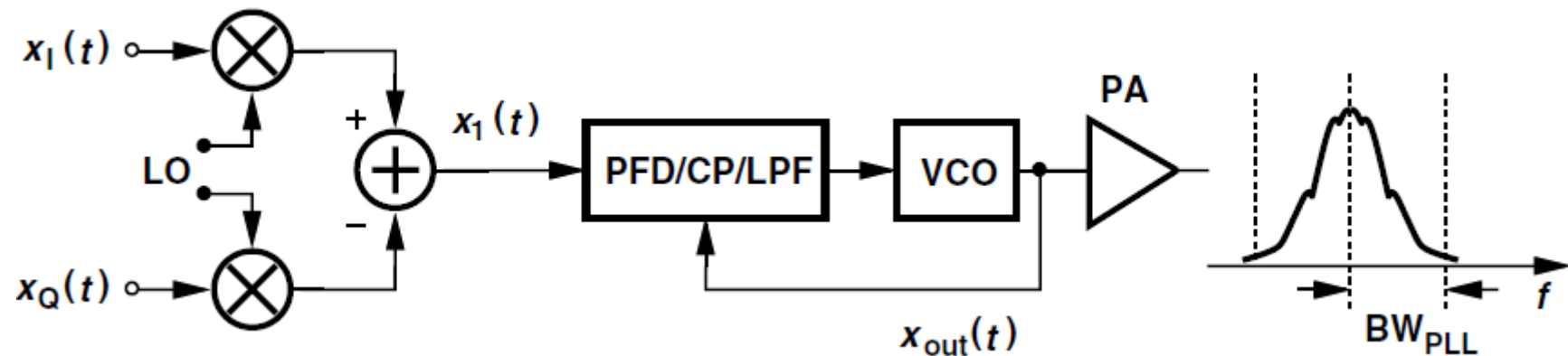


□ If the PLL bandwidth is only large enough to accommodate the signal, then the broadband noise traveling to the antenna arises primarily from the far-out phase noise of the VCO. So this architecture need only minimize the broadband noise of one building block (VCO)

[B. Razavi, RF Microelectronics]



# Nx PLL Modulation


---

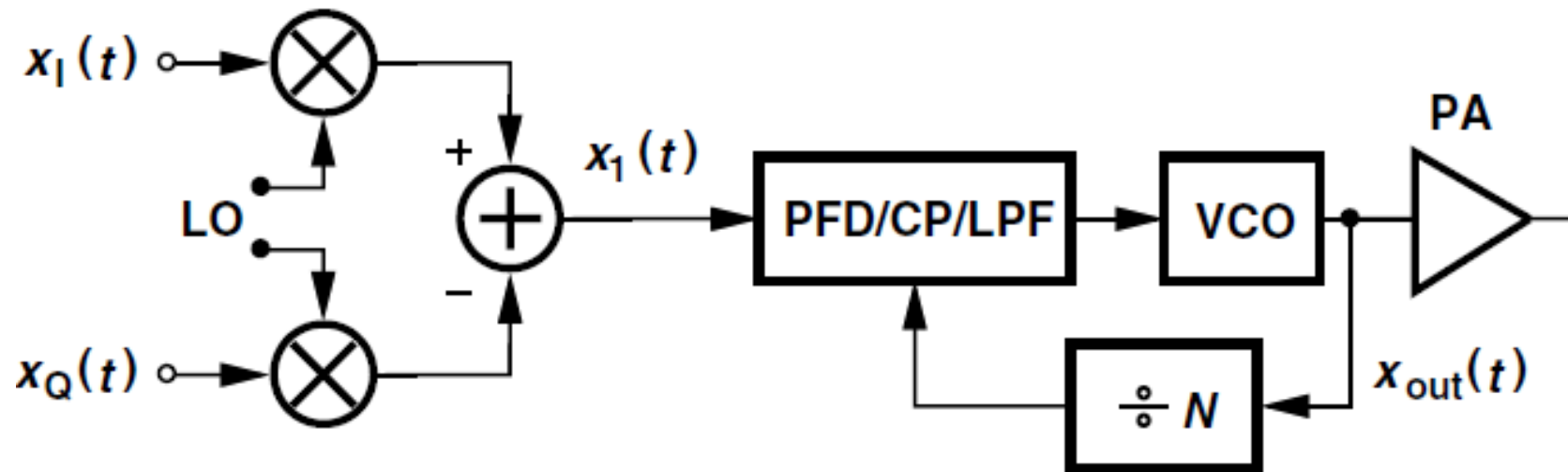

- ❑ Adding a feedback divider to the PLL proportionally reduces the carrier frequency
- ❑ But the PLL multiplies the phase by a factor of  $N$ , altering the signal bandwidth and modulation


[B. Razavi, RF Microelectronics]

# Offset PLL Modulation

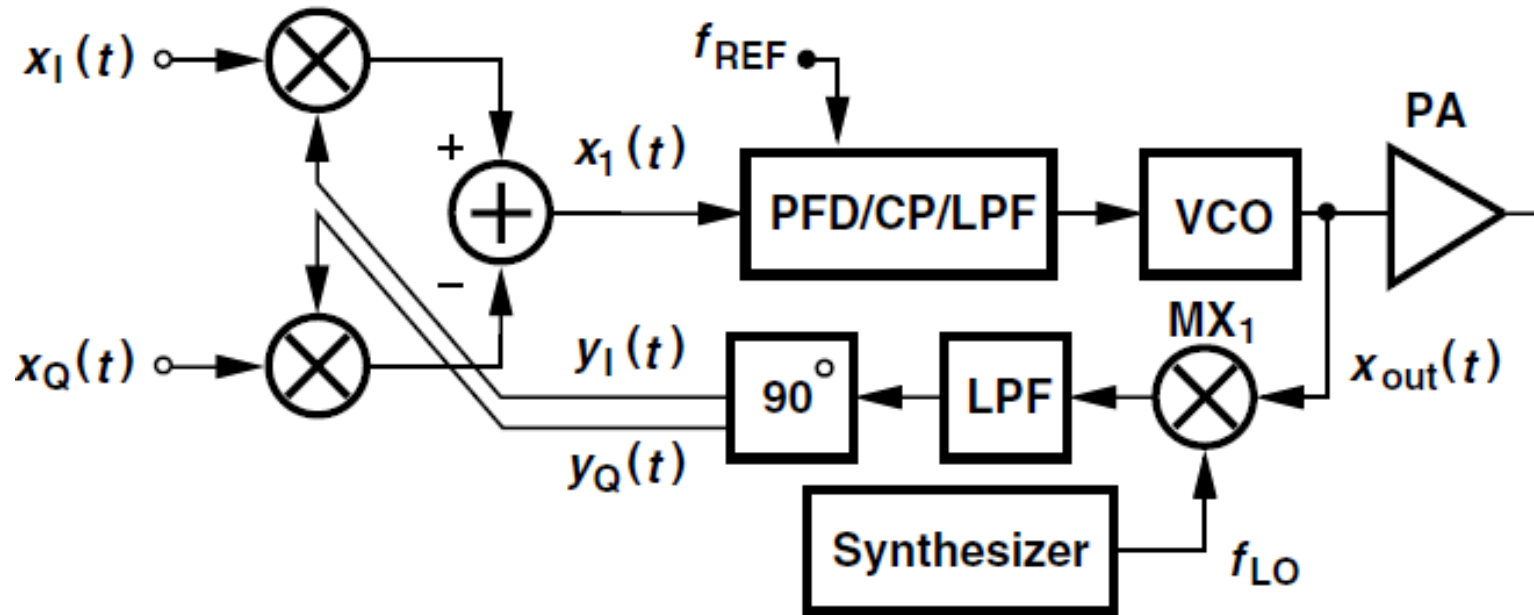

□ An “offset mixer,”  $MX_1$ , downconverts the output to a center frequency of  $f_{REF}$ , and the result is separated into quadrature phases, mixed with the baseband signals, and applied to the PFD

# Offset PLL Modulation

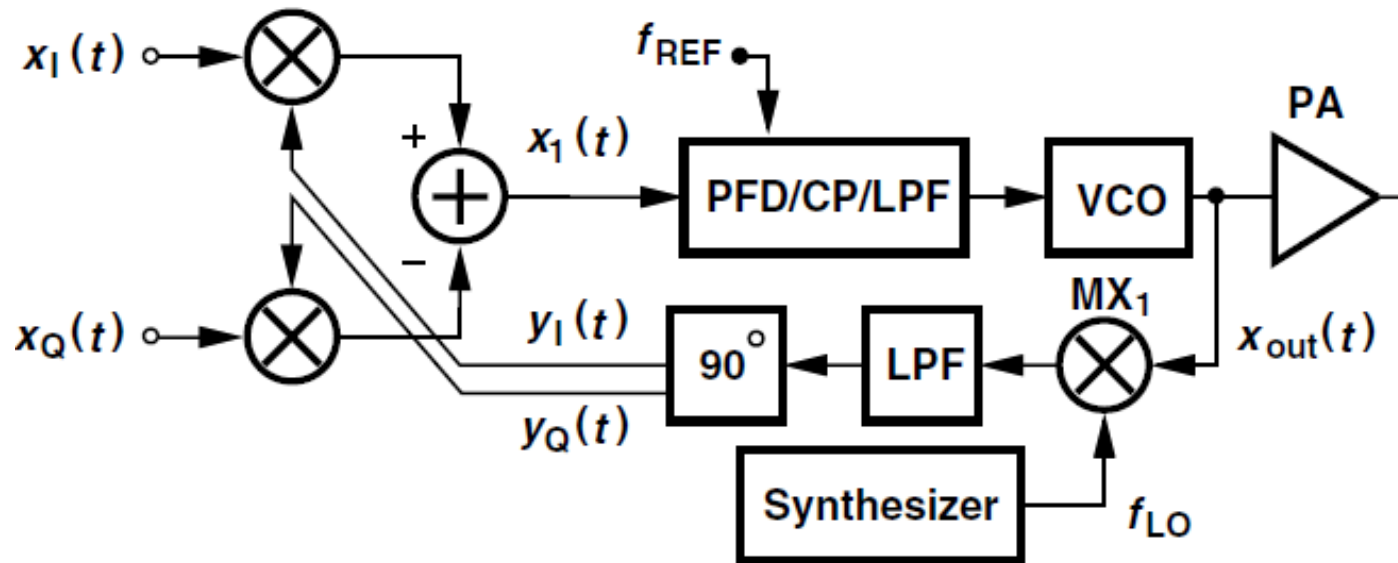


- ❑ The local oscillator waveform driving the offset mixer must be generated by another PLL
- ❑ The presence of two VCOs on the same chip raises mutual injection pulling between them. To ensure a sufficient difference between their frequencies, the offset frequency,  $f_{REF}$ , must be chosen high enough

[B. Razavi, RF Microelectronics]
 
# Oscillator Pulling

❑ The PA output exhibits very large swings, which couple to the oscillator through the silicon substrate, package parasitics, and traces on the PCB.




❑ In order to avoid injection pulling, the PA output frequency and the oscillator frequency must be made sufficiently different

[B. Razavi, RF Microelectronics]

# VCO Pulling

---

 


- ❑ The instantaneous output voltage of the PA is simply an amplified replica of that of the VCO
- ❑ The overall effect on the VCO is typically negligible

[B. Razavi, RF Microelectronics]
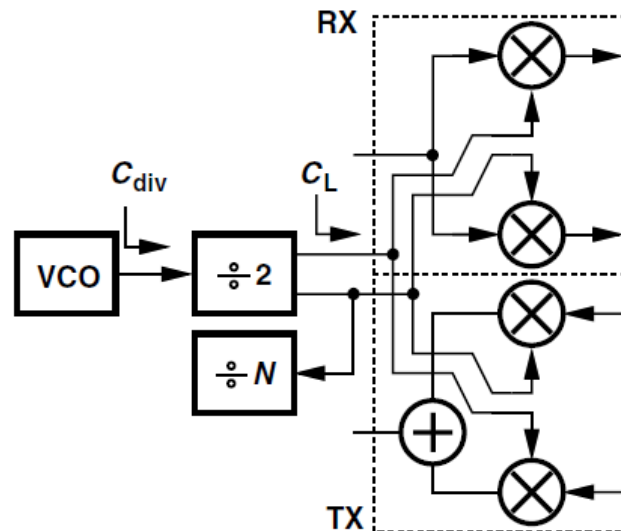
# Divider

---


- ❑ The divider modulus,  $N$ , must change in unity steps
- ❑ The first stage of the divider must operate as fast as the VCO
- ❑ The divider input capacitance load the VCO
- ❑ The divider must consume low power



- ❑ A buffer can be inserted at the input and/or output of the divider but at the cost of greater power dissipation

[B. Razavi, RF Microelectronics]


# Pulse Swallow Divider

 

- ❑ Dual-modulus prescaler: provides a divide ratio of  $N+1$  or  $N$
- ❑ Swallow counter: divides its input frequency by a factor of  $S$ , which controls the modulus of the prescaler
- ❑ Program counter: has a constant modulus,  $P$ . When it counts  $P$  pulses at its input, it resets the swallow counter

[B. Razavi, RF Microelectronics]

# Pulse Swallow Divider

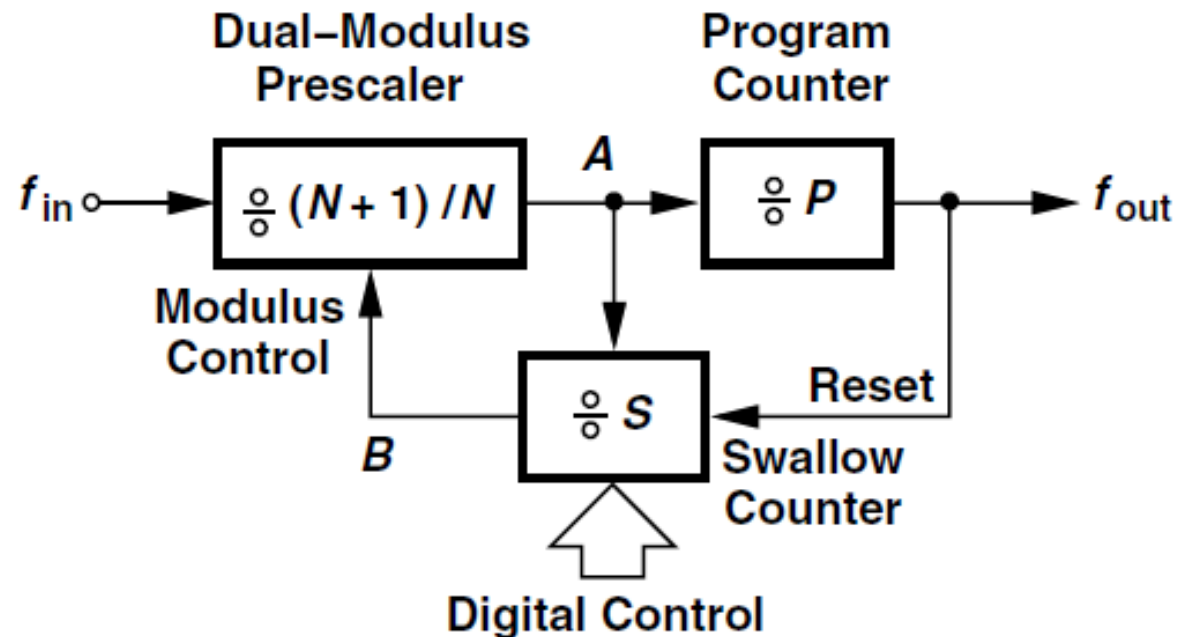



□ Adding the total number of the pulses at the prescaler input in the two modes, we have  $(N+1)S + N(P-S) = NP + S$

□ Sensing the high-frequency input, the prescaler proves the most challenging (Power Scaling Techniques)

[B. Razavi, RF Microelectronics]



# Pulse Swallow Divider with $\div 2$

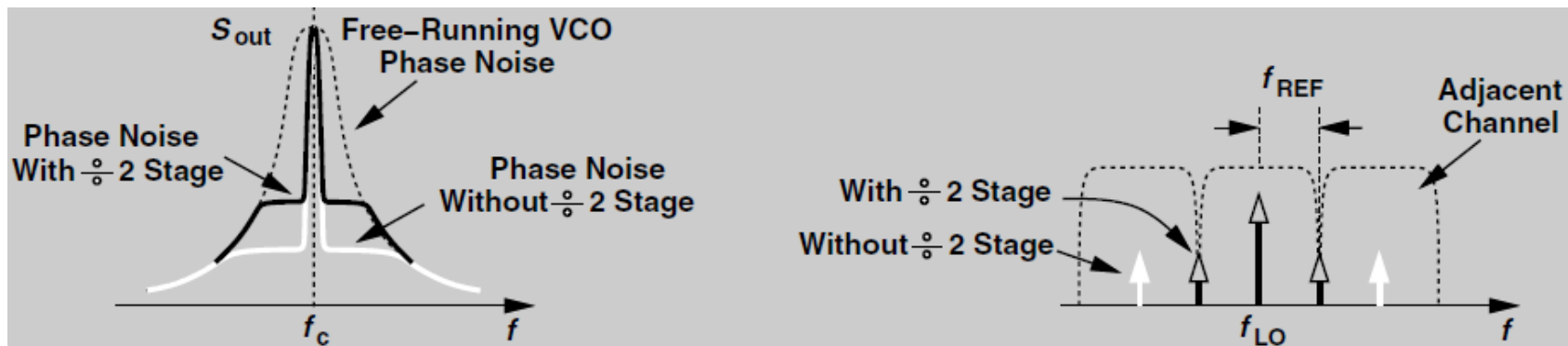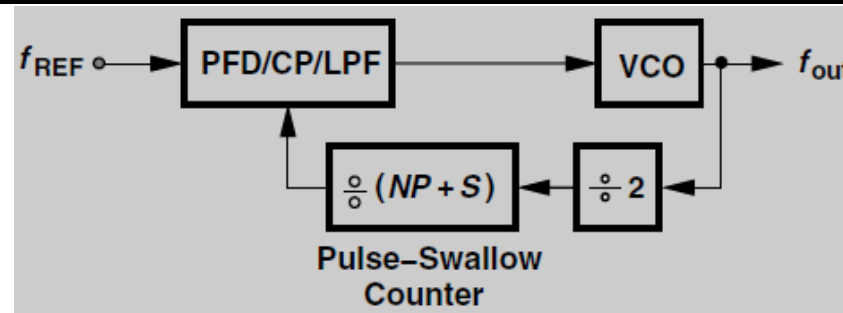


□  $f_{REF} = f_{ch}/2$ . The lock speed and the loop bandwidth are therefore scaled down by a factor of two, making the VCO phase noise more pronounced

□ The reference sideband lies at the edge of the adjacent channel rather than in the middle of the channel

[B. Razavi, RF Microelectronics]

# Swallow Counter

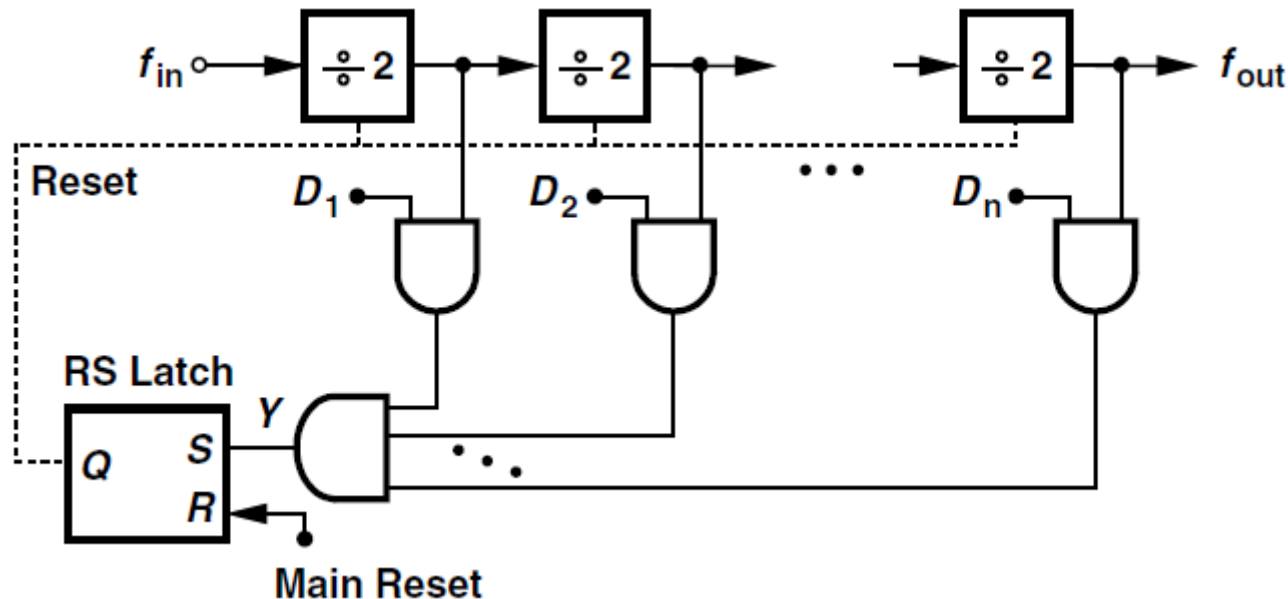


- ❑ Cascaded  $\div 2$  stages count the input and the NAND gates compare the count with the digital input,  $D_n D_{n-1} \cdots D_1$
- ❑ Once the count reaches the digital input, Y goes high, setting the RS latch. The latch output then disables the  $\div 2$  stages

[B. Razavi, RF Microelectronics]
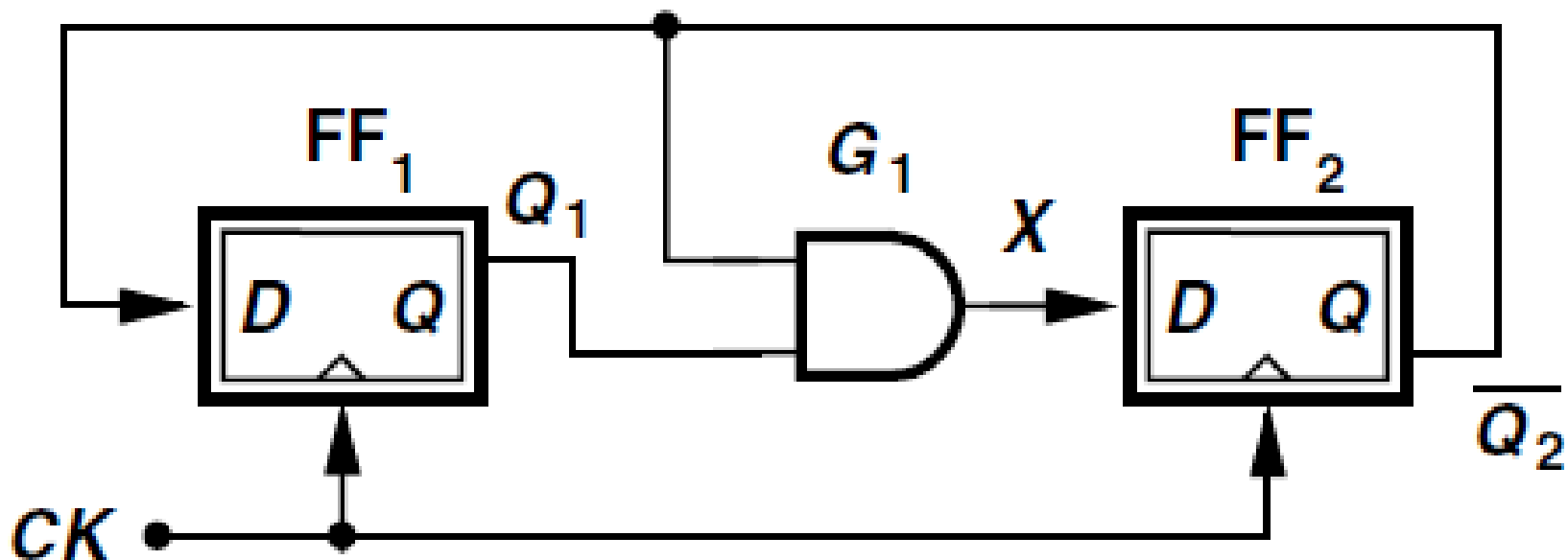
# Divide-by-3 Circuit

- Note that a  $\div 2$  circuit can be realized as a D-flipflop placed in a negative feedback loop
- A  $\div 3$  circuit, on the other hand, requires two flipflops




[B. Razavi, RF Microelectronics]

- [B. Razavi, RF Microelectronics]**
 
# Divide-by-2/3 Circuit

- It is possible to rearrange the  $\div 2/3$  stage so as to reduce the loading on the second flipflop
- The delay between the two FFs is also reduced




- This circuit has a 40% speed advantage over the previous one

[B. Razavi, RF Microelectronics]
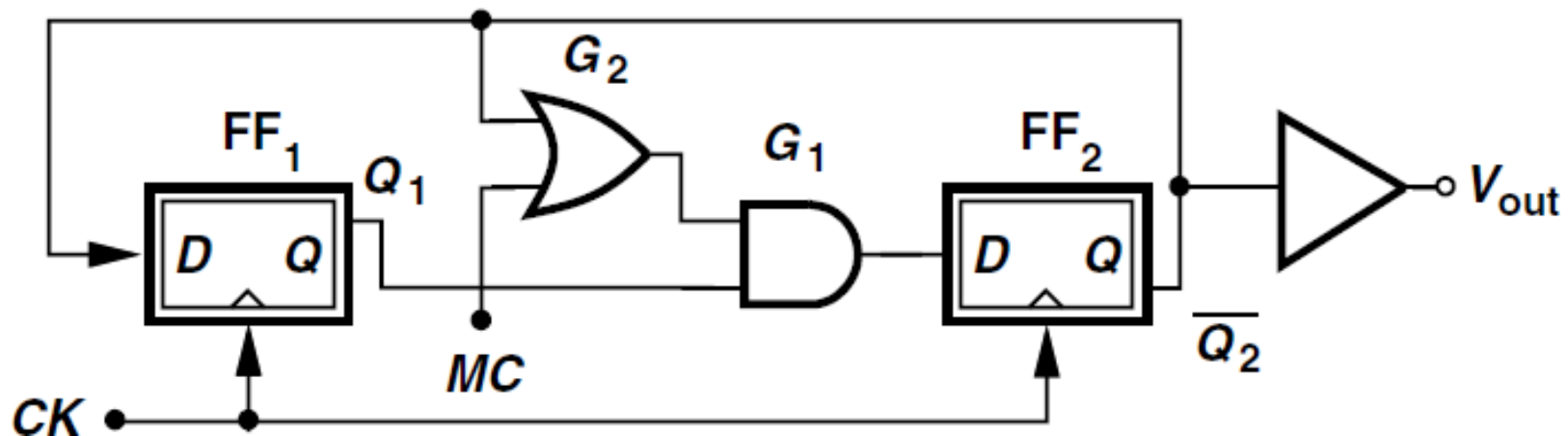
# Divide-by-3/4 Circuit

□ It is possible to rearrange the  $\div 2/3$  stage so as to reduce the loading on the second flipflop




□ The critical path (around FF<sub>2</sub>) contains a greater delay in this circuit than in the  $\div 3$  stage

[B. Razavi, RF Microelectronics]


# Other Dividers

□ Divide-by-8/9 circuit:

$\div 2/3$

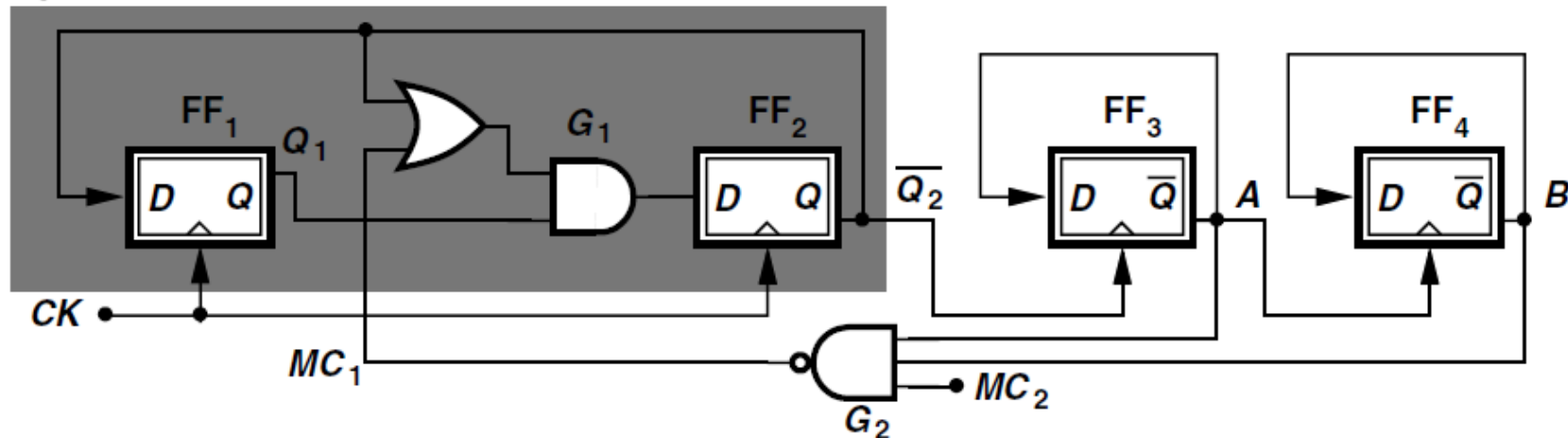


□ Divide-by-15/16 circuit:

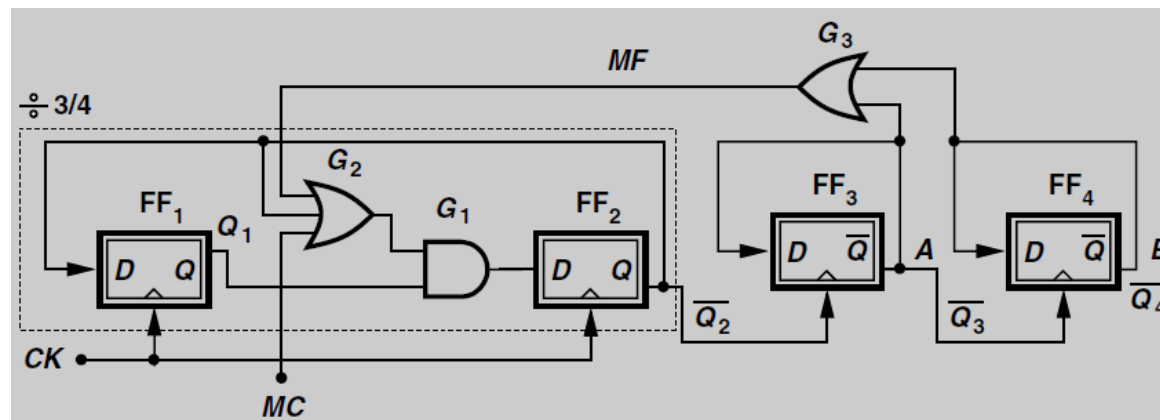

[B. Razavi, RF Microelectronics]
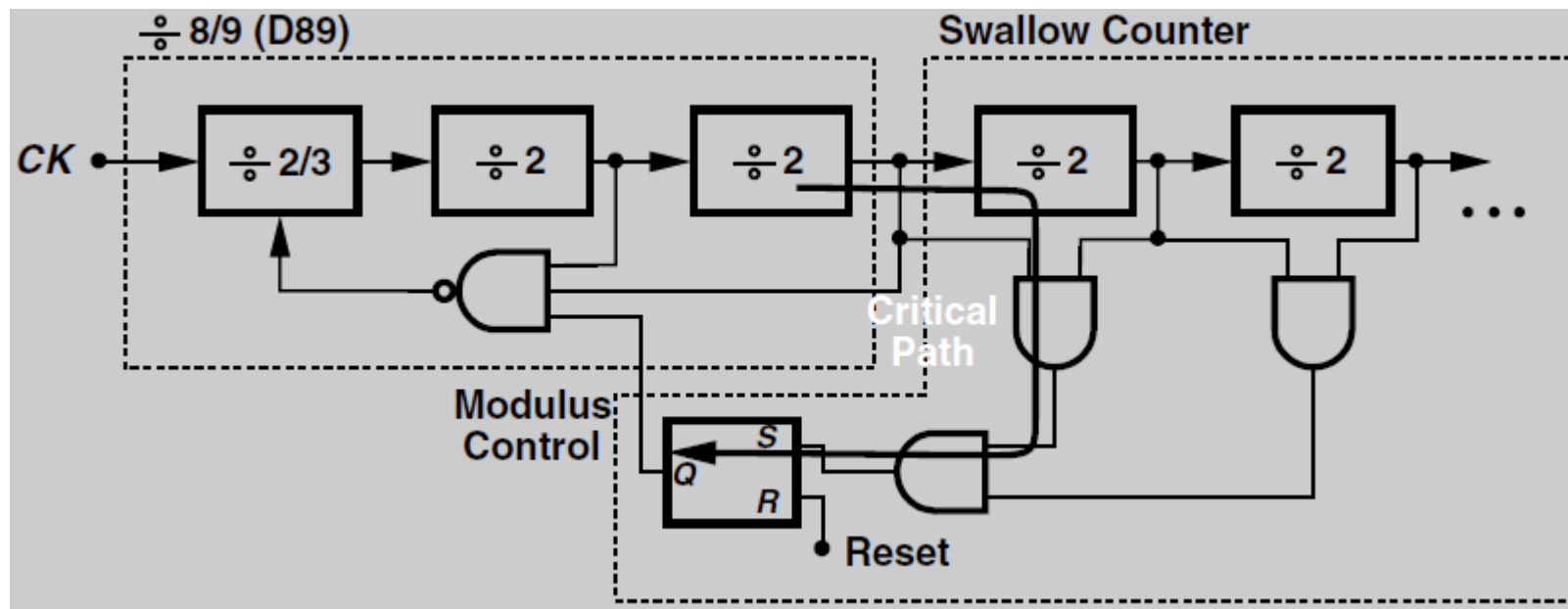
# Critical Path

- ❑ As the prescaler operates at a high frequency, the delay of critical path should be considered**




- ❑ Nowadays, the digital design tools can help to analyze the delay issue of critical path ( $\text{Slack} > 0$ )**

**[B. Razavi, RF Microelectronics]**


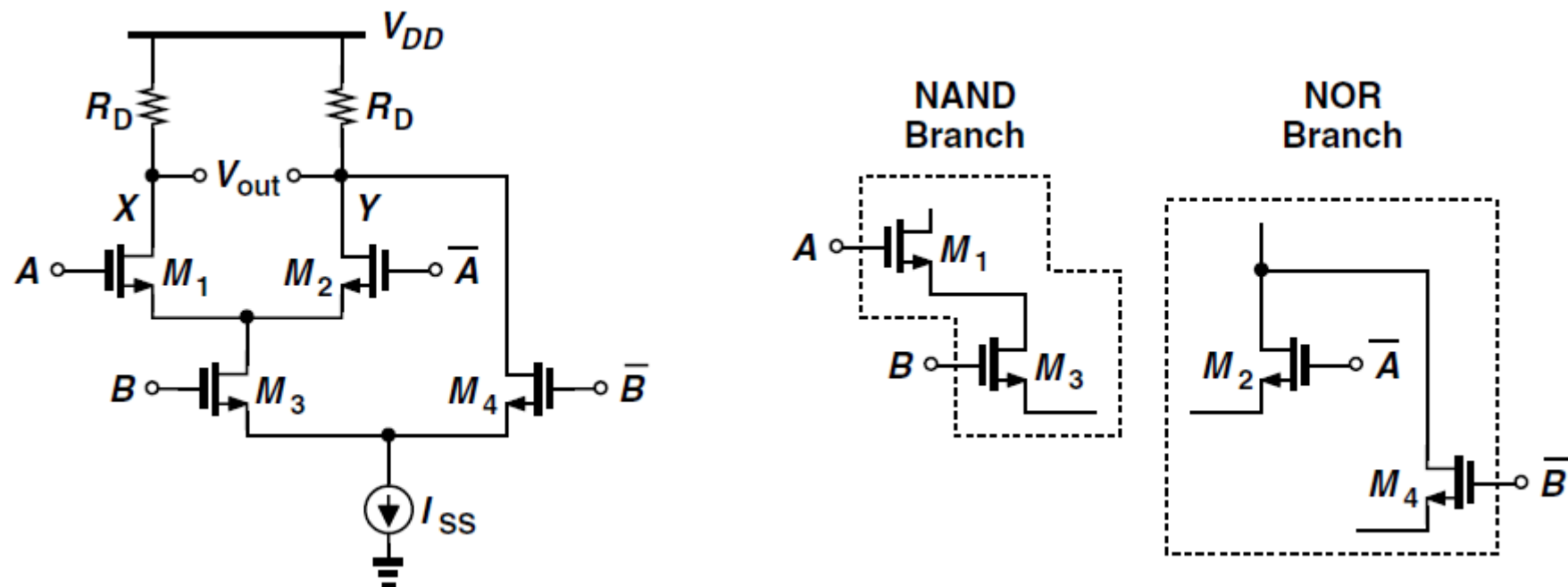
# Current Mode Logic (CML)



- ❑ CML derives its speed from the property that a differential pair can be rapidly enabled and disabled through its tail current source



**[B. Razavi, RF Microelectronics]**


# CML NOR & XOR

---

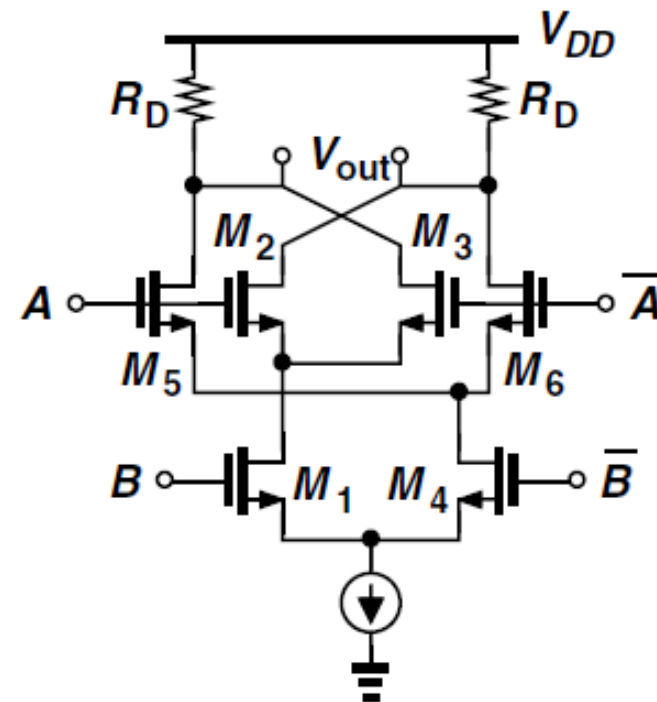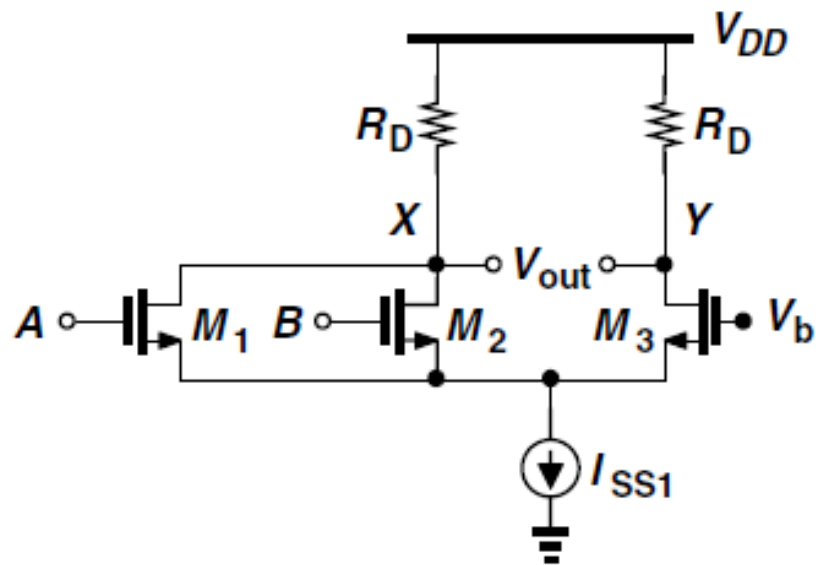

[B. Razavi, RF Microelectronics]

# Low-Voltage XOR

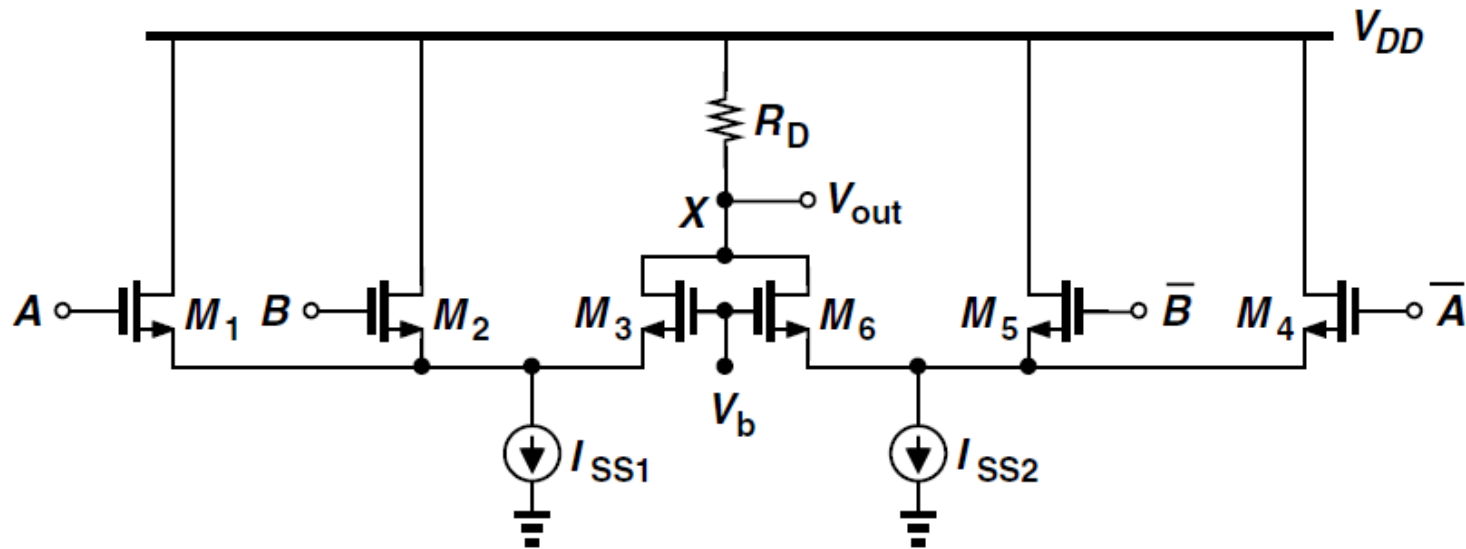

□The XOR gate can avoid stacking to realize low-voltage operation  $I_{D3} = \overline{A + B}$   $I_{D6} = \overline{\overline{A} + \overline{B}}$

□The summation of  $I_{D3}$  and  $I_{D6}$  at node X is equivalent to an OR operation, and the flow of the sum through  $R_D$  produces an inversion.



$$V_{out} = \overline{(\overline{A + B} + \overline{\overline{A} + \overline{B}})}$$

$$= \overline{AB} + A\overline{B}$$

[B. Razavi, RF Microelectronics]
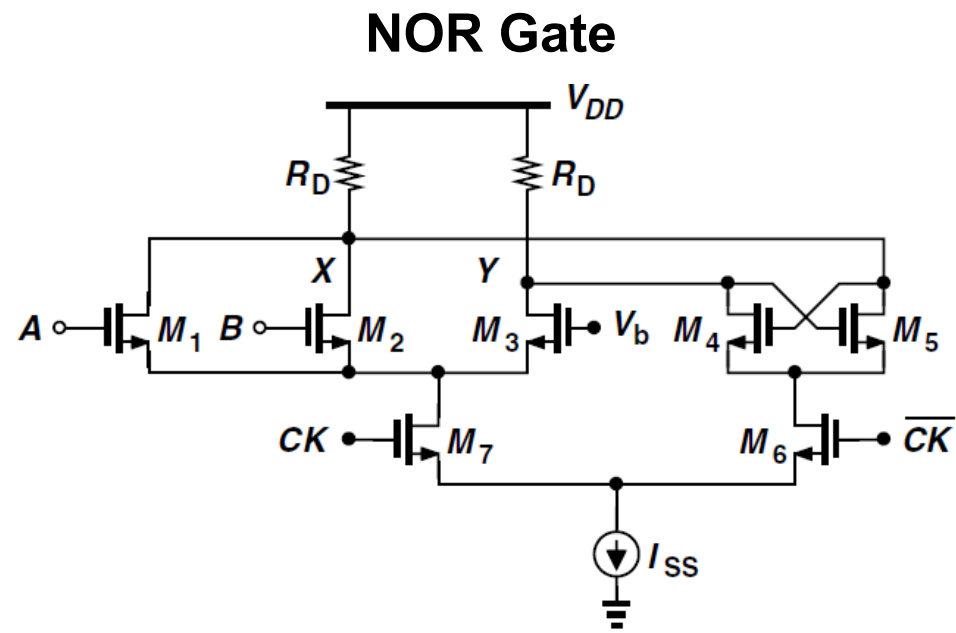 
# CML Latch

□ The speed advantage of CML circuits is especially pronounced in latches




□ In the latch mode, the positive feedback of regeneration pair  $M_3$  and  $M_4$  amplifies the difference between  $V_X$  and  $V_Y$

[B. Razavi, RF Microelectronics]
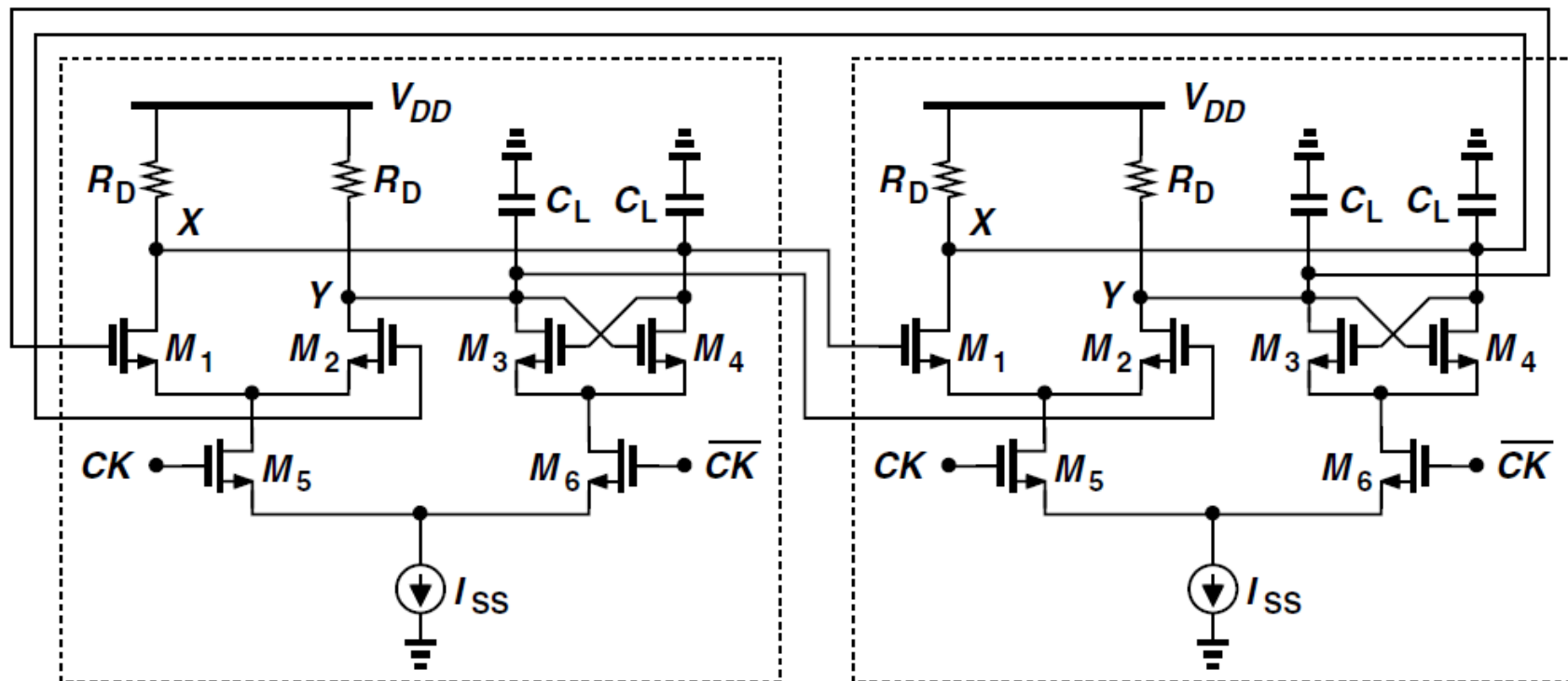
# CML Divide-by-2 Circuit


□ A  $\div 2$  circuit can be constructed by placing two D latches in a negative feedback loop



[B. Razavi, RF Microelectronics]
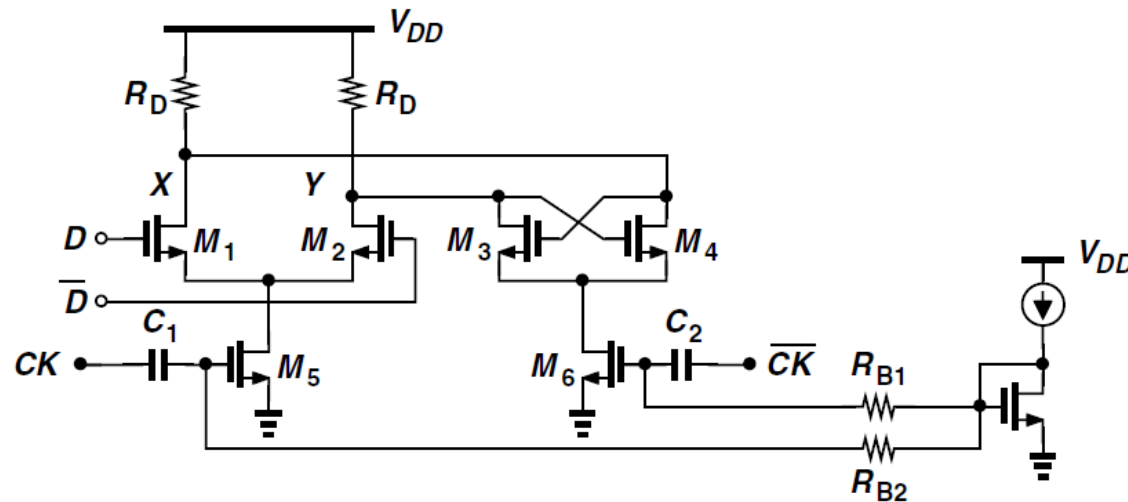
# Class-AB Latch



- ☐ With low supply voltage, the tail current can be removed



- ❑ The bias of the clocked pair is defined by a current mirror and the clock is coupled capacitively
- ❑ Large clock swings allow transistors  $M_5$  and  $M_6$  to operate in the class AB mode, i.e., their peak currents well exceed their bias current. This attribute improves the speed of the divider

**[B. Razavi, RF Microelectronics]**

# Inductive Peaking

  

□ From a small-signal perspective, we observe that the inductors rise in impedance at higher frequencies, allowing more of the currents produced by the transistors to flow through the capacitors and hence generate a larger output voltage.

[B. Razavi, RF Microelectronics]