
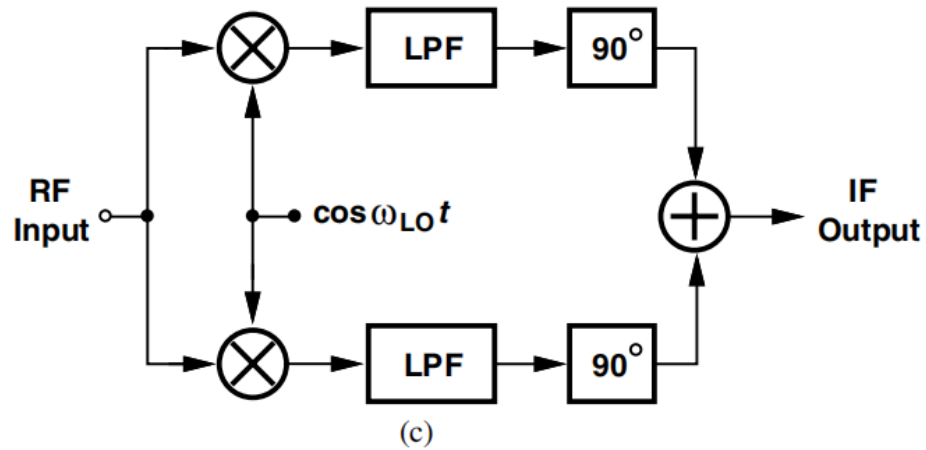
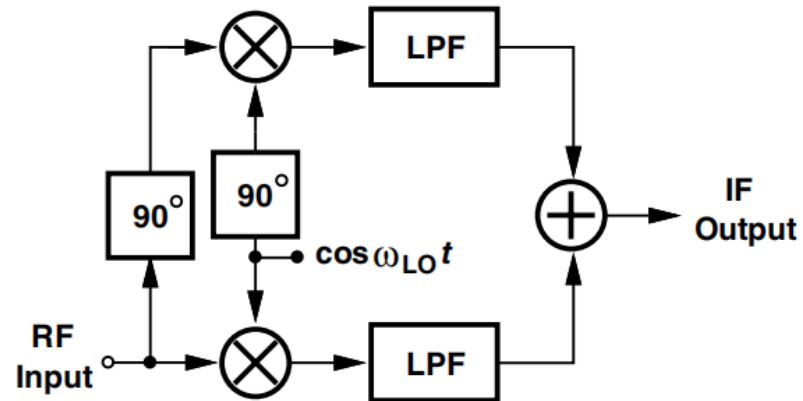


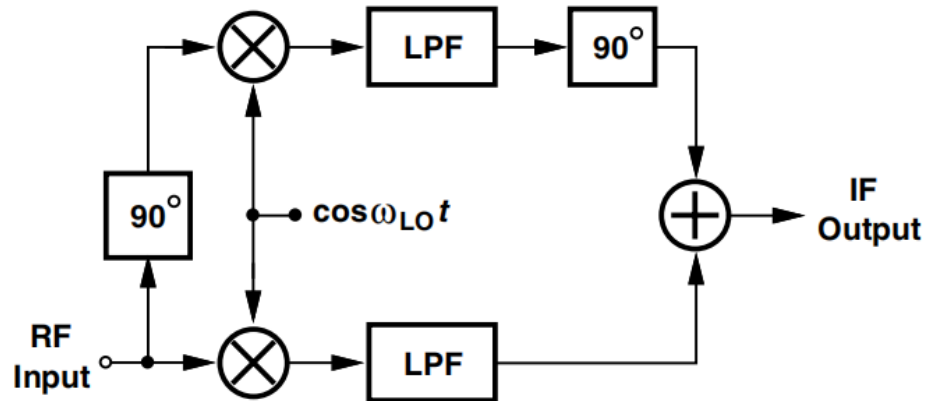
1. The figure below shows three variants of the Hartley architecture. Explain which one(s) can reject the image.



- (a) Can
- (b) Can not
- (c) Can not

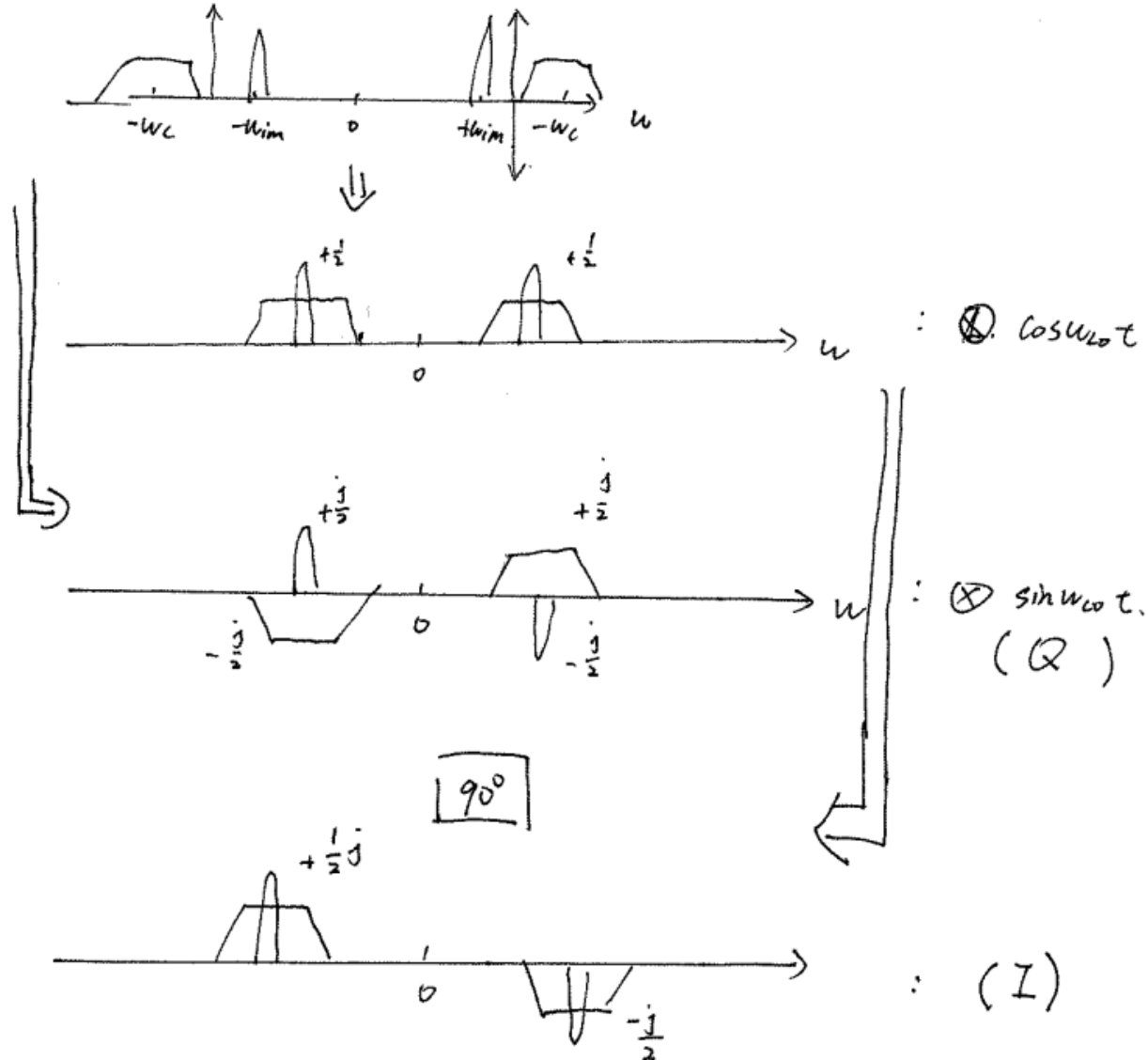2. If  $\sin\omega_{LO}t$  and  $\cos\omega_{LO}t$  in the Hartley architecture are swapped, does the RX still reject the image?

(Perform the above analysis graphically using the spectra)



Yes,  $\sin\omega_{LO}t$  and  $\cos\omega_{LO}t$  can be swapped as long as I will be subtracted by Q.

3. In the Weaver architecture of Fig. 2.3, assume high-side injection for the first quadrature downconversion and low-side injection for the second quadrature downconversion. Figure out the results in E and F should be added or subtracted **with the aid of signal spectra at nodes ABEF.**

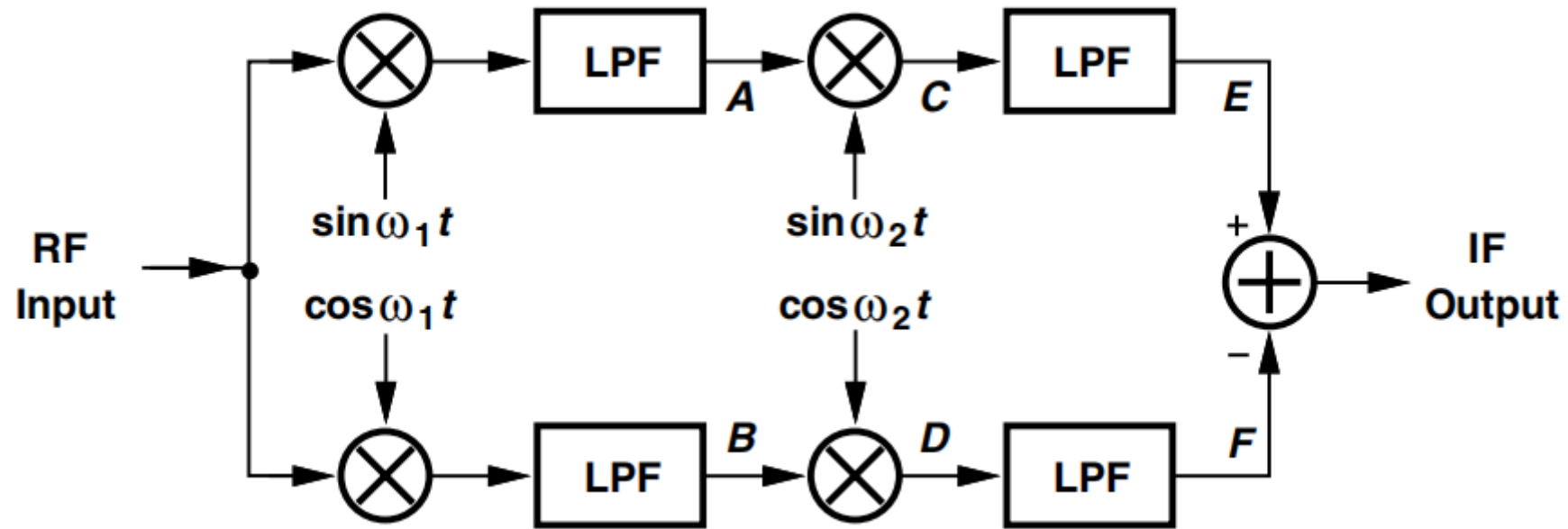


Fig.2.3

3. In the Weaver architecture of Fig. 2.3, assume high-side injection for the first quadrature downconversion and low-side injection for the second quadrature downconversion. Figure out the results in E and F should be added or subtracted with the aid of signal spectra at nodes ABEF.

