

1. Prove that the Q of the circuit shown in Fig. 7. 1 is given by Eq. (7.1).

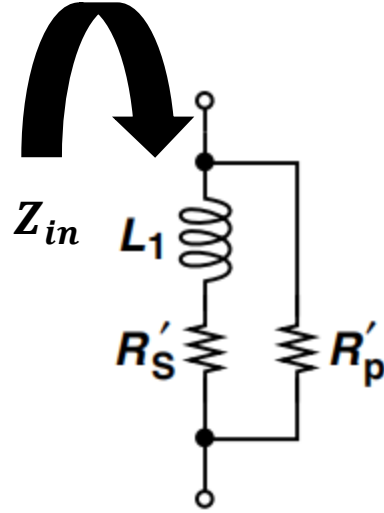


Fig. 7.1

$$Q = \frac{L_1 \omega R'_p}{L_1^2 \omega^2 + R'_S (R'_S + R'_p)}.$$

Eq. (7.1)

$$Z_{in}(s) = (sL_1 + R'_S) \parallel R'_p = \frac{sL_1 R'_p + R'_S R'_p}{sL_1 + R'_S + R'_p}$$

$$Z_{in}(j\omega) = \frac{R'_S R'_p + j\omega L_1 R'_p}{R'_S + R'_p + j\omega L_1} = \frac{(R'_S R'_p + j\omega L_1 R'_p)(R'_S + R'_p - j\omega L_1)}{(R'_S + R'_p)^2 - \omega^2 L_1^2}$$

$$Q \triangleq \frac{\text{Im}(Z_{in})}{\text{Re}(Z_{in})} = \frac{\omega L_1 R'_p (R'_S + R'_p) - \omega L_1 (R'_S R'_p)}{(R'_S)^2 R'_p + (R'_p)^2 R'_S + \omega^2 L_1^2 R'_p} = \frac{L_1 \omega R'_p}{L_1^2 \omega^2 + R'_S (R'_S + R'_p)}$$

2. Repeat Example 7.19 for four turns.

Example 7.19

Estimate the equivalent lumped interwinding capacitance of the three-turn spiral shown in Fig. 7.39(a).


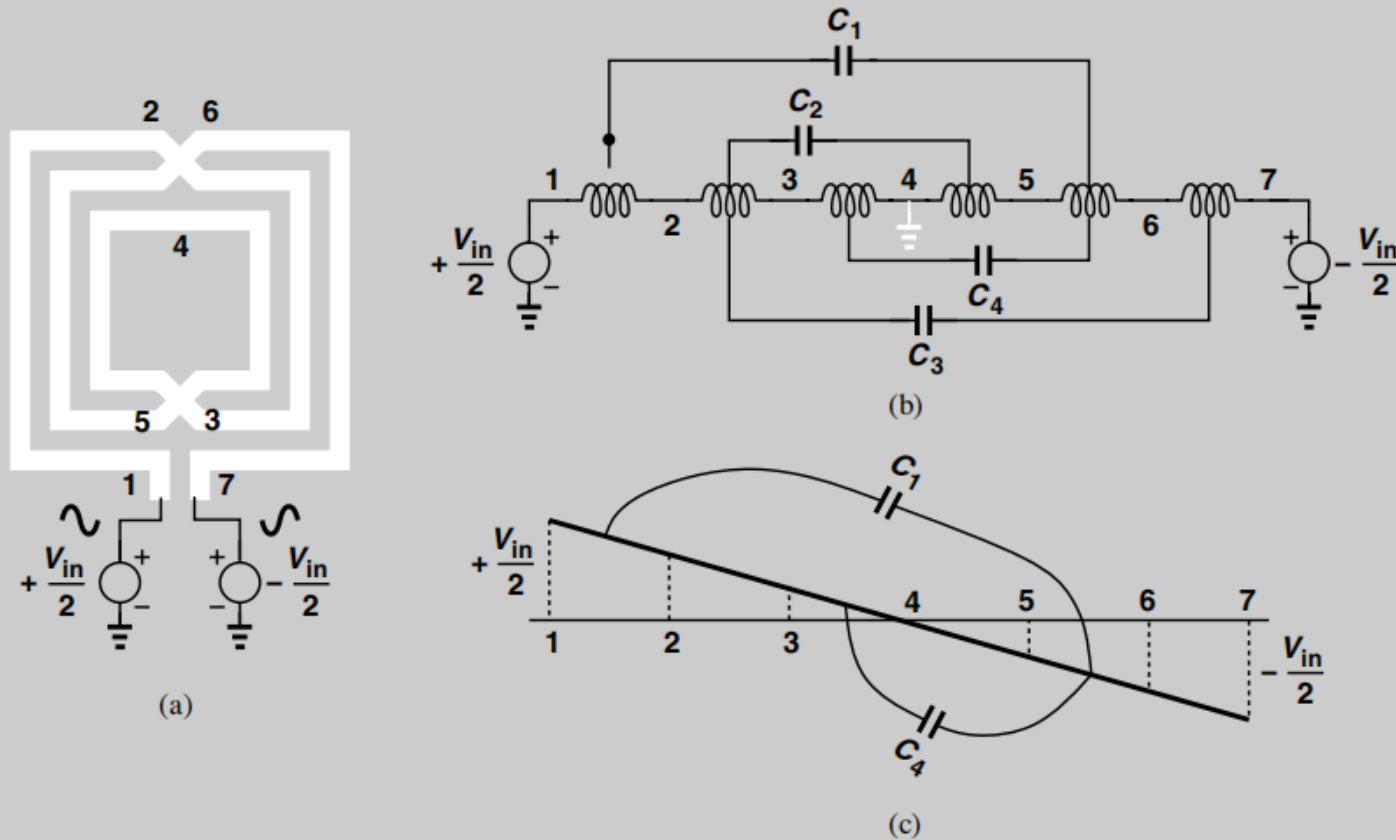
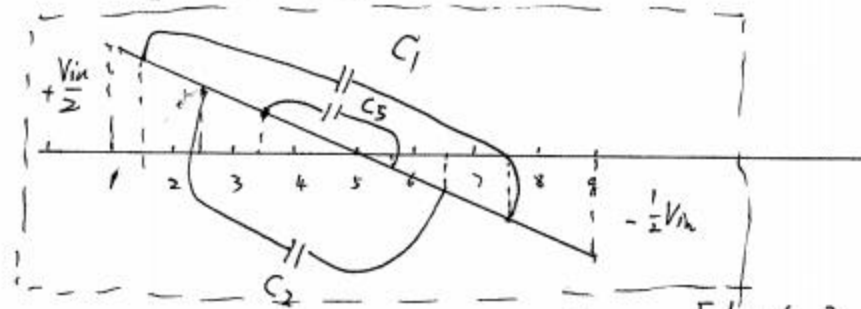


Figure 7.39 (a) Three-turn symmetric inductor, (b) equivalent circuit, (c) voltage profile along the ladder.

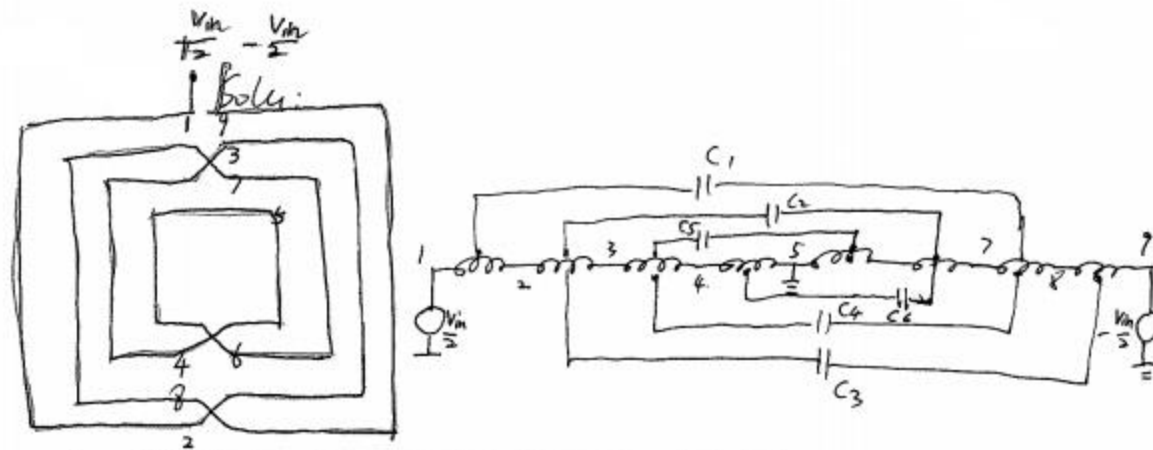

$$\left. \begin{array}{l} C_1 \& C_3 \text{ sustains } \frac{6}{8} V_{in} \\ C_2 \& C_4 \text{ sustains } \frac{4}{8} V_{in} \\ C_5 \& C_6 \text{ sustains } \frac{2}{8} V_{in} \end{array} \right\} \Rightarrow$$

$$E_{tot} = 2 \cdot \left[\frac{1}{2} C \left(\frac{6}{8} V_{in} \right)^2 + \frac{1}{2} C \left(\frac{4}{8} V_{in} \right)^2 + \frac{1}{2} C \left(\frac{2}{8} V_{in} \right)^2 \right]$$

$$= \frac{7}{8} \cdot C \cdot V_{in}^2$$

$$\therefore C_1 + C_2 + \dots + C_6 = C_{tot} \Rightarrow C = \frac{C_{tot}}{6}$$

$$\therefore E_{tot} = \frac{7}{8} \cdot \frac{C_{tot}}{6} \cdot V_{in}^2$$

$$\Rightarrow \boxed{C_{eq} = \frac{7}{24} C_{tot}}$$