

Power Amplifiers (1/2)

ZHAO BO


Institute of VLSI Design

Zhejiang University

Email: zhaobo@zju.edu.cn


Web: person.zju.edu.cn/zhaobo

A Cell Phone

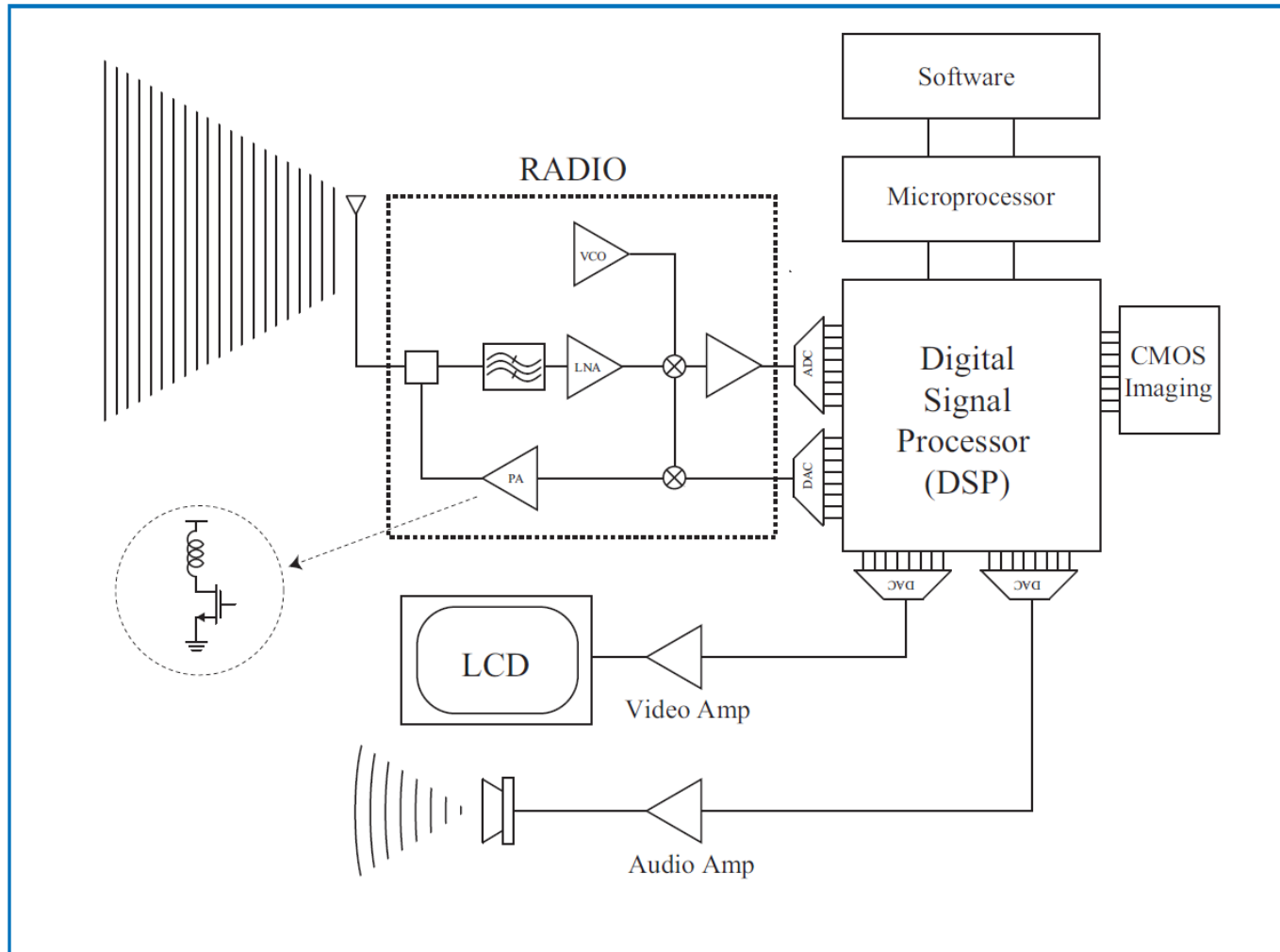

[Ali Niknejad, EE142 & EE242 of UC Berkeley]


Power Amplifier (PA)

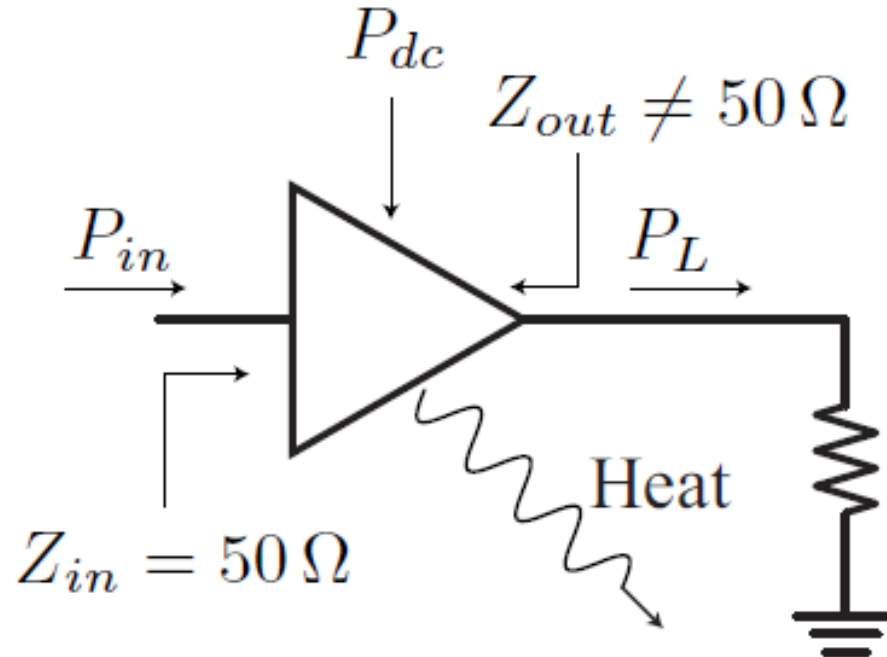

- ❑ **Powerful:** PA delivers power to a given load with maximum efficiency
- ❑ **Linear:** PA faithfully transfers the modulation from the input to the output

[Ali Niknejad, EE142&EE242 of UC Berkeley]

Audio PA Example

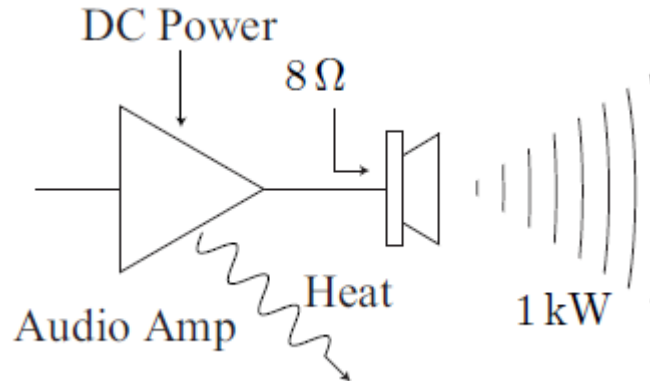

- ❑ Consider a PA that delivers 1kW of power into 8 speakers.
- ❑ Assuming a sinusoidal input, the peak voltage and current are


$$V = \sqrt{2RP} = \sqrt{2 \cdot 8 \cdot 1000} = 126V$$

$$I = \frac{2P}{V} = 15.8A$$

- ❑ Such large currents and voltages require special techniques and/or technology

[Ali Niknejad, EE142&EE242 of UC Berkeley]

Mobile Phone Example

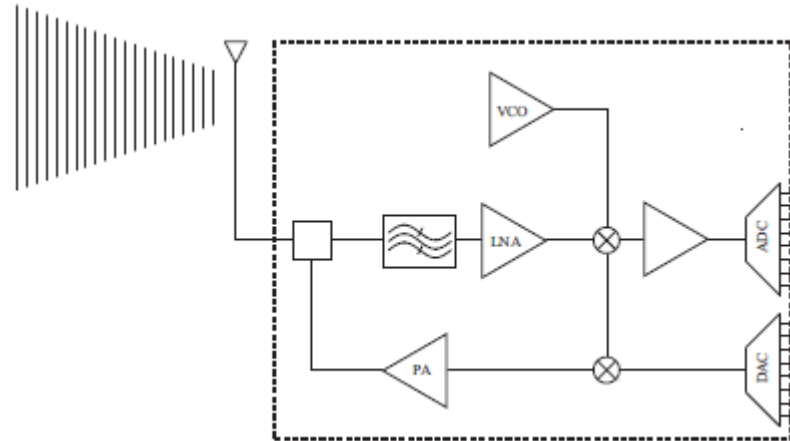

- Consider a typical mobile phone that delivers 1W in to a 50 antenna. Here we find that


$$V_0 = \sqrt{2PR} = \sqrt{2 \cdot 50} = 10V$$

$$I_0 = 2/10 = 0.2A$$

- Most high-frequency Si transistors cannot handle 10V due to breakdown. Thus we need to transform the voltage down to a safe value


[Ali Niknejad, EE142&EE242 of UC Berkeley]

CS Stages

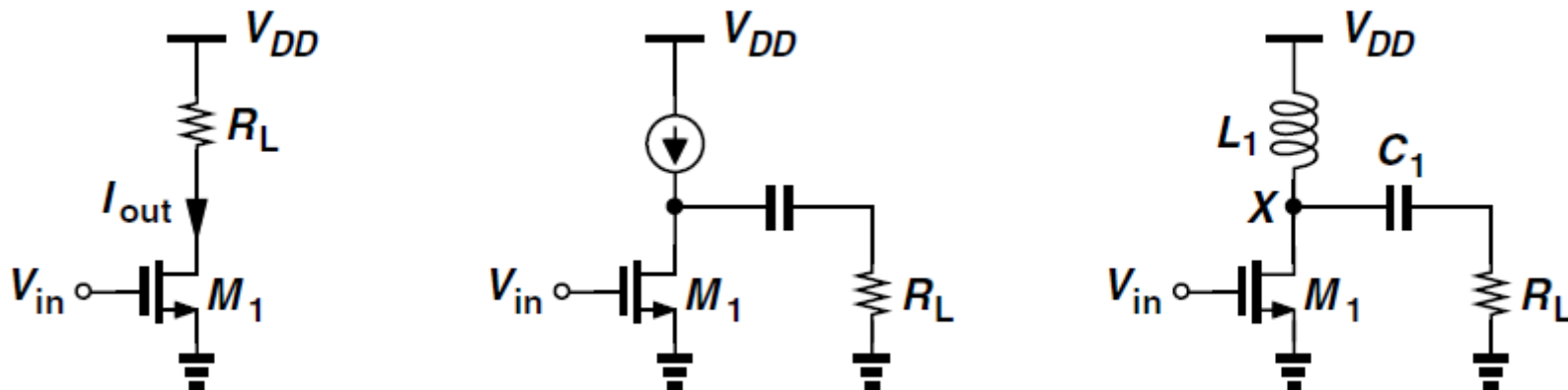

- ❑ Without an inductor, the circuits require a supply voltage greater than 10V
- ❑ If the load is realized as an inductor, the drain AC voltage exceeds the supply V_{DD} , even reaching $2V_{DD}$ (or higher)
- ❑ While allowing a lower supply voltage, the inductive load does not relax the “stress” on the transistor

CS Stages

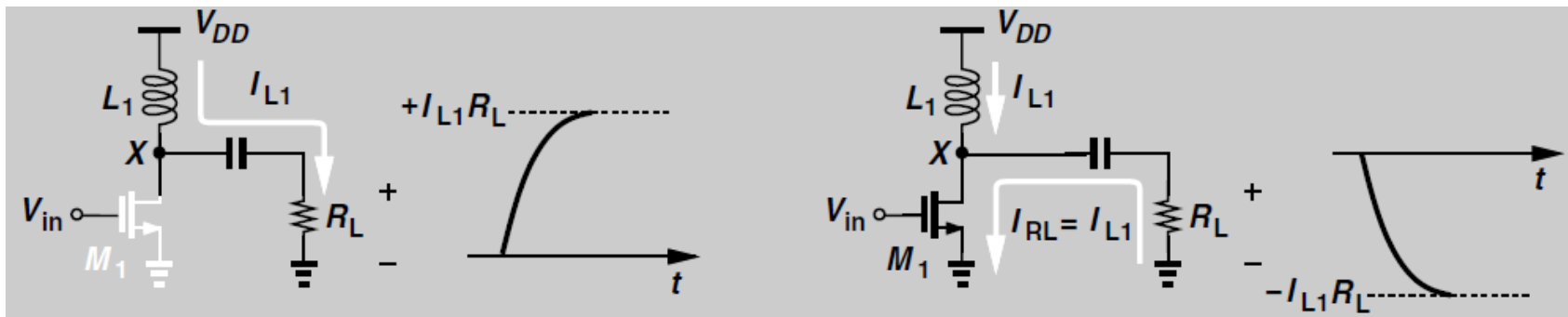



- ❑ A fundamental issue in PA design: The trade-off between the output power and the voltage swing experienced by the output transistor
- ❑ The product of the breakdown voltage and f_T of silicon devices is around 200 GHz · V

PA Considerations

- ❑ PAs drive large voltages/currents into small load impedances. Thus matching networks are critical. Any loss in the matching network has a severe impact on the efficiency of the amplifier.
- ❑ Heat generation is high. We need to carefully provide heat sinks to keep the junction temperatures as low as possible.
- ❑ Due to the interface with the external “off-chip” world, packaging and board parasitics are very important.
- ❑ The spectral “leakage” and harmonic generation in a PA must be kept to the a minimum in order to minimize interference to other users.

[Ali Niknejad, EE142&EE242 of UC Berkeley]

Impedance Transformation

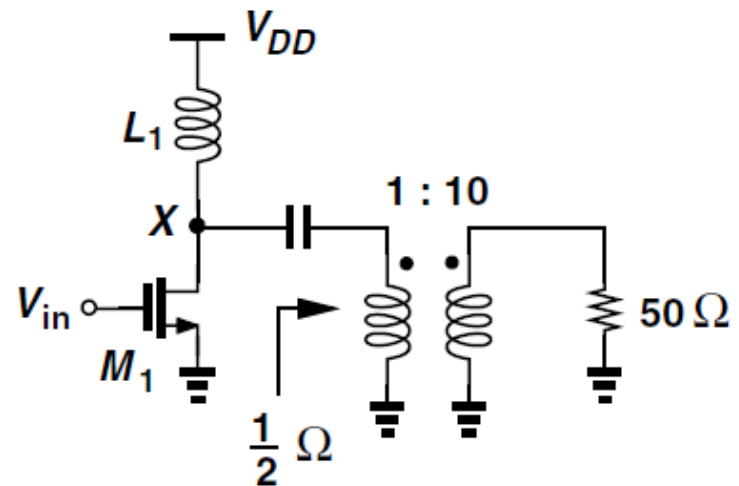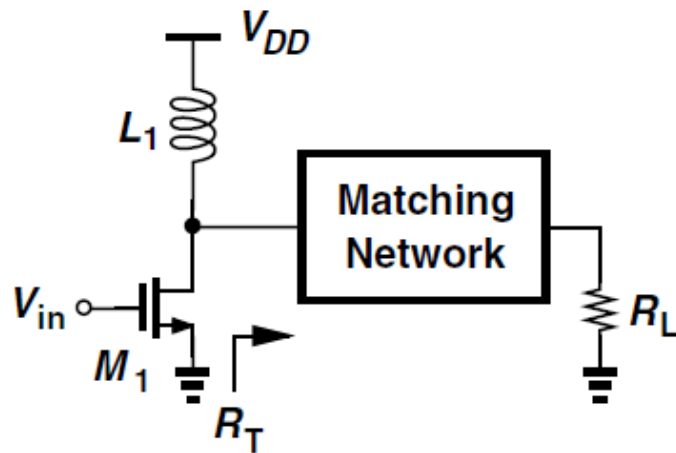


- ❑ The network transfers the load resistance to a lower value (R_T) so that smaller voltage swings still deliver the required power
- ❑ The need for transforming the voltage swings means that the current generated by the output transistor must be proportionally higher

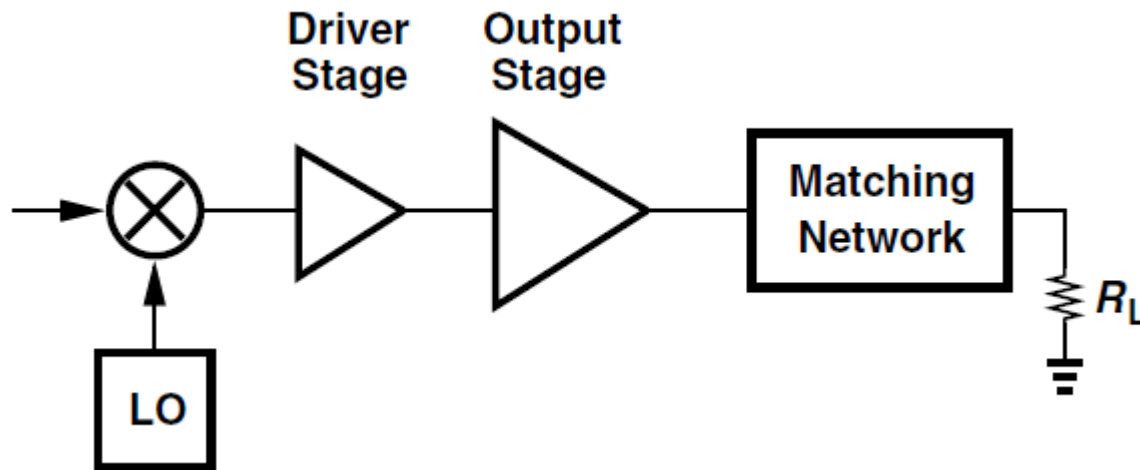[B. Razavi, RF Microelectronics]

Effect of High Current

- ❑ If the output transistor is chosen wide enough to carry a large current, then its input capacitance is very large, making the design of the preceding stage difficult



- ❑ Tapered stages can be interposed between the upconversion mixers and the output stage
- ❑ The multiple stages tend to limit TX output compression point
- ❑ The driver also consumes high power

[B. Razavi, RF Microelectronics]

Efficiency

- The Power Added Efficiency, or PAE, is a measure of how much power is added to a signal normalized by the DC power consumption

$$PAE = \eta = \frac{P_L - P_{in}}{P_{dc}}$$

- If the power gain is large


$$PAE = \frac{P_L(1 - G_p^{-1})}{P_{dc}} \approx \frac{P_L}{P_{dc}}$$

- The drain efficiency is defined as

$$\eta_{c|d} = \frac{P_L}{P_{dc}}$$

Linearity

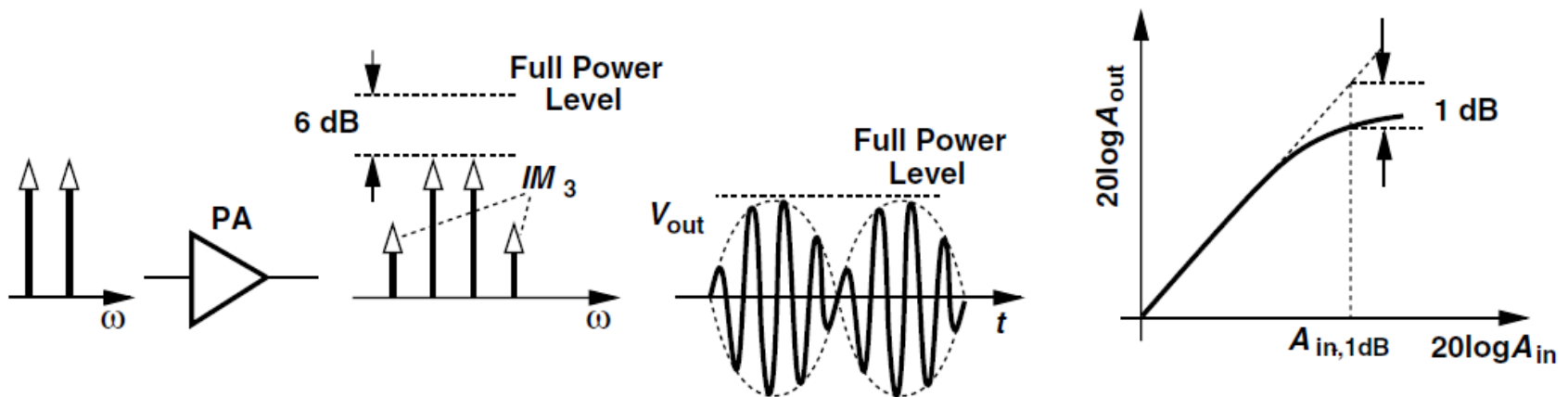□ PA nonlinearity leads to: 1) high adjacent channel power as a result of spectral regrowth, and 2) amplitude compression




□ The amplitude of the tones is chosen such that each main component at the output is 6 dB below the full power level, thus producing the maximum desired output voltage swing when the two tones add in-phase

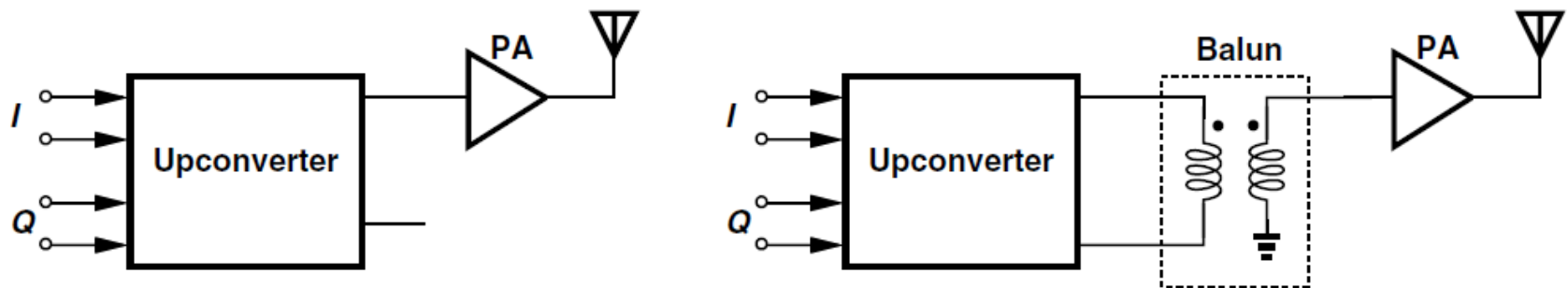[B. Razavi, RF Microelectronics]

Single Ended and Differential



- ❑ The antenna is typically single-ended, and single-ended RF circuits are much simpler to test
- ❑ Single-ended transmitter “waste” half of the voltage gain because they sense only one output of the upconverter



- ❑ A balun can be interposed between upconverter and PA
- ❑ But the balun introduces its own loss, especially if it is integrated on the chip

[B. Razavi, RF Microelectronics]


Bond Wires

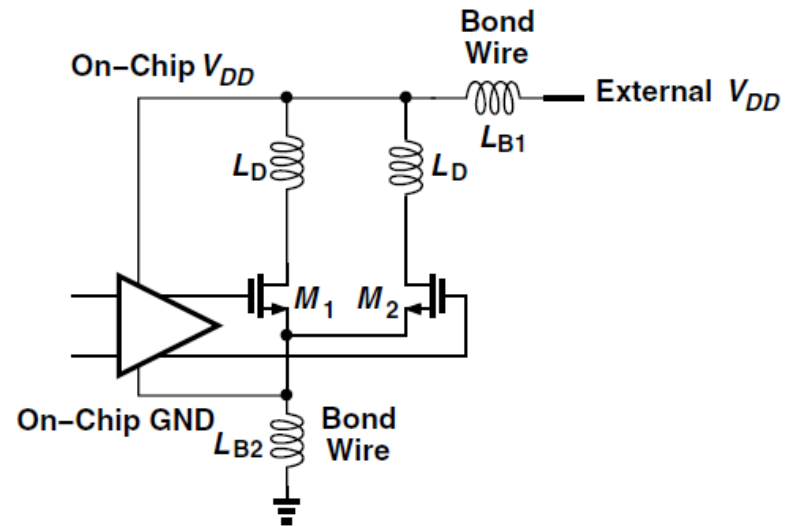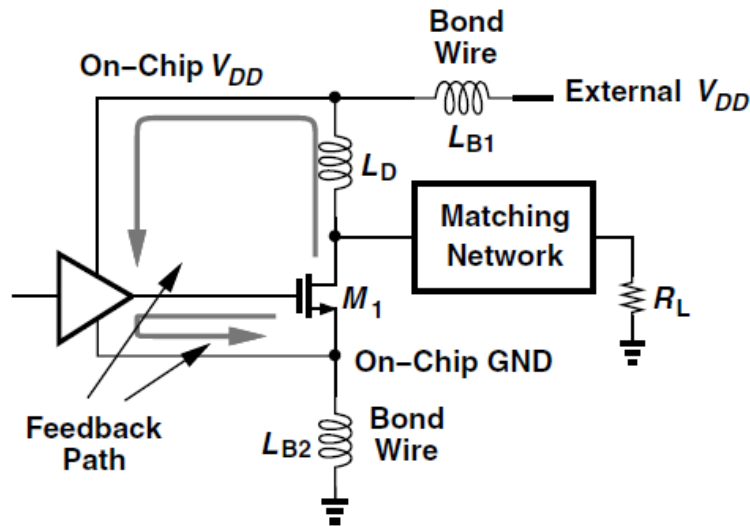

- ❑ Single-ended PAs stems from very large transient currents that they pull from the supply to the ground
- ❑ The resonance or impedance transformation is altered, and allows signal to travel back through the supply line
- ❑ The ground bond wire inductance degenerates the output stage and introduces feedback


[B. Razavi, RF Microelectronics]

Differential PA

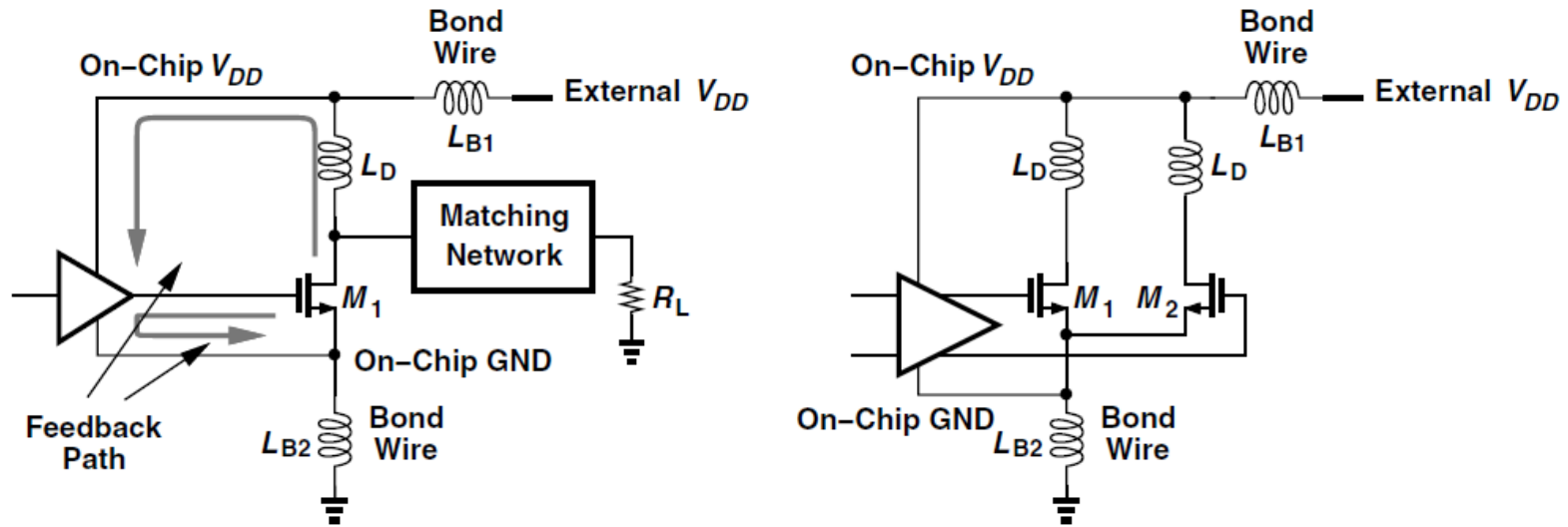

- ❑ A differential PA draws much smaller transient currents from supply and ground lines, exhibiting less sensitivity to the bond-wire inductors and creating less feedback
- ❑ The degeneration issue is also relaxed considerably



Differential PA

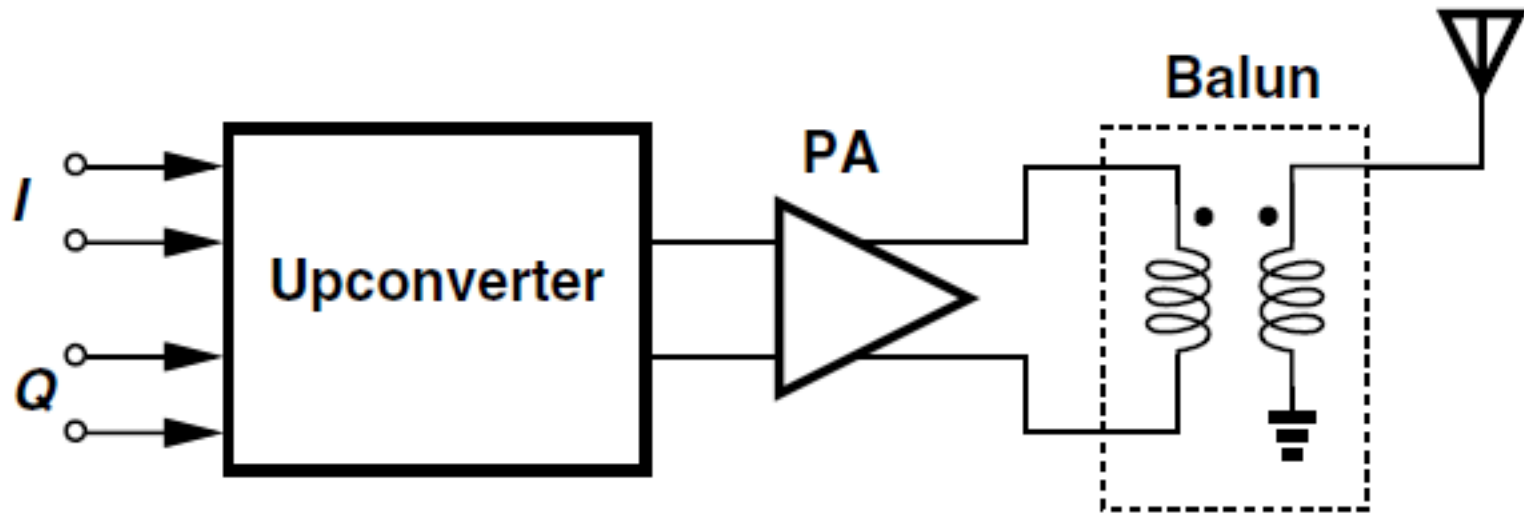

- ❑ The use of a differential PA ameliorates both the voltage gain and package parasitic issues
- ❑ The PA must still drive a single-ended antenna in most cases, so a balun must be inserted between PA and antenna
- ❑ Differential PA can also reduce LO pulling by propagating symmetrically toward the LO

[B. Razavi, RF Microelectronics]



Class-A PA

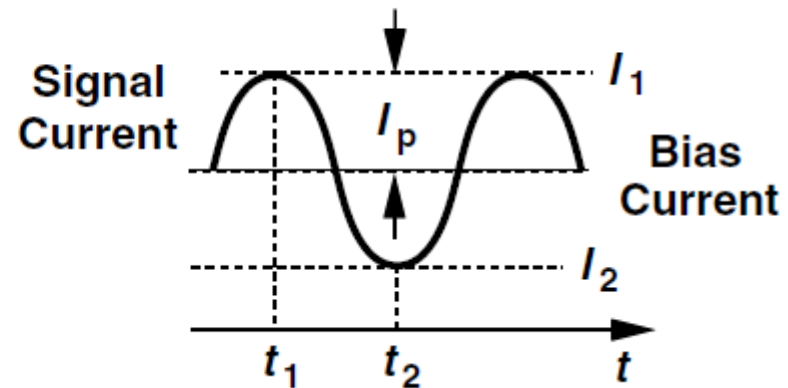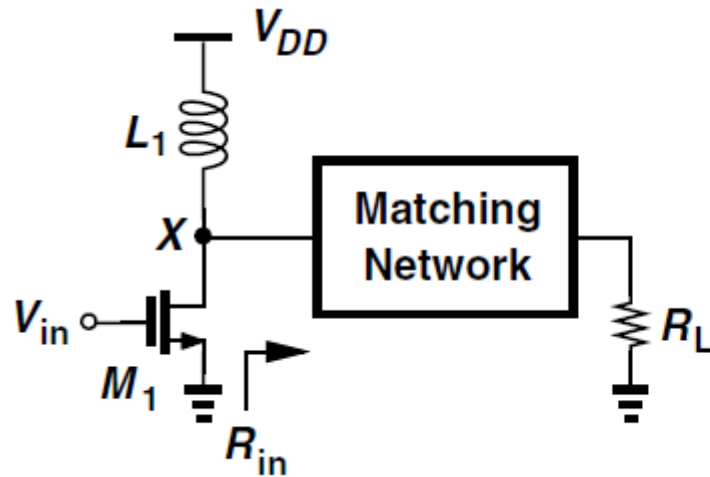

- ❑ Class-A PAs are defined as circuits in which the transistor(s) remain on and operate linearly across the full input and output range
- ❑ The transistor bias current is chosen higher than the peak signal current
- ❑ The input voltage should be small to ensure the linearity

[B. Razavi, RF Microelectronics]

Efficiency of Class-A PA

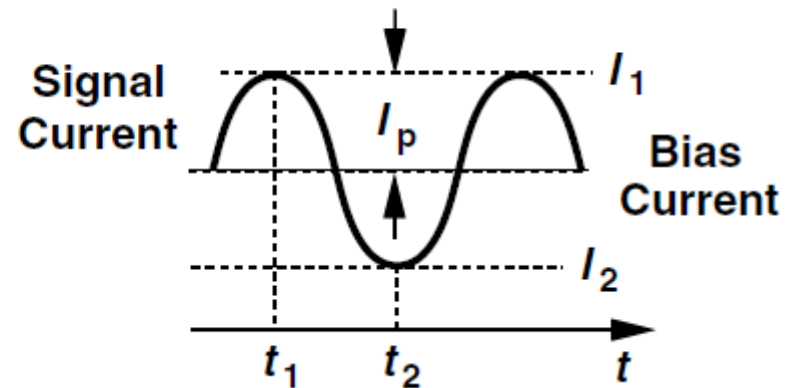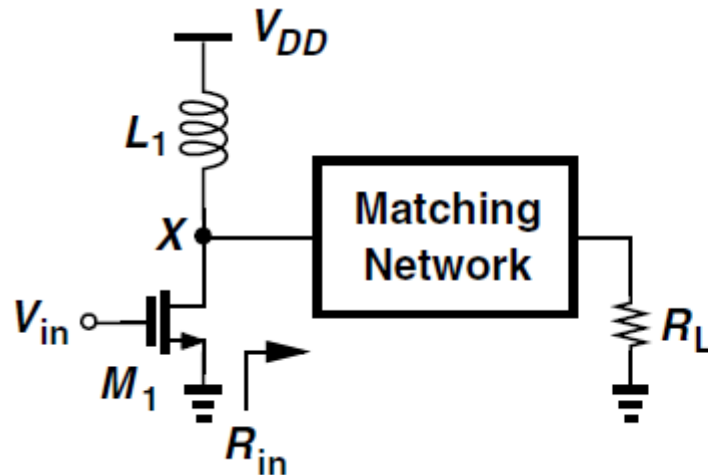

- To reach maximum efficiency, we allow V_X to reach $2V_{DD}$ and nearly zero. Thus, the power delivered to the load

$$(2V_{DD}/2)^2 / (2R_{in}) = V_{DD}^2 / (2R_{in})$$



- The DC power is consumed by the constant current of V_{DD}/R_{in} from the supply voltage, so

$$\eta = \frac{V_{DD}^2 / (2R_{in})}{V_{DD}^2 / R_{in}} = 50\%$$

- The other 50% of the supply power is dissipated by transistor

[B. Razavi, RF Microelectronics]



Efficiency of Class-A PA

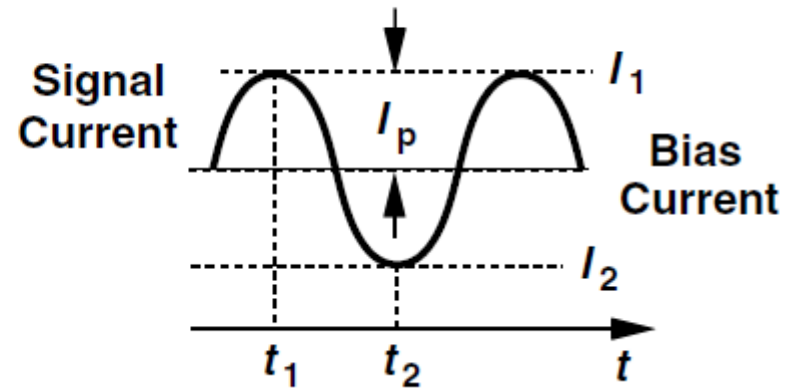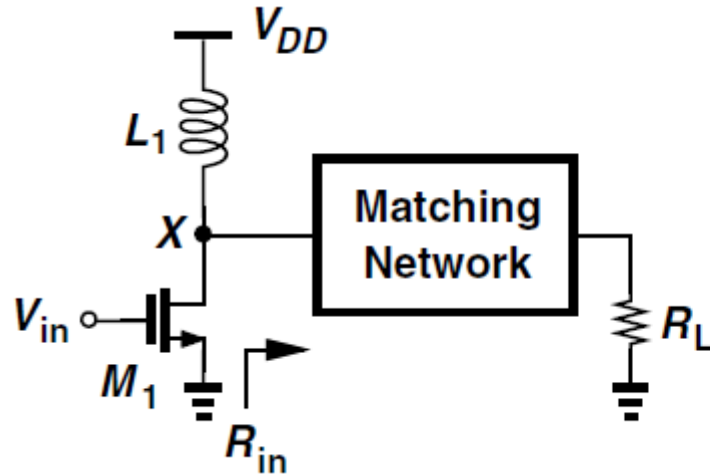

- The assumptions lead to an efficiency of 50% in class-A PA:
- The drain peak-to-peak voltage swing is equal to twice the supply voltage with no reliability or breakdown issues
 - The transistor barely turns off (tolerable nonlinearity)
 - The matching network is lossless


[B. Razavi, RF Microelectronics]

Conduction Angle

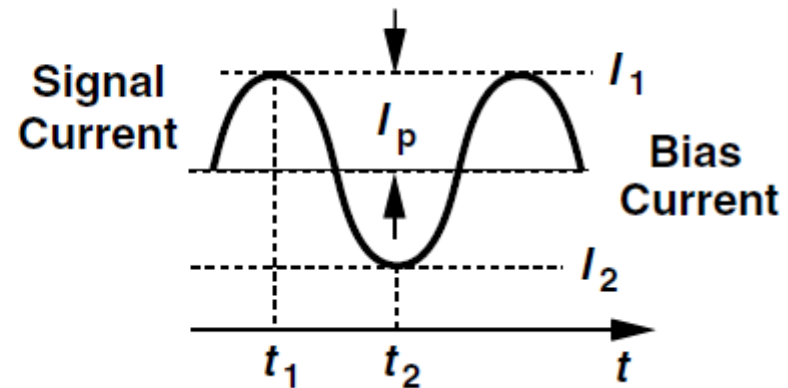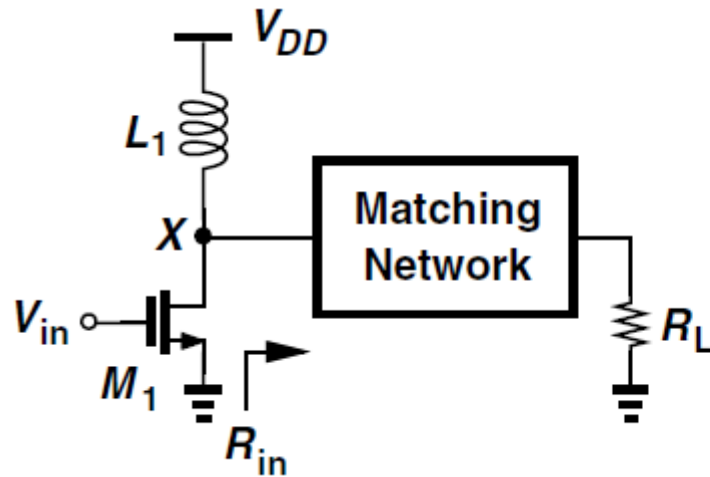

- ❑ The conduction angle is defined as the percentage of the signal period during which the transistor(s) remain on multiplied by 360°
- ❑ In class-A stages, the conduction angle is 360° because the output transistor is always on




Class-B PA

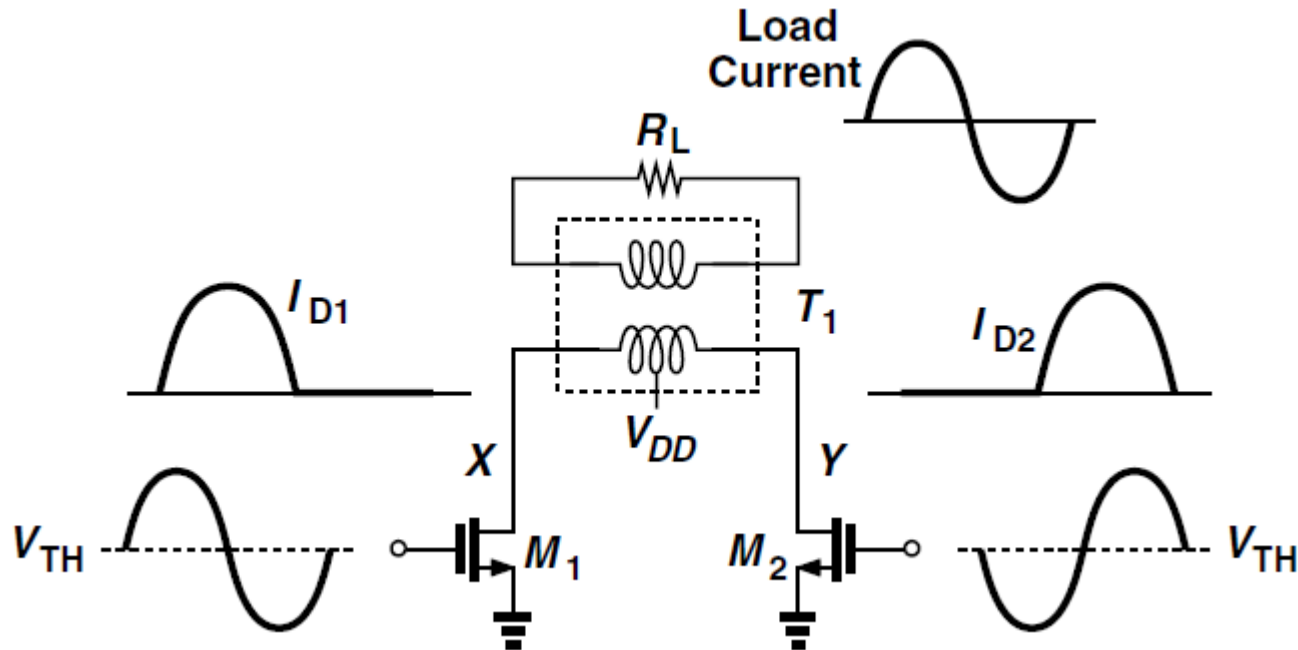

- ❑ The drain currents of M_1 and M_2 are combined by a transformer
- ❑ Each transistor turns off for half of period (i.e., the conduction angle is 180°)


[B. Razavi, RF Microelectronics]

Current Combine

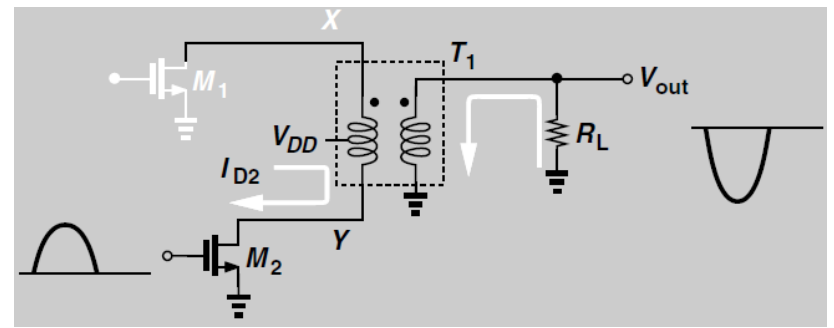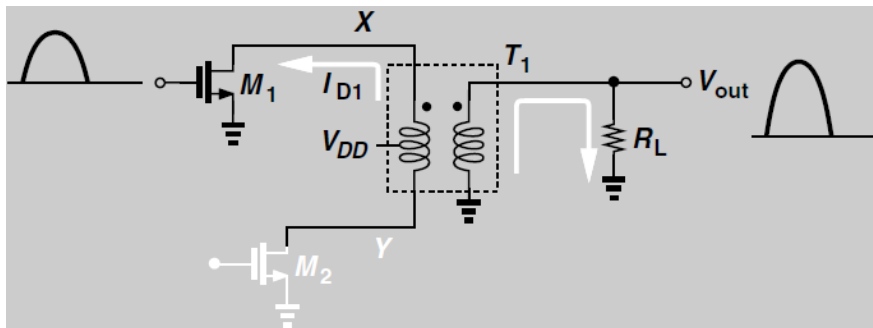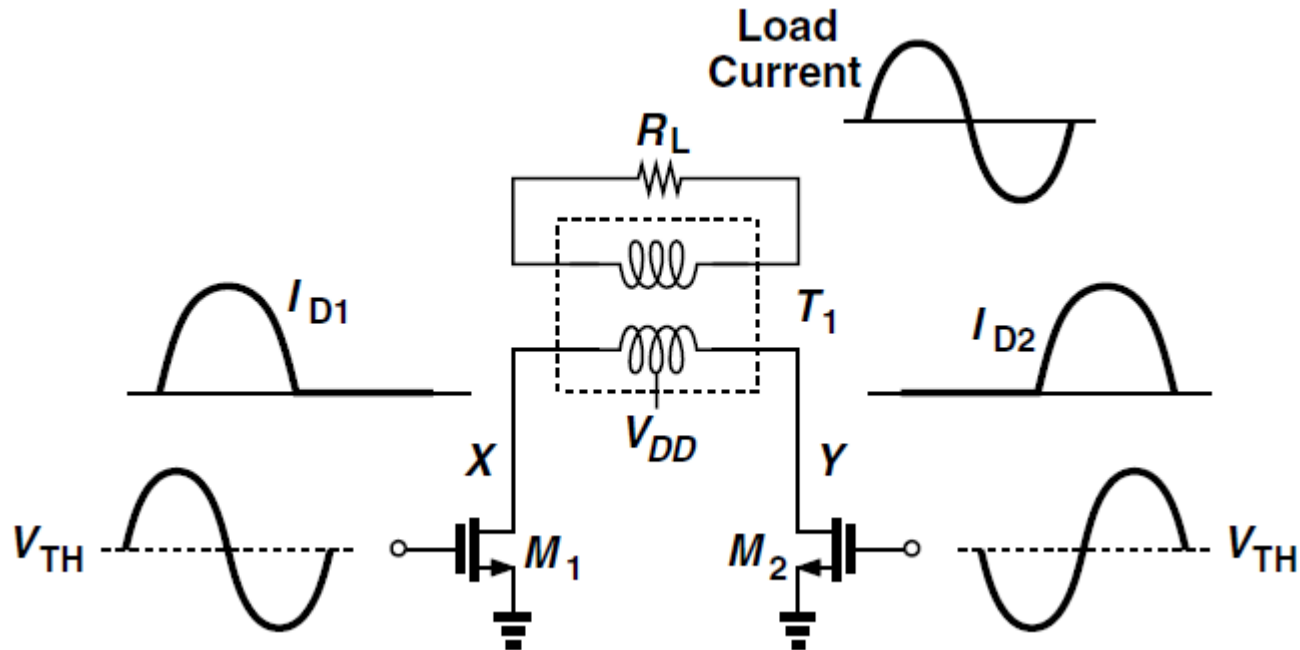

[B. Razavi, RF Microelectronics]

Efficiency of Class-B PA

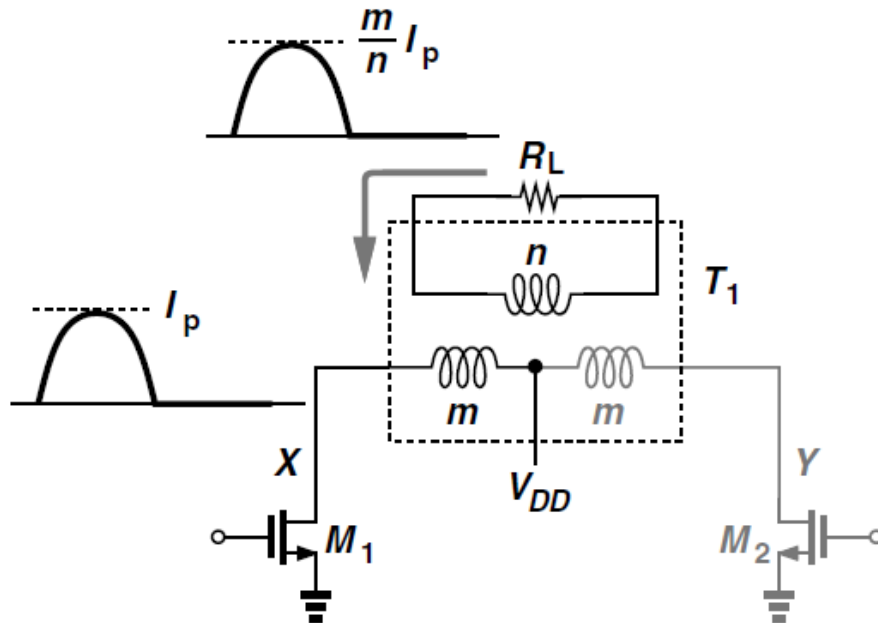

□ Since two current waveforms are drawn from V_{DD} in each period, the average power provided by V_{DD} is equal to

$$P_{supp} = 2 \frac{I_p}{\pi} V_{DD}$$


□ The transistor current $I_{D1} = I_p \sin \omega_0 t$ produces a similar current in the load $I_L = (m/n) I_p \sin \omega_0 t$, producing an average power:

$$P_{out} = \left(\frac{m}{n} \right)^2 \frac{R_L I_p^2}{2}$$

$$\eta = \frac{\pi}{4 V_{DD}} \left(\frac{m}{n} \right)^2 I_p R_L$$

[B. Razavi, RF Microelectronics]

Efficiency of Class-B PA

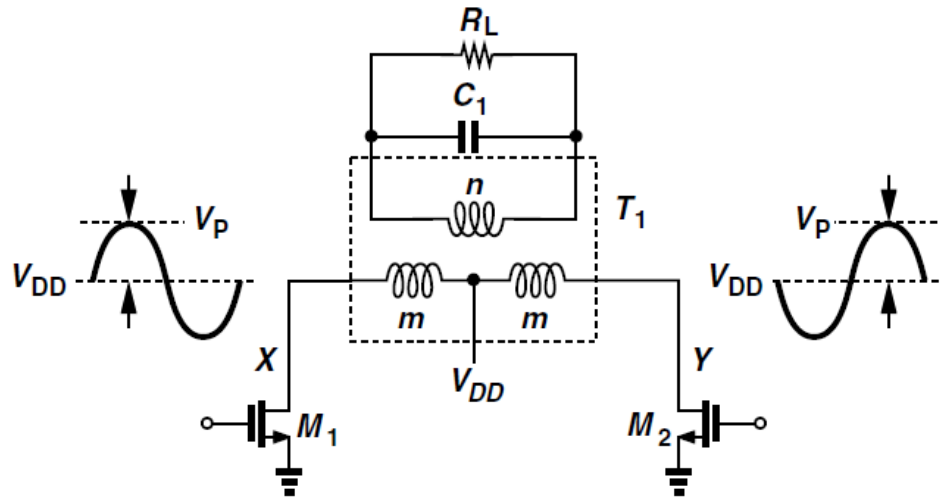

□ In the presence of a resonant load, the primary transformer senses a voltage given by

$$V_{XY} = 2V_p \sin \omega_0 t$$

□ Experiencing a ratio of $n/(2m)$ outputs a voltage:

$$V_{out}(t) = \left(\frac{n}{2m} \right) 2V_p \sin \omega_0 t = \frac{m}{n} I_p R_L \sin \omega_0 t \quad V_p = \frac{m^2}{n^2} I_p R_L$$

□ We choose $V_p = V_{DD}$ to maximize the efficiency: $\eta = \frac{\pi}{4} \approx 79\%$

□ In recent RF design literature, class B operation often refers to half of the circuits, which still has a maximum efficiency of $\pi/4$



[B. Razavi, RF Microelectronics]

Class-AB PA

- ❑ The term “class AB” is sometimes used to refer to a single-ended PA whose conduction angle falls between 180° and 360° , i.e., in which the output transistor turns off for less than half of a period
- ❑ From another perspective, a class-AB PA is less linear than a class A stage and more linear than a class B stage
- ❑ Class-AB PA is usually accomplished by reducing the input voltage swing and hence backing off from the 1-dB compression point

Class-C PA

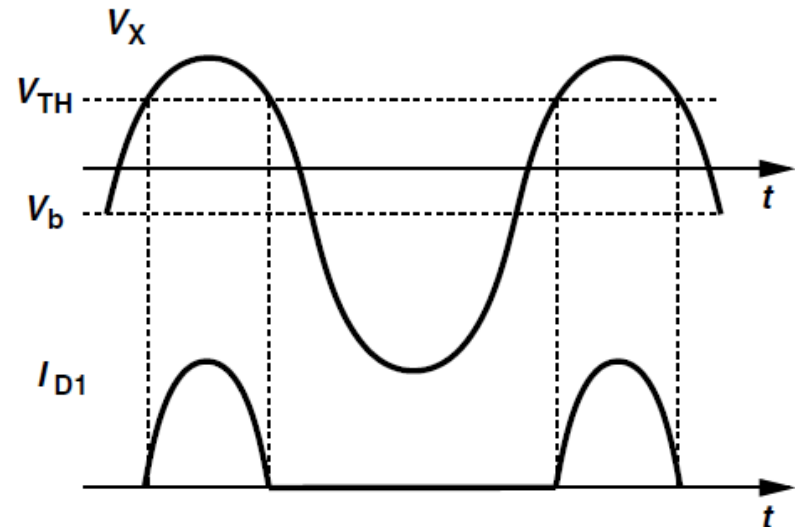
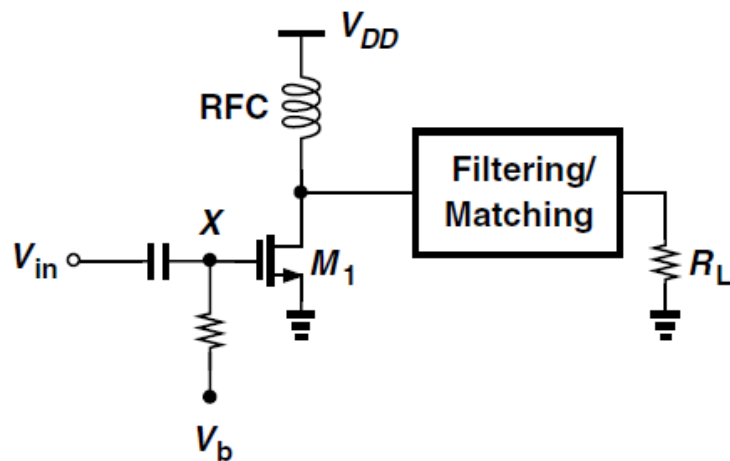
- ❑ Class A and B stages indicate that a smaller conduction angle yields a higher efficiency
- ❑ In class C stages, this angle is reduced further (and the circuit becomes more nonlinear)



- ❑ To avoid large harmonic levels at the antenna, the input/output matching network must provide some filtering


[B. Razavi, RF Microelectronics]

Class-C PA

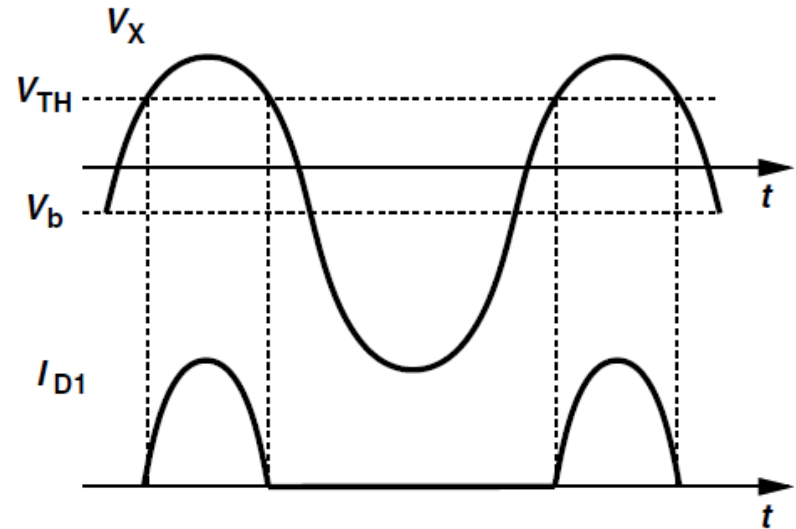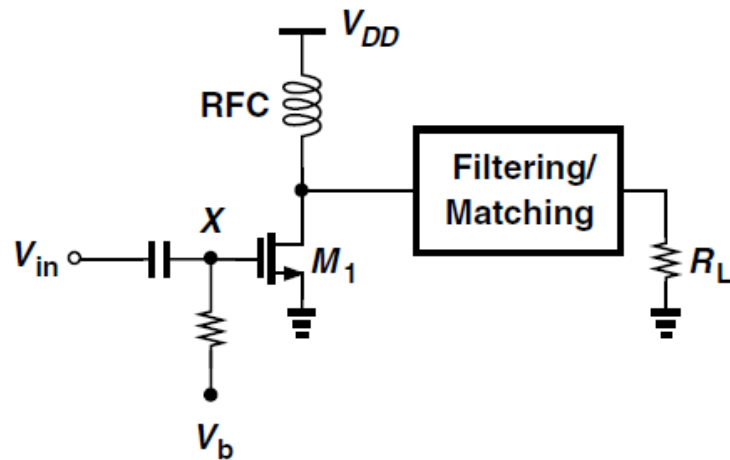

- ❑ The distinction between class C and one-transistor class B stages is in the conduction angle θ
- ❑ As θ decreases, the transistor is on for a smaller fraction of the period, thus dissipating less power, and meanwhile the PA outputs less power

Efficiency of Class-C PA

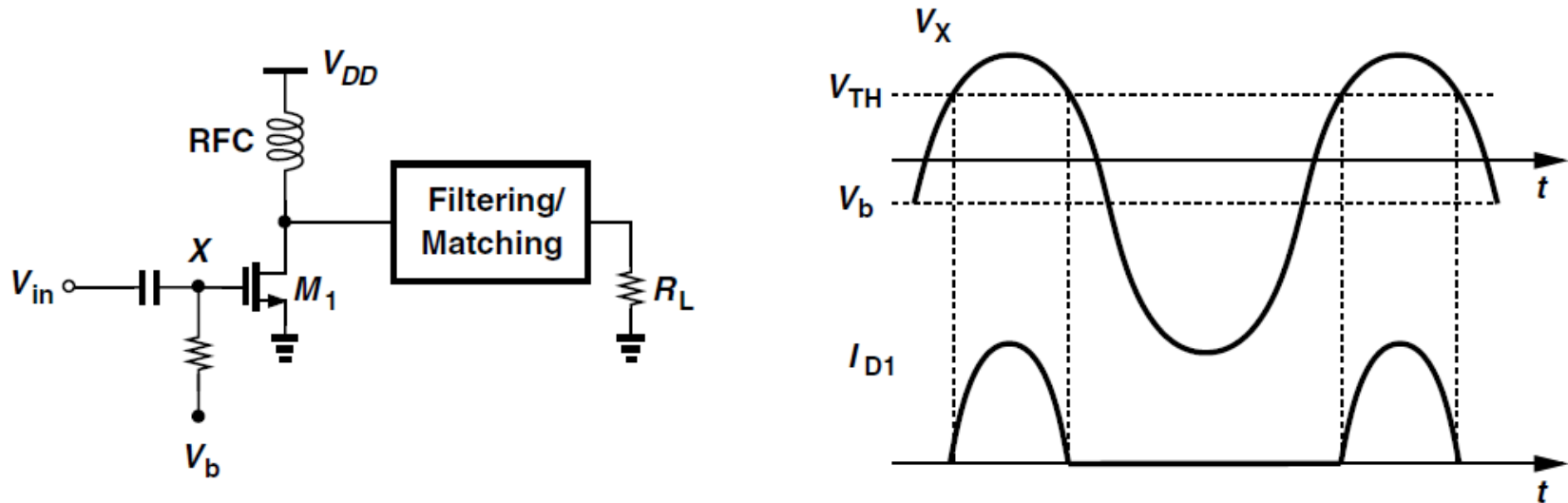

□ If the drain current of M_1 is assumed to be the peak section of a sinusoid and the drain voltage is a sinusoid having a peak amplitude of V_{DD} , then the efficiency can be obtained as

$$\eta = \frac{1}{4} \frac{\theta - \sin \theta}{\sin(\theta/2) - (\theta/2) \cos(\theta/2)}$$

□ This relation suggests an efficiency of 100% as θ approaches zero

[B. Razavi, RF Microelectronics]

Efficiency of Class-C PA



- ❑ The maximum efficiency of class-C PA is 100%, while the actual power delivered to the load:

$$P_{out} \propto \frac{\theta - \sin \theta}{1 - \cos(\theta/2)}$$

- ❑ The output power falls to zero as θ approaches zero
- ❑ In other words, a class-C PA provides a high efficiency only if it delivers a fraction of the peak output power
- ❑ The small conduction angle dictates that the output transistor be very wide so as to deliver a high current for a short amount of time

Harmonic Enhanced Class-A

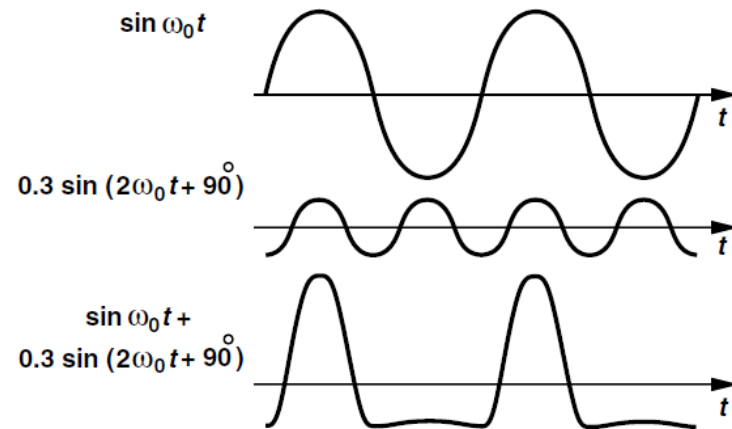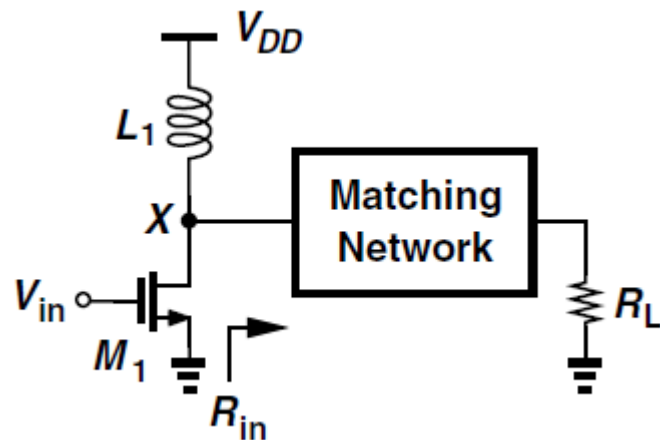
- If we minimize the time during which the transistor carries a large current and sustains a large voltage, we can reduce the power consumed by the transistor and raise the efficiency



- The input impedance of matching network is low at the fundamental and high at the second harmonic
- The overlap time between the voltage across and the current flowing in the output transistor is reduced

[B. Razavi, RF Microelectronics]

Harmonic Enhanced Class-A

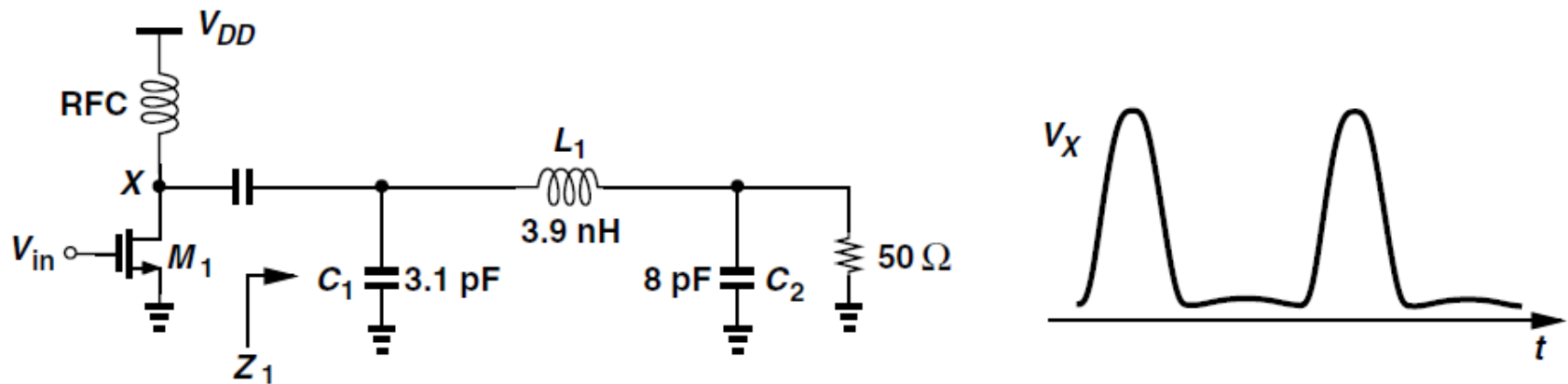


- ❑ The technique realizes different impedances for different harmonics to make the drain voltage approach a square wave
- ❑ A matching network transforms the 50 Ω load to $Z_1 = 90 \Omega$ at $f = 850 \text{ MHz}$ and $Z_2 = 330 \Omega$ at $2f = 1.7 \text{ GHz}$
- ❑ The second harmonic is enhanced by a factor of 37, and then the PA achieves 73% efficiency

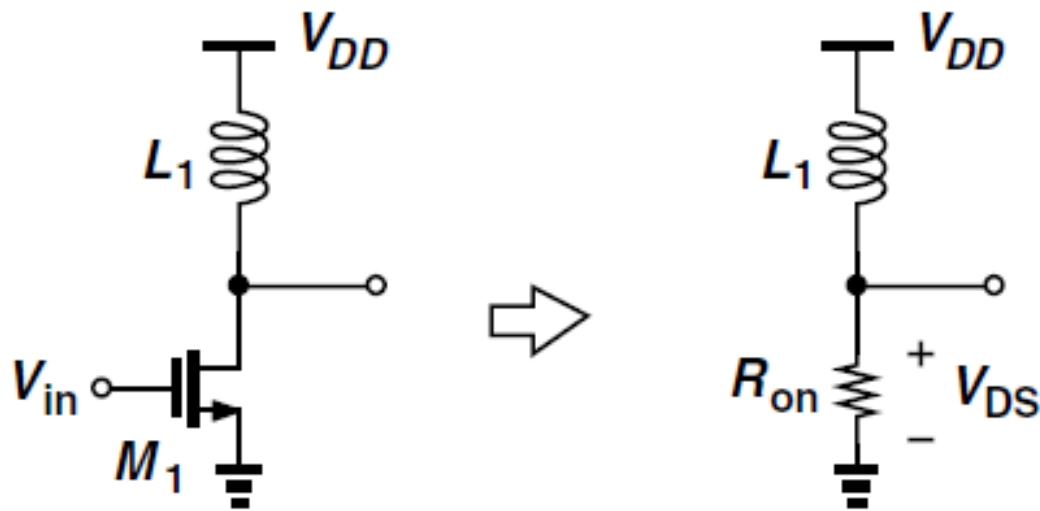[B. Razavi, RF Microelectronics]

Class-E PA

- Class-E PAs are nonlinear amplifiers that achieve efficiencies approaching 100% while delivering full power





- If the transistor operates as a switch, rather than a voltage dependent current source, ideally turning on and off abruptly, resulting in a class-E PA (switching PA)

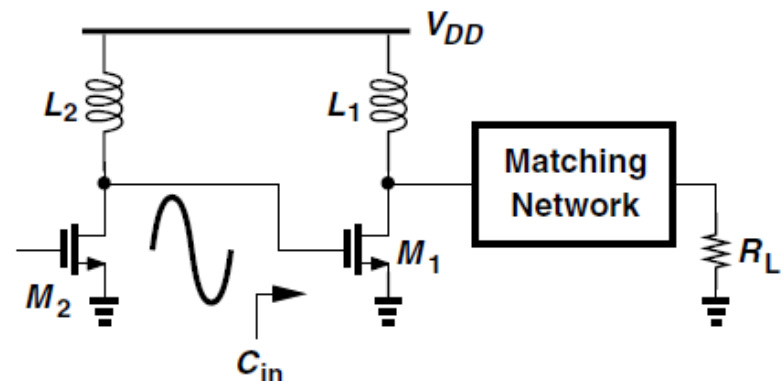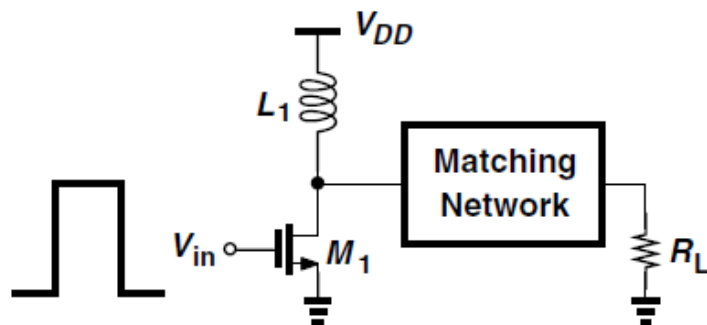[B. Razavi, RF Microelectronics]


Class-E PA

- ❑ A serious dilemma in class-E PA design is that the gate of transistor must be switched as abruptly as possible so as to maximize the efficiency
- ❑ But the input of transistor is usually a sinusoid waveform from previous stages



[B. Razavi, RF Microelectronics]


Class-E PA

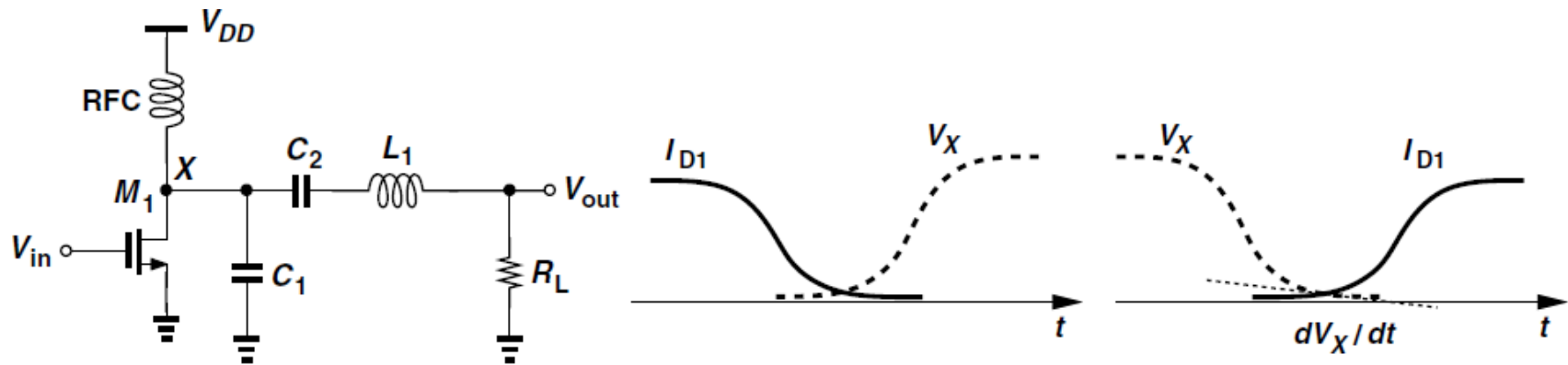

- ❑ As the switch turns off, V_X remains low long enough for the current to drop to zero (guaranteed by C_1)
- ❑ V_X reaches zero just before the switch turns on, ensuring that the voltage and current of transistor do not overlap
- ❑ In the vicinity of the turn-on point, dV_X/dt is also near zero to lower the sensitivity to violations


[B. Razavi, RF Microelectronics]

Class-E PA

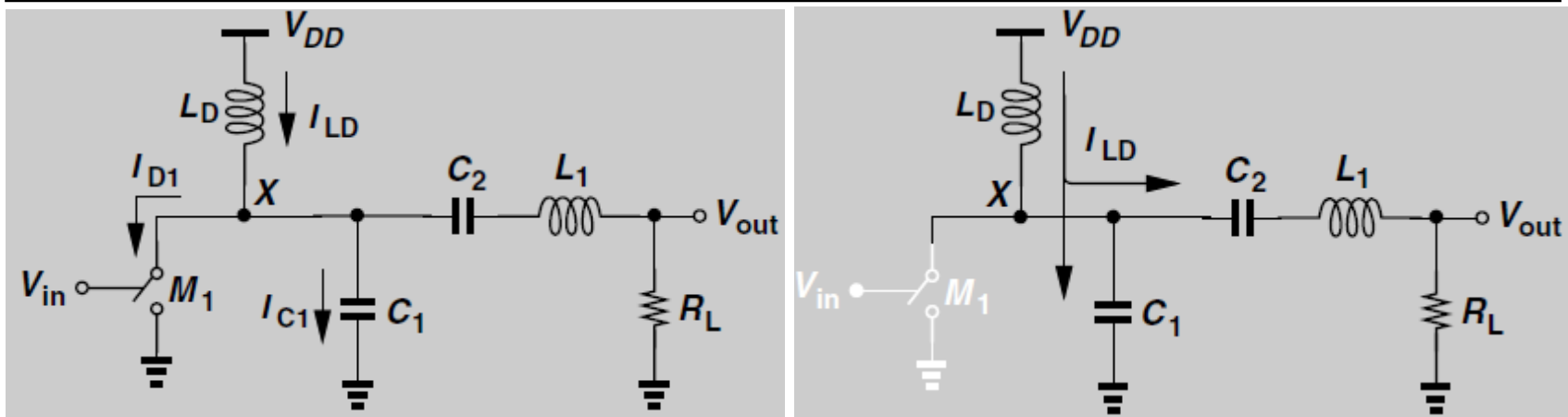

- ❑ One half cycle is dedicated to charging L_D at a small voltage V_X
- ❑ When M_1 turns off, the inductor current begins to flow through C_1 , and V_X start to go up
- ❑ The matching network attenuates higher harmonics of V_X , yielding a nearly sinusoidal output


Class-E PA

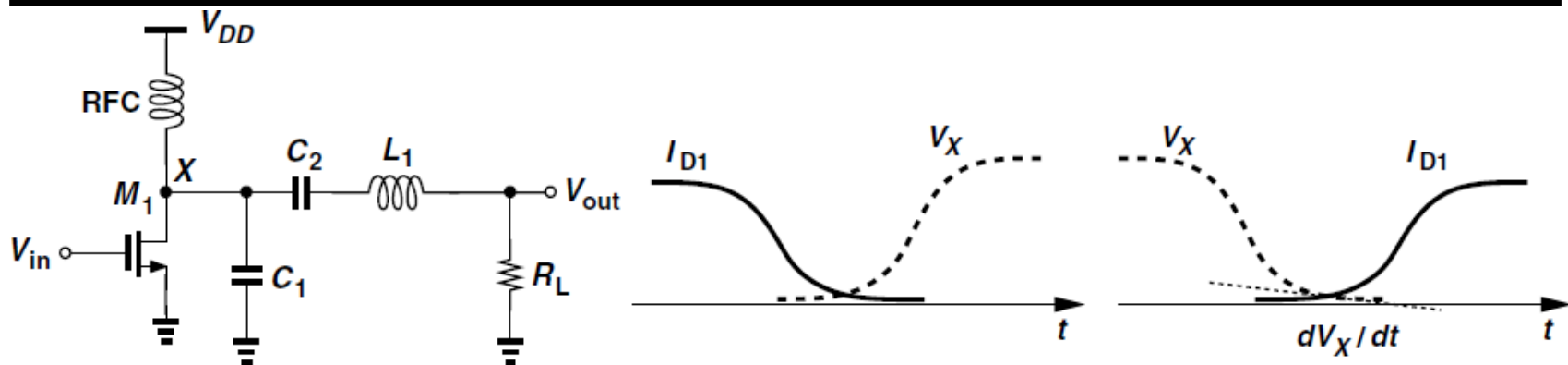

- ❑ Class-E PA is quite nonlinear and exhibit a trade-off between efficiency and output harmonic content
- ❑ Class-E PA sustains a large peak voltage in the off state, raising serious device reliability or breakdown issues

Class-F PA

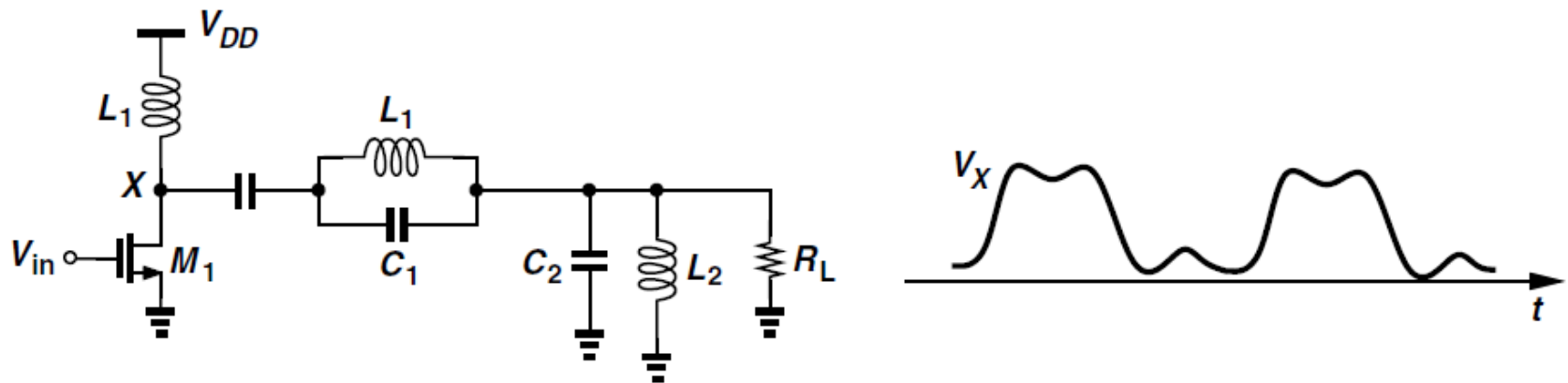
□ If the load network provides a high termination impedance at the second or third harmonics, the voltage waveform across the switch exhibits sharper edges than a sinusoid, thereby reducing the power loss in the transistor



□ The tank consisting of L_1 and C_1 resonates at three times the input frequency, and then V_X approaches a rectangular waveform with the addition of the third harmonic


[B. Razavi, RF Microelectronics]

Class-F PA

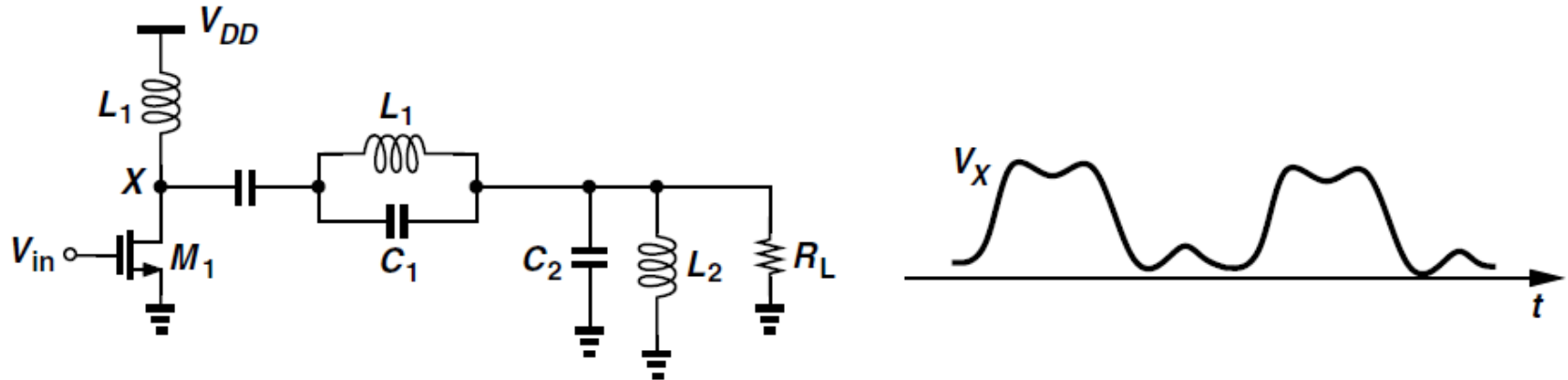

□ If the drain current of the transistor is assumed to be a half-wave rectified sinusoid, it can be proved that the peak efficiency of class F amplifiers is equal to 88% for third harmonic peaking

Class-D PA

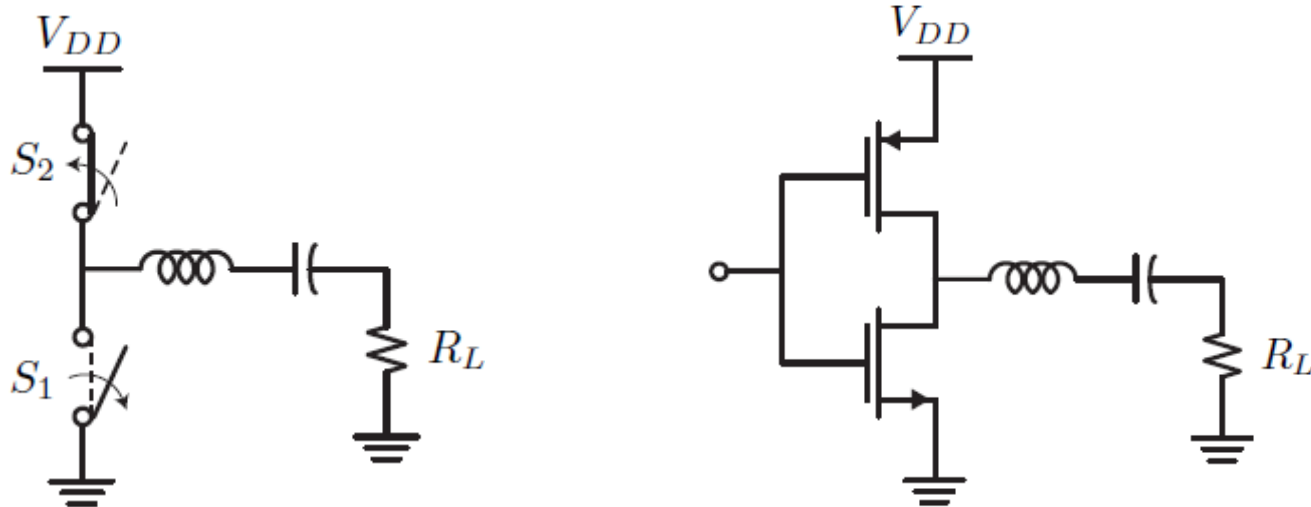


- ❑ If give up linearity, then we can create some intrinsically efficient amplifiers using switches. An ideal switch does not dissipate any power since either the voltage or current is zero
- ❑ MOS transistors make particularly good switches. The input voltage should be large enough
- ❑ A series LCR filter only allows the first harmonic of voltage to flow into the load

[Ali Niknejad, EE142 & EE242 of UC Berkeley]

Efficiency of Class-D PA

- ❑ We can see that the efficiency has to be 100% for an ideal switch. That's because there is no where for the DC power to flow except to the load
- ❑ The real efficiency is lowered by the switch-on resistance
- ❑ We can make our switches bigger to minimize the resistance, but this in turn increases the parasitic capacitance
- ❑ There are two forms of loss associated with the parasitic capacitance, the capacitor charging losses CV^2f and the parasitic substrate losses
- ❑ The power required to drive the switches also increases proportional to C_{gs} since we have to burn CV^2f power to drive the inverter


Class-S PA

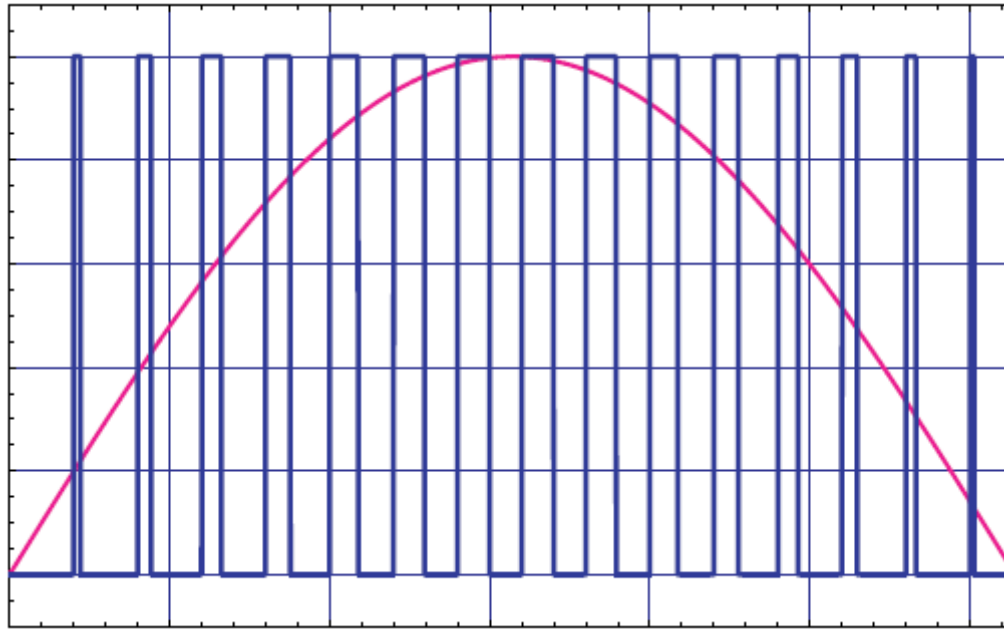

- ❑ If the switching rate is much higher than the fundamental, then amplitude modulation can be converted to pulse-width modulation
- ❑ A low-pass filter at the output faithfully recreates the envelope of the signal

[Ali Niknejad, EE142 & EE242 of UC Berkeley]

Class-S PA

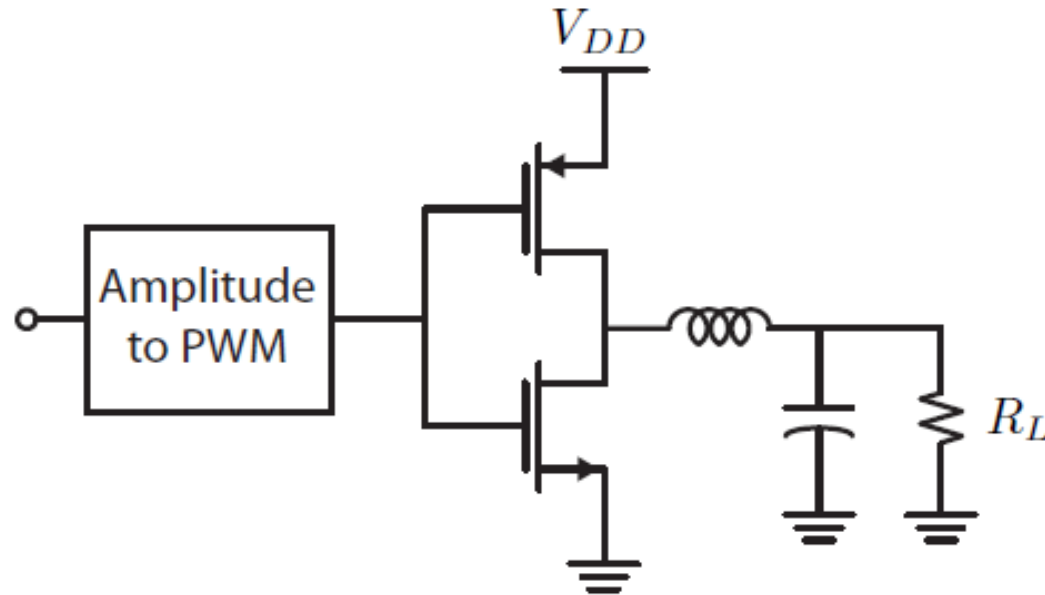

- ❑ Class S amplifiers are commonly used at low frequencies (audio) since the transistors can be switched at a much higher frequency than the fundamental
- ❑ This allows efficiencies approaching 100% with good linearity

[Ali Niknejad, EE142 & EE242 of UC Berkeley]

Efficiency Summary

Typology	Efficiency
Class A	50%
Harmonic Enhanced Class A	~73%
Class B	79%
Class AB	50%-79%
Class C	~100%
Class E	~100%
Class F	~88%
Class D	~100%
Class S	~100%